

CHAPTER 17

17.1

$$A_v(s) = 25 \frac{s^2}{(s+1)(s+20)} \quad | \quad A_{mid} = 25 \quad | \quad F_L(s) = \frac{s^2}{(s+1)(s+20)} \quad | \quad \text{Poles : } -1, -20 \quad | \quad \text{Zeros : } 0, 0$$

$$\text{yes, } s = -20 \quad | \quad A_v(s) \approx 25 \frac{s}{(s+20)} \quad | \quad \omega_L = 20 \frac{\text{rad}}{s} \quad | \quad f_L = \frac{\omega_L}{2\pi} \cong \frac{20}{2\pi} = 3.18 \text{ Hz}$$

$$f_L = \frac{1}{2\pi} \sqrt{20^2 + 1^2 - 2(0)^2 - 2(0)^2} = 3.19 \text{ Hz}$$

$$|A_v(j\omega)| = \frac{25\omega^2}{\sqrt{\omega^2 + 1^2} \sqrt{\omega^2 + 20^2}} \quad | \quad \text{MATLAB : } -3.19 \text{ Hz}$$

17.2

$$A_v(s) = 250 \frac{s^2}{(s+100)(s+500)} \quad | \quad A_{mid} = 250 \quad | \quad F_L(s) = \frac{s^2}{(s+100)(s+500)}$$

$$\text{Poles : } -100, -500 \frac{\text{rad}}{s} \quad | \quad \text{Zeros : } 0, 0 \quad | \quad \text{Yes, a 5:1 split is sufficient} \quad | \quad s = -500$$

$$A_v(s) \approx 250 \frac{s}{(s+500)} \quad | \quad \omega_L \cong 500 \frac{\text{rad}}{s} \quad | \quad f_L \cong \frac{500}{2\pi} = 79.6 \text{ Hz}$$

$$f_L \cong \frac{1}{2\pi} \sqrt{100^2 + 500^2 - 2(0)^2 - 2(0)^2} = 81.2 \text{ Hz}$$

$$|A_v(j\omega)| = \frac{250\omega^2}{\sqrt{\omega^2 + 100^2} \sqrt{\omega^2 + 500^2}} \quad | \quad \text{MATLAB : } 82.6 \text{ Hz}$$

17.3

$$A_v(s) = -150 \frac{s(s+15)}{(s+12)(s+20)} \quad | \quad A_{mid} = -150 \quad | \quad F_L(s) = \frac{s(s+15)}{(s+12)(s+20)}$$

$$\text{Poles : } -12, -20 \frac{\text{rad}}{s} \quad | \quad \text{Zeros : } 0, -15 \frac{\text{rad}}{s} \quad | \quad \text{No, the poles and zeros are closely spaced.}$$

$$f_L \cong \frac{1}{2\pi} \sqrt{12^2 + 20^2 - 2(0)^2 - 2(15)^2} = 1.54 \text{ Hz}$$

$$|A_v(j\omega)| = \frac{150\omega\sqrt{\omega^2 + 15^2}}{\sqrt{\omega^2 + 12^2} \sqrt{\omega^2 + 20^2}} \quad | \quad \text{MATLAB : } f_L = 2.72 \text{ Hz} \quad | \quad \omega_L = 17.1 \frac{\text{rad}}{s}$$

Note that $\omega_L = 17.1 \text{ rad/s}$ does not satisfy the assumption used to obtain Eq. (17.15), and the estimate using Eq. (17.15) is rather poor.

17.4

$$A_v(s) = \frac{(2 \times 10^{11})(10^{-4})(10^{-5})}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} = \frac{200}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)} \quad | \quad A_{mid} = 200 \quad | \quad F_H(s) = \frac{1}{\left(\frac{s}{10^4} + 1\right)\left(\frac{s}{10^5} + 1\right)}$$

$$\text{Poles : } -10^4, -10^5 \frac{\text{rad}}{\text{s}} \quad | \quad \text{Yes : } A_v(s) \approx \frac{200}{\frac{s}{10^4} + 1} \quad | \quad \omega_H \cong 10^4 \frac{\text{rad}}{\text{s}} \quad | \quad f_H \cong \frac{10^4}{2p} = 1.59 \text{ kHz}$$

$$f_H \cong \frac{1}{2p} \left(\sqrt{\left(\frac{1}{10^4}\right)^2 + \left(\frac{1}{10^5}\right)^2} - 2\left(\frac{1}{\infty}\right)^2 - 2\left(\frac{1}{\infty}\right)^2 \right)^{-1} = 1.58 \text{ kHz}$$

$$|A_v(j\omega)| = \frac{2 \times 10^{11}}{\sqrt{\omega^2 + (10^4)^2} \sqrt{\omega^2 + (10^5)^2}} \quad | \quad \text{MATLAB : } f_H = 1.58 \text{ kHz}$$

17.5

$$A_v(s) = \frac{(2 \times 10^9) \left(1 + \frac{s}{2 \times 10^9}\right)}{10^7 \left(1 + \frac{s}{10^7}\right) \left(1 + \frac{s}{10^9}\right)} = 200 \frac{\left(1 + \frac{s}{2 \times 10^9}\right)}{\left(1 + \frac{s}{10^7}\right) \left(1 + \frac{s}{10^9}\right)}$$

$$A_{mid} = 200 \quad | \quad F_H(s) = \frac{\left(1 + \frac{s}{2 \times 10^9}\right)}{\left(1 + \frac{s}{10^7}\right) \left(1 + \frac{s}{10^9}\right)} \quad | \quad \text{Poles : } -10^7, -10^9 \quad \text{Zeros : } -2 \times 10^9, \infty$$

$$\text{Yes : } A_v(s) \approx \frac{200}{\left(1 + \frac{s}{10^7}\right)} \quad | \quad \omega_H \cong 10^7 \frac{\text{rad}}{\text{s}} \quad | \quad f_H \cong \frac{10^4}{2p} = 1.59 \text{ MHz}$$

$$f_H = \frac{1}{2p} \left(\sqrt{\left(\frac{1}{10^7}\right)^2 + \left(\frac{1}{10^9}\right)^2} - 2\left(\frac{1}{2 \times 10^9}\right)^2 - 2\left(\frac{1}{\infty}\right)^2 \right)^{-1} = 1.59 \text{ MHz}$$

$$|A_v(j\omega)| = \frac{2 \times 10^9 \sqrt{\omega^2 + (2 \times 10^9)^2}}{\sqrt{\omega^2 + (10^7)^2} \sqrt{\omega^2 + (10^9)^2}} \quad | \quad \text{MATLAB : } f_H = 1.59 \text{ MHz}$$

17.6

$$A_v(s) = \frac{(4 \times 10^9)(5 \times 10^5) \left(1 + \frac{s}{5 \times 10^5}\right)}{(1.3 \times 10^5)(2 \times 10^6) \left(1 + \frac{s}{1.3 \times 10^5}\right) \left(1 + \frac{s}{2 \times 10^6}\right)} = 7692 \frac{\left(1 + \frac{s}{5 \times 10^5}\right)}{\left(1 + \frac{s}{1.3 \times 10^5}\right) \left(1 + \frac{s}{2 \times 10^6}\right)}$$

$$A_{mid} = 7692 \quad | \quad F_H(s) = \frac{\left(1 + \frac{s}{5 \times 10^5}\right)}{\left(1 + \frac{s}{1.3 \times 10^5}\right) \left(1 + \frac{s}{2 \times 10^6}\right)} \quad | \quad \text{Poles : } -1.3 \times 10^5, -2 \times 10^6 \frac{\text{rad}}{\text{s}}$$

Zeros : $-5 \times 10^5 \frac{\text{rad}}{\text{s}}, \infty$ | No, the poles and zeros are closely spaced and will interact.

$$f_H \cong \frac{1}{2p} \sqrt{\left(\frac{1}{1.3 \times 10^5}\right)^2 + \left(\frac{1}{2 \times 10^6}\right)^2 - 2\left(\frac{1}{5 \times 10^5}\right)^2 - 2\left(\frac{1}{\infty}\right)^2} = 22.2 \text{ kHz}$$

$$|A_v(j\omega)| = \frac{4 \times 10^9 \sqrt{\omega^2 + (5 \times 10^5)^2}}{\sqrt{\omega^2 + (1.3 \times 10^5)^2} \sqrt{\omega^2 + (2 \times 10^6)^2}} \quad | \quad \text{MATLAB : } 22.1 \text{ kHz}$$

17.7

$$A_v(s) = \frac{10^8}{500(1000)} \frac{s^2}{(s+1)(s+2)} \frac{1}{\left(1 + \frac{s}{500}\right) \left(1 + \frac{s}{1000}\right)}$$

$$A_v(s) = 200 \left[\frac{s^2}{(s+1)(s+2)} \right] \left[\frac{1}{\left(1 + \frac{s}{500}\right) \left(1 + \frac{s}{1000}\right)} \right] = 200 F_L(s) F_H(s)$$

Poles; $-1, -2, -500, -1000 \frac{\text{rad}}{\text{s}}$ | Zeros : $0, 0, \infty, \infty$ | No. | No.

$$|A_v(j\omega)| = \frac{10^8 \omega^2}{\sqrt{1^2 + \omega^2} \sqrt{2^2 + \omega^2} \sqrt{500^2 + \omega^2} \sqrt{1000^2 + \omega^2}}$$

$$f_L = \frac{1}{2p} \sqrt{(1)^2 + (2)^2 - 2(0)^2 - 2(0)^2} = 0.356 \text{ Hz} \quad | \quad \text{MATLAB : } 0.380 \text{ Hz}$$

$$f_H = \frac{1}{2p} \sqrt{\left(\frac{1}{500}\right)^2 + \left(\frac{1}{1000}\right)^2 - 2\left(\frac{1}{\infty}\right)^2 - 2\left(\frac{1}{\infty}\right)^2} = 71.2 \text{ kHz} \quad | \quad \text{MATLAB : } 66.7 \text{ Hz}$$

17.8

$$A_v(s) = \frac{10^{10}(200)}{(100)^2(300)} \frac{s^2(s+1)}{(s+3)(s+5)(s+7)} \frac{\left(1 + \frac{s}{200}\right)}{\left(1 + \frac{s}{100}\right)^2 \left(1 + \frac{s}{300}\right)}$$

$$A_v(s) = 6.67 \times 10^5 \left[\frac{s^2(s+1)}{(s+3)(s+5)(s+7)} \right] \left[\frac{\left(1 + \frac{s}{200}\right)}{\left(1 + \frac{s}{100}\right)^2 \left(1 + \frac{s}{300}\right)} \right] = 6.67 \times 10^5 F_L(s) F_H(s)$$


No dominant pole at either low or high frequencies.

$$|A_v(j\omega)| = \frac{10^{10} \omega^2 \sqrt{\omega^2 + 1^2} \sqrt{\omega^2 + 200^2}}{\sqrt{\omega^2 + 3^2} \sqrt{\omega^2 + 5^2} \sqrt{\omega^2 + 7^2} (\omega^2 + 100^2) \sqrt{\omega^2 + 300^2}}$$


$$f_L = \frac{1}{2p} \sqrt{(3)^2 + (5)^2 + (7)^2 - 2(1)^2 - 2(0)^2} = 1.43 \text{ Hz} \quad | \quad \text{MATLAB} : 1.62 \text{ Hz}$$

$$f_H = \frac{1}{2p} \left(\sqrt{\left(\frac{1}{100}\right)^2 + \left(\frac{1}{100}\right)^2 + \left(\frac{1}{300}\right)^2 - 2\left(\frac{1}{200}\right)^2 - 2\left(\frac{1}{\infty}\right)^2} \right)^{-1} = 12.5 \text{ Hz} \quad | \quad \text{MATLAB} : 10.6 \text{ Hz}$$

17.9

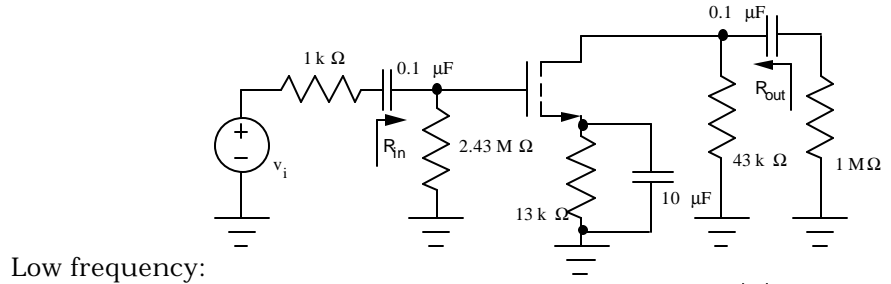

Low frequency:

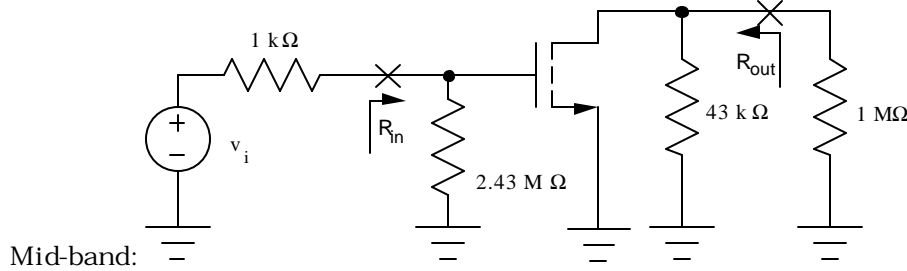

Mid-band:

$$A_{vt} = \frac{v_d}{v_g} = -g_m R_L = -g_m (R_{out} \parallel R_3) \quad | \quad A_{mid} = \frac{R_{in}}{R_i + R_{in}} A_{vt} \quad | \quad g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.2 \text{ mA})}{1 \text{ V}} = 0.400 \text{ mS}$$

$$R_{in} = 2.43 \text{ M}\Omega \quad | \quad R_{out} = R_D \parallel r_o \cong R_D = 43 \text{ k}\Omega \quad \text{assuming } I = 0 \text{ since it is not specified.}$$

$$A_{mid} = -\left(\frac{2.43 \text{ M}\Omega}{1 \text{ k}\Omega + 2.43 \text{ M}\Omega} \right) (0.400 \text{ mS}) (43 \text{ k}\Omega \parallel 1 \text{ M}\Omega) = -16.5$$


$$\omega_1 = \frac{1}{(10^{-7} \text{ F})(2.43 \text{ M}\Omega + 1 \text{ k}\Omega)} = 4.11 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_2 = \frac{1}{(10^{-7} \text{ F})(43 \text{ k}\Omega + 1 \text{ M}\Omega)} = 9.59 \frac{\text{rad}}{\text{s}}$$

$$\omega_3 = \frac{1}{(10^{-5} \text{ F}) \left(13 \text{ k}\Omega \parallel \frac{1}{g_m} \right)} = \frac{1}{(10^{-5} \text{ F})(13 \text{ k}\Omega \parallel 2.5 \text{ k}\Omega)} = 47.7 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_z = \frac{1}{(10^{-5} \text{ F})(13 \text{ k}\Omega)} = 7.69 \frac{\text{rad}}{\text{s}}$$


$$\omega_3 \text{ is dominant} : f_L \cong \frac{\omega_3}{2p} = 7.59 \text{ Hz}$$

$$\text{Using Eq. (17.16) yields} : f_L \cong \frac{1}{2p} \sqrt{(4.11)^2 + (9.59)^2 + (47.7)^2 - 2(7.69)^2} = 7.58 \text{ Hz}$$

17.10

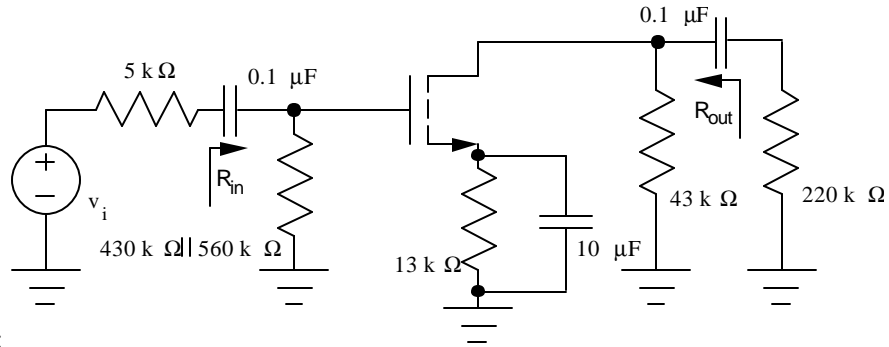

Low frequency:

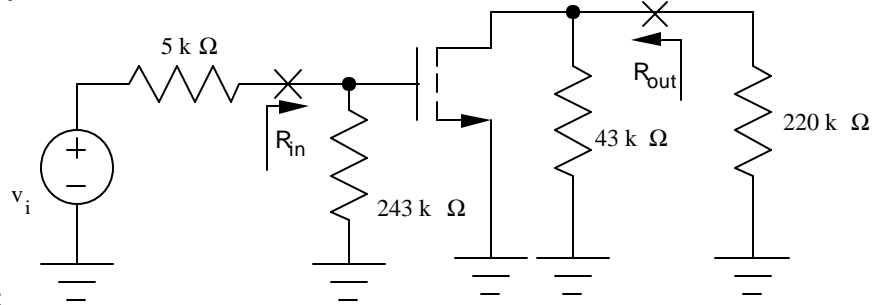

Mid-band:

$$A_{vt} = \frac{v_d}{v_g} = -g_m R_L = -g_m (R_{out} \parallel R_3) \quad | \quad A_{mid} = \frac{R_{in}}{R_i + R_{in}} A_{vt} \quad | \quad g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.2mA)}{1V} = 0.400mS$$

$$R_{in} = 243k\Omega \quad | \quad R_{out} = R_D \parallel r_o \cong R_D = 43k\Omega \quad \text{assuming } I = 0 \text{ since it is not specified.}$$

$$A_{mid} = -\left(\frac{243k\Omega}{5k\Omega + 243k\Omega} \right) (0.400mS) (43k\Omega \parallel 220k\Omega) = -14.1$$

$$w_1 = \frac{1}{(10^{-7}F)(243k\Omega + 5k\Omega)} = 40.3 \frac{rad}{s} \quad | \quad w_2 = \frac{1}{(10^{-7}F)(43k\Omega + 220k\Omega)} = 38.0 \frac{rad}{s}$$

$$w_3 = \frac{1}{(10^{-5}F)\left(13k\Omega \parallel \frac{1}{g_m}\right)} = \frac{1}{(10^{-5}F)(13k\Omega \parallel 2.5k\Omega)} = 47.7 \frac{rad}{s} \quad | \quad w_z = \frac{1}{(10^{-5}F)(13k\Omega)} = 7.69 \frac{rad}{s}$$

$$\text{Using Eq. (17.16)} : f_L \cong \frac{1}{2\pi} \sqrt{(40.3)^2 + (38.0)^2 + (47.7)^2 - 2(7.69)^2} = 11.5 \text{ Hz}$$

17.11

(a) Assume that ω_3 is dominant : $f_L \cong \omega_3 = 2p(50) = 314 \frac{rad}{s}$

$$C_3 = \frac{1}{\omega_3 \left(R_S \parallel \frac{1}{g_m} \right)} = \frac{1}{314 (13k\Omega \parallel 2.5k\Omega)} = 1.52 \text{ nF} \quad \text{where} \quad g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{0.4mA}{1V} = 0.4 \text{ mS}$$

(b) Choose $C_3 = 1.5 \text{ nF}$ | $\omega_3 = \frac{1}{1.5 \text{ nF} (13k\Omega \parallel 2.5k\Omega)} = 318 \frac{rad}{s}$ | $\omega_z = \frac{1}{(1.5 \text{ nF})(13k\Omega)} = 51.3 \frac{rad}{s}$

$$\omega_1 = \frac{1}{(10^{-7} F)(2.43M\Omega + 1k\Omega)} = 4.11 \frac{rad}{s} \quad | \quad \omega_2 = \frac{1}{(10^{-7} F)(43k\Omega + 1M\Omega)} = 9.59 \frac{rad}{s}$$

Using Eq. (17.16) yields : $f_L \cong \frac{1}{2p} \sqrt{(4.11)^2 + (9.59)^2 + (318)^2 - 2(51.3)^2} = 49.3 \text{ Hz}$

(c) Assume that ω_3 is dominant : $f_L \cong \omega_3 = 2p(50) = 314 \frac{rad}{s}$


$$C_3 = \frac{1}{\omega_3 \left(R_S \parallel \frac{1}{g_m} \right)} = \frac{1}{314 (13k\Omega \parallel 2.5k\Omega)} = 1.52 \text{ nF} \quad \text{where} \quad g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{0.4mA}{1V} = 0.4 \text{ mS}$$

Choose $C_3 = 1.5 \text{ nF}$ | $\omega_3 = \frac{1}{1.5 \text{ nF} (13k\Omega \parallel 2.5k\Omega)} = 318 \frac{rad}{s}$ | $\omega_z = \frac{1}{(1.5 \text{ nF})(13k\Omega)} = 51.3 \frac{rad}{s}$

$$\omega_1 = \frac{1}{(10^{-7} F)(243k\Omega + 5k\Omega)} = 40.3 \frac{rad}{s} \quad | \quad \omega_2 = \frac{1}{(10^{-7} F)(43k\Omega + 220k\Omega)} = 38.0 \frac{rad}{s}$$

Using Eq. (17.16) yields : $f_L \cong \frac{1}{2p} \sqrt{(40.3)^2 + (38.0)^2 + (318)^2 - 2(51.3)^2} = 50.1 \text{ Hz}$

17.12

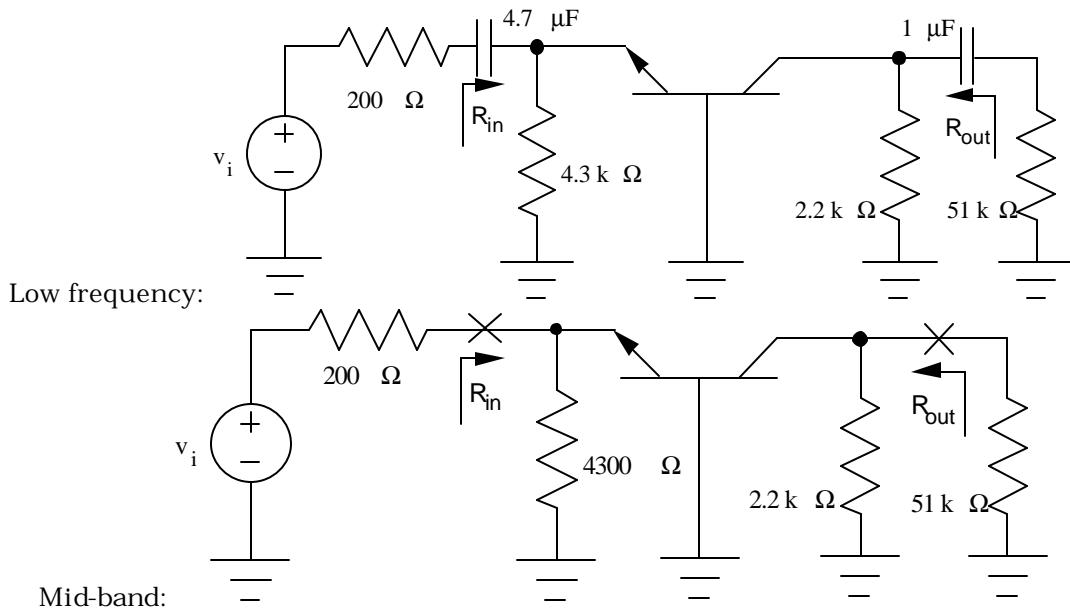

$$(b) A_v(s) = A_{mid} \frac{s^2}{(s + \mathbf{w}_1)(s + \mathbf{w}_2)} \quad | \quad \mathbf{w}_1 = \frac{1}{C_1 \left(R_S + R_E \parallel \frac{1}{g_m} \right)} \quad | \quad \mathbf{w}_2 = \frac{1}{C_2 (R_C + R_3)} \quad | \quad 2 \text{ zeros at } \mathbf{w} = 0$$

$$(c) A_{mid} = \left(\frac{R_{in}}{R_I + R_{in}} \right) A_{vt} = \left(\frac{R_{in}}{R_I + R_{in}} \right) g_m R_L = \left(\frac{R_{in}}{R_I + R_{in}} \right) g_m (R_{out} \parallel R_3) \quad | \quad g_m = 40(1mA) = 0.04S$$

$$R_{in} = R_E \parallel \frac{1}{g_m} = 24.9\Omega \quad | \quad R_L = R_{out} \parallel R_3 \quad | \quad R_{out} = R_C \parallel r_o = R_C = 2.2k\Omega$$

$$A_{mid} = \left(\frac{24.9\Omega}{200\Omega + 24.9\Omega} \right) (0.04) (2.2k\Omega \parallel 51k\Omega) = +9.34 \rightarrow 19.4 \text{ dB}$$

$$\mathbf{w}_1 = \frac{1}{4.7 \times 10^{-6} (200 + 24.9)} = 946 \frac{\text{rad}}{s} \quad | \quad \mathbf{w}_2 = \frac{1}{10^{-6} (2.2k\Omega + 51k\Omega)} = 18.8 \frac{\text{rad}}{s}$$

$$\mathbf{w}_1 \text{ is dominant} : f_L \cong \frac{\mathbf{w}_1}{2p} = 151 \text{ Hz}$$

$$(d) g_m = 40(10mA) = 0.0004S \quad | \quad R_{in} = 2.49k\Omega \quad | \quad R_{out} = R_C \parallel r_o = R_C = 220k\Omega$$

$$A_{mid} = \left(\frac{2.49k\Omega}{200\Omega + 2.49k\Omega} \right) (0.0004) (220k\Omega \parallel 510k\Omega) = +56.9 \rightarrow 35.1 \text{ dB}$$

$$\mathbf{w}_1 = \frac{1}{4.7 \times 10^{-6} (200 + 2.49k\Omega)} = 79.1 \frac{\text{rad}}{s} \quad | \quad \mathbf{w}_2 = \frac{1}{10^{-6} (220k\Omega + 510k\Omega)} = 1.37 \frac{\text{rad}}{s}$$

$$\mathbf{w}_1 \text{ is dominant} : f_L \cong \frac{\mathbf{w}_1}{2p} = 12.6 \text{ Hz}$$

17.13

$$(a) \text{ Assume } \mathbf{w}_1 \text{ is dominant} : \mathbf{w}_L \cong \mathbf{w}_1 = 2p(500\text{Hz}) = 3140 \frac{\text{rad}}{s}$$

$$C_1 = \frac{1}{\mathbf{w}_1 (R_I + R_{in})} \quad | \quad R_{in} = R_E \parallel \frac{1}{g_m} \quad | \quad g_m = 40(1mA) = 0.04S \quad | \quad R_{in} = 4300\Omega \parallel 25\Omega = 24.9\Omega$$

$$C_1 = \frac{1}{3.14 \times 10^3 (200 + 24.9)} = 1.42 \text{ nF}$$

$$(b) \text{ Choose } C_1 = 1.5 \text{ nF} \quad | \quad \mathbf{w}_1 = \frac{1}{1.5 \times 10^{-6} (200 + 24.9)} = 2960 \frac{\text{rad}}{s}$$

$$\mathbf{w}_2 = \frac{1}{10^{-6} (2.2k\Omega + 51k\Omega)} = 18.8 \frac{\text{rad}}{s} \quad | \quad \mathbf{w}_1 \text{ is dominant} : f_L \cong \frac{\mathbf{w}_1}{2p} = 472 \text{ Hz}$$

(c) Assume w_1 is dominant : $w_L \cong w_1 = 2p(500Hz) = 3140 \frac{rad}{s}$


$$C_1 = \frac{1}{w_1(R_I + R_{in})} \quad | \quad R_{in} = R_E \parallel \frac{1}{g_m} \quad | \quad g_m = 40(10mA) = 0.0004S \quad | \quad R_{in} = 430k\Omega \parallel 2500\Omega = 2.49k\Omega$$

$$C_1 = \frac{1}{3.14 \times 10^3 (200 + 2490)} = 0.118 \text{ } \mu F \quad | \quad \text{Choose } C_1 = 0.12 \text{ } \mu F$$

$$w_1 = \frac{1}{0.12 \times 10^{-6} (200 + 2490)} = 2100 \frac{rad}{s} \quad | \quad w_2 = \frac{1}{10^{-6} (2.2k\Omega + 51k\Omega)} = 18.8 \frac{rad}{s}$$

w_1 is dominant : $f_L \cong \frac{w_1}{2p} = 493 \text{ Hz}$

17.14

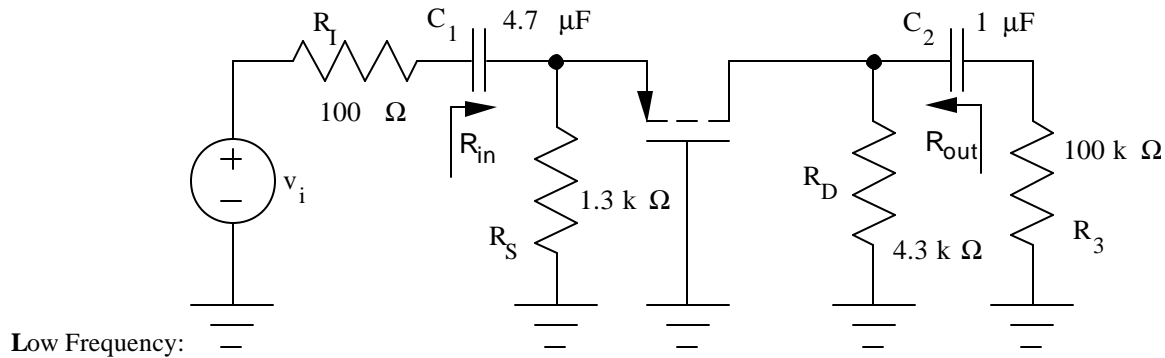

$$(b) A_v(s) = A_{mid} \frac{s^2}{(s + w_1)(s + w_2)} \quad | \quad w_1 = \frac{1}{C_1 \left(R_I + R_S \parallel \frac{1}{g_m} \right)} \quad | \quad w_2 = \frac{1}{C_2 (R_D + R_3)} \quad | \quad 2 \text{ zeros at } w = 0$$

$$(c) A_{mid} = \left(\frac{R_{in}}{R_I + R_{in}} \right) A_{vt} = \left(\frac{R_{in}}{R_I + R_{in}} \right) g_m R_L = \left(\frac{R_{in}}{R_I + R_{in}} \right) g_m (R_{out} \parallel R_3) \quad | \quad g_m = 5mS$$

$$R_{in} = R_S \parallel \frac{1}{g_m} = 173\Omega \quad | \quad R_L = R_{out} \parallel R_3 \quad | \quad R_{out} = R_D \parallel r_o = R_D = 4.3k\Omega \quad (\text{assuming } r_o = \infty)$$

$$A_{mid} = \left(\frac{173\Omega}{100\Omega + 173\Omega} \right) (0.005) (4.3k\Omega \parallel 100k\Omega) = +13.1 \rightarrow 22.3 \text{ dB}$$

$$w_1 = \frac{1}{4.7 \times 10^{-6} (100 + 173)} = 779 \frac{rad}{s} \quad | \quad w_2 = \frac{1}{10^{-6} (4.3k\Omega + 100k\Omega)} = 9.59 \frac{rad}{s}$$

w_1 is dominant : $f_L \cong \frac{w_1}{2p} = 124 \text{ Hz}$

17.15

(a) Assume \mathbf{w}_1 is dominant : $\mathbf{w}_L \cong \mathbf{w}_1 = 2\mathbf{p}(1000\text{Hz}) = 6280 \frac{\text{rad}}{\text{s}}$ | $C_1 = \frac{1}{\mathbf{w}_1(R_I + R_{in})}$

$$R_{in} = R_S \parallel \frac{1}{g_m} = 1300\Omega \parallel 200\Omega = 173\Omega \quad | \quad C_1 = \frac{1}{6.28 \times 10^3 (100 + 173)} = 0.583 \text{ nF}$$

(b) Choose $C_1 = 0.56 \text{ nF}$ | $\mathbf{w}_1 = \frac{1}{0.56 \times 10^{-6} (100 + 173)} = 6540 \frac{\text{rad}}{\text{s}}$

$$\mathbf{w}_2 = \frac{1}{10^{-6} (22\text{k}\Omega + 75\text{k}\Omega)} = 10.3 \frac{\text{rad}}{\text{s}} \quad | \quad \mathbf{w}_1 \text{ is dominant : } f_L \cong \frac{\mathbf{w}_1}{2\mathbf{p}} = 1040 \text{ Hz}$$

17.16

(a) $g_m = 40I_C = 40(0.175\text{mA}) = 7.00\text{mS}$ | $r_p = \frac{\mathbf{b}_o}{g_m} = \frac{100}{7.00\text{mS}} = 14.3\text{k}\Omega$ | $r_o = \infty$ (V_A not given)

$$R_{in} = R_1 \parallel R_2 \parallel r_p = 100\text{k}\Omega \parallel 300\text{k}\Omega \parallel 14.3\text{k}\Omega = 12.0\text{k}\Omega \quad | \quad R_L = R_C \parallel R_3 = 43\text{k}\Omega \parallel 100\text{k}\Omega = 30.1\text{k}\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{12.0\text{k}\Omega}{1\text{k}\Omega + 12.0\text{k}\Omega} (7.00\text{mS})(30.1\text{k}\Omega) = -194$$

SCTC : $R_{1S} = R_I + R_{in} = 1\text{k}\Omega + 12.0\text{k}\Omega = 13.0\text{k}\Omega$ | $R_{th} = R_1 \parallel R_2 \parallel R_I = 100\text{k}\Omega \parallel 300\text{k}\Omega \parallel 1\text{k}\Omega = 987\Omega$

$$R_{2S} = R_E \parallel \frac{R_{th} + r_p}{\mathbf{b}_o + 1} = 15\text{k}\Omega \parallel \frac{987\Omega + 14.3\text{k}\Omega}{101} = 150\Omega \quad | \quad R_{3S} = R_C + R_3 = 43\text{k}\Omega + 100\text{k}\Omega = 143\text{k}\Omega$$

$$f_L \cong \frac{1}{2\mathbf{p}} \left[\frac{1}{2 \times 10^{-6} (13.0\text{k}\Omega)} + \frac{1}{10 \times 10^{-6} (150\Omega)} + \frac{1}{1 \times 10^{-7} (143\text{k}\Omega)} \right] = \frac{(38.5 + 667 + 69.9)}{2\mathbf{p}} = 123 \text{ Hz}$$

(b) Note that the Q-point assumed in part (a) is not quite correct.

SPICE yields: (144 μA , 3.67 V), $A_{mid} = 43.9 \text{ dB}$, $f_L = 91 \text{ Hz}$

(c) $V_{EQ} = V_{CC} \frac{R_1}{R_1 + R_2} = 12 \frac{100\text{k}\Omega}{100\text{k}\Omega + 300\text{k}\Omega} = 3\text{V}$ | $R_{EQ} = R_1 \parallel R_2 = 100\text{k}\Omega \parallel 300\text{k}\Omega = 75.0\text{k}\Omega$

$$I_C = \mathbf{b}_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\mathbf{b}_F + 1)R_E} = 100 \frac{3 - 0.7}{75\text{k}\Omega + (101)15\text{k}\Omega} = 145 \mu\text{A}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 12 - (0.145\text{mA})(43\text{k}\Omega) - \frac{101}{100} (0.145\text{mA})(15\text{k}\Omega) = 3.57 \text{ V}$$

These values agree with the SPICE results listed above in part (b).

17.17

(a) Use the values from Section 17.3.1, and assume ω_3 is dominant.

$$\omega_L = 2\pi(1000\text{Hz}) = 6280 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_3 = \omega_L - \omega_1 - \omega_2 = 6280 - 225 + 96.1 = 5960 \frac{\text{rad}}{\text{s}}$$

$$C_3 = \frac{1}{\omega_3 R_{3s}} = \frac{1}{5960(22.7\Omega)} = 7.39 \text{ nF}$$


(b) Choose $C_3 = 6.8 \text{ nF}$ | $\omega_3 = \frac{1}{6.8 \times 10^{-6}(22.7\Omega)} = 6480 \frac{\text{rad}}{\text{s}}$

$$\omega_2 = 96.1 \frac{\text{rad}}{\text{s}} \quad | \quad \omega_1 = 225 \frac{\text{rad}}{\text{s}} \quad | \quad f_L \cong \frac{225 + 96.1 + 6480}{2\pi} = 1080 \text{ Hz}$$


or if ω_L must be no more than 1000 Hz, choose $C_3 = 8.2 \text{ nF}$

$$\omega_3 = \frac{1}{8.2 \times 10^{-6}(22.7\Omega)} = 5370 \frac{\text{rad}}{\text{s}} \quad | \quad f_L \cong \frac{225 + 96.1 + 5370}{2\pi} = 906 \text{ Hz}$$

17.18

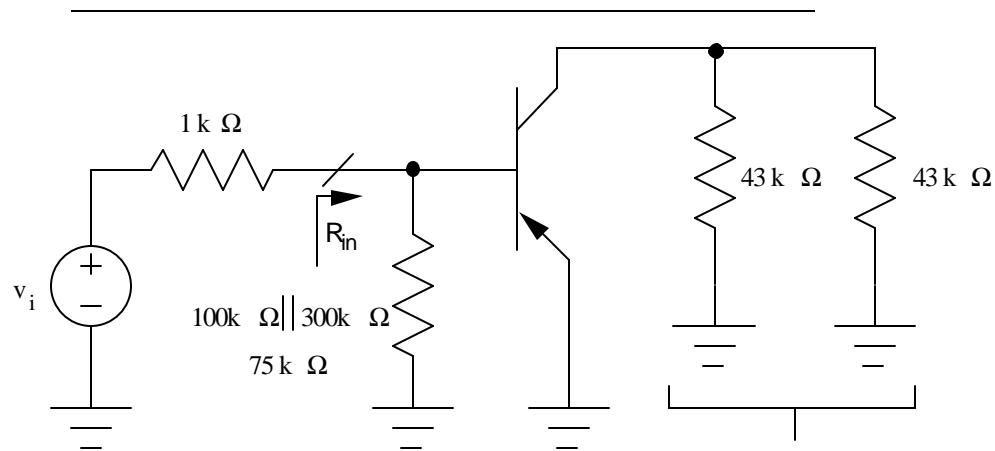

Mid-band:

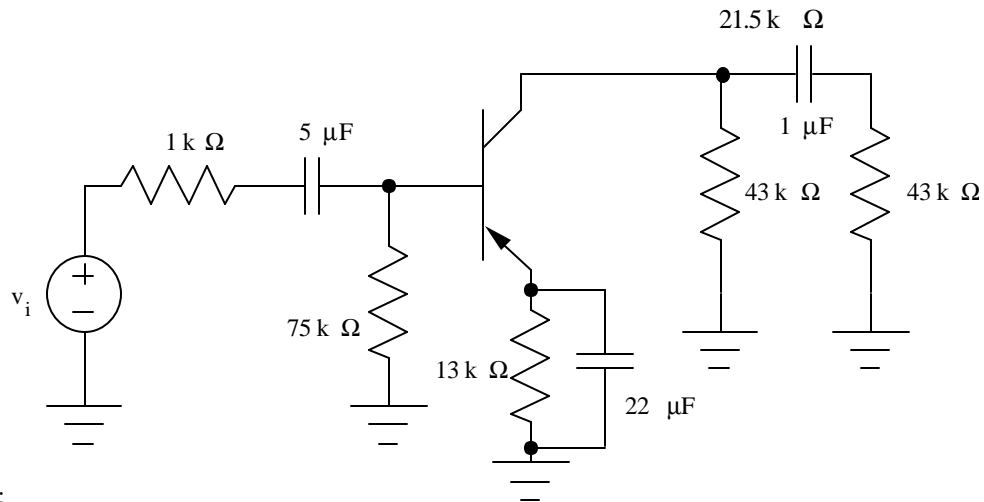

Low frequency:

$$(b) \ g_m = 40I_C = 40(0.164mA) = 6.56mS \mid r_p = \frac{b_o}{g_m} = \frac{100}{6.56mS} = 15.2k\Omega \mid r_o = \infty \text{ (V}_A \text{ not given)}$$

$$R_{in} = R_1 \parallel R_2 \parallel r_p = 100k\Omega \parallel 300k\Omega \parallel 15.2k\Omega = 12.6k\Omega \mid R_L = R_C \parallel R_3 = 43k\Omega \parallel 43k\Omega = 21.5k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{12.6k\Omega}{1k\Omega + 12.6k\Omega} (6.56mS)(21.5k\Omega) = -131$$

$$SCTC : R_{1S} = R_I + R_{in} = 1k\Omega + 12.6k\Omega = 13.6k\Omega \mid R_{th} = R_1 \parallel R_2 \parallel R_I = 100k\Omega \parallel 300k\Omega \parallel 1k\Omega = 987\Omega$$

$$R_{2S} = R_E \parallel \left[\frac{R_{th} + r_p}{b_o + 1} \right] = 13k\Omega \parallel \left[\frac{987\Omega + 15.2k\Omega}{101} \right] = 158\Omega \mid R_{3S} = R_C + R_3 = 43k\Omega + 43k\Omega = 86k\Omega$$

$$f_L \cong \frac{1}{2p} \left[\frac{1}{5 \times 10^{-6} (13.6k\Omega)} + \frac{1}{22 \times 10^{-6} (158\Omega)} + \frac{1}{1 \times 10^{-6} (86k\Omega)} \right] = \frac{(14.7 + 288 + 11.6)}{2p} = 50.0 \text{ Hz}$$

17.19 $R_S = 6.8 \text{ k}\Omega$

$$SCTC : R_{1S} = R_I + R_G = 1k\Omega + 1M\Omega = 1.00M\Omega \mid w_1 = \frac{1}{1.00M\Omega(0.1mF)} = 10.0 \frac{rad}{s}$$

$$R_{2S} = R_S \parallel \left[\frac{1}{g_m} \right] = 6.8k\Omega \parallel \left[\frac{1}{1.5mS} \right] = 607\Omega \mid w_2 = \frac{1}{607\Omega(10mF)} = 165 \frac{rad}{s}$$

$$R_{3S} = R_D + R_3 = 22k\Omega + 100k\Omega = 122k\Omega \mid w_3 = \frac{1}{122k\Omega(0.1mF)} = 82.0 \frac{rad}{s}$$

$$f_L \cong \frac{(10.0 + 165 + 82.0)}{2p} = 40.9 \text{ Hz}$$

17.20 $R_S = 10 \text{ k}\Omega$


$$SCTC : R_{1S} = R_I + R_G = 1k\Omega + 500k\Omega = 501k\Omega \mid w_1 = \frac{1}{501k\Omega(0.1mF)} = 20.0 \frac{rad}{s}$$

$$R_{2S} = R_S \parallel \left[\frac{1}{g_m} \right] = 10k\Omega \parallel \left[\frac{1}{0.75mS} \right] = 1.18k\Omega \mid w_2 = \frac{1}{1.18k\Omega(10mF)} = 84.8 \frac{rad}{s}$$


$$R_{3S} = R_D + R_3 = 43k\Omega + 100k\Omega = 143k\Omega \mid w_3 = \frac{1}{143k\Omega(0.1mF)} = 69.9 \frac{rad}{s}$$

$$f_L \cong \frac{(20.0 + 84.8 + 69.9)}{2p} = 27.8 \text{ Hz}$$

17.21

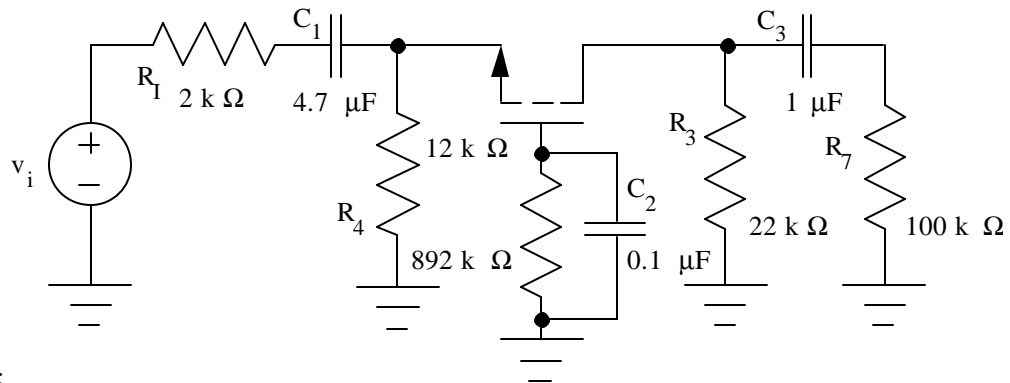

Low Frequency:

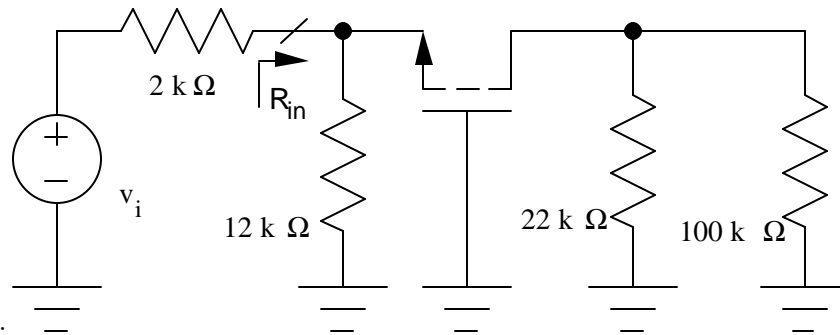

Mid-band:

$$g_m = \frac{2(0.1mA)}{1V} = 0.200mS \quad | \quad \frac{1}{g_m} = 5000\Omega$$


$$R_{in} = R_s \parallel \frac{1}{g_m} = 12k\Omega \parallel 5k\Omega = 3.53k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{3.53k\Omega}{2k\Omega + 3.53k\Omega} (0.200mS)(18k\Omega) = 2.30 \quad (7.24dB)$$


$$w_1 = \frac{1}{C_1(R_I + R_{in})} = \frac{1}{4.7 \times 10^{-6} (2k\Omega + 3.53k\Omega)} = 38.5 \frac{rad}{s} \quad | \quad w_2 = \text{doesn't matter since } i_g = 0!$$

$$w_3 = \frac{1}{C_3(R_3 + R_7)} = \frac{1}{10^{-7} (100k\Omega + 22k\Omega)} = 82.0 \frac{rad}{s} \quad | \quad f_L \cong \frac{1}{2p} (38.5 + 82.0) = 19.2Hz$$

17.22

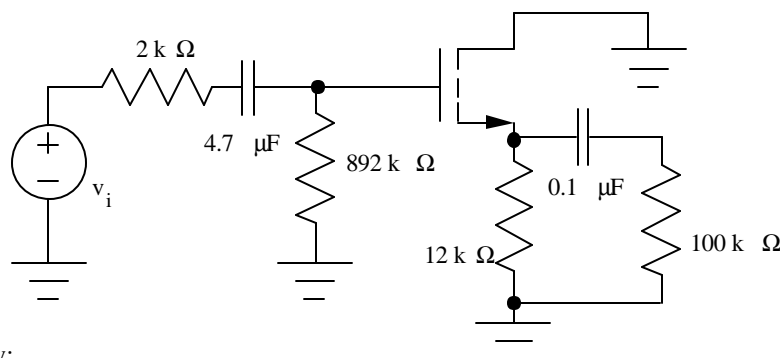

Low Frequency:

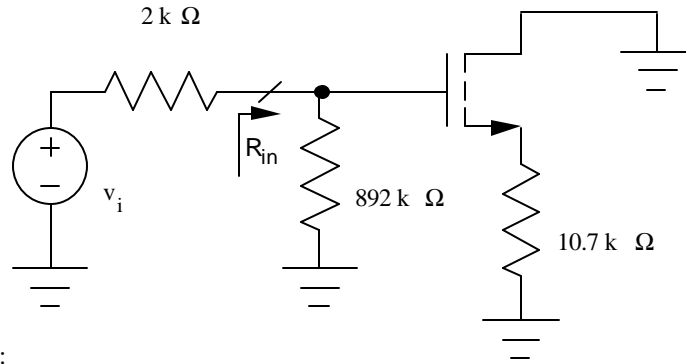

Mid-band:

$$g_m = \frac{2(0.1mA)}{0.75V} = 0.267mS \quad | \quad R_{in} = R_1 \parallel R_2 = 892k\Omega \quad | \quad R_L = 12k\Omega \parallel 100k\Omega = 10.7k\Omega$$


$$A_{mid} = \frac{R_{in}}{R_i + R_{in}} \frac{g_m R_L}{1 + g_m R_L} = 0.998 \frac{(0.267mS)(10.7k\Omega)}{1 + (0.267mS)(10.7k\Omega)} = +0.739 \quad (-2.62 \text{ dB})$$

$$w_1 = \frac{1}{C_1(R_i + R_{in})} = \frac{1}{4.7 \times 10^{-6}(2k\Omega + 892k\Omega)} = 0.238 \frac{rad}{s}$$


$$w_3 = \frac{1}{C_3 \left[R_7 + \left(R_S \parallel \frac{1}{g_m} \right) \right]} = \frac{1}{10^{-7} \left[100k\Omega + \left(12k\Omega \parallel \frac{1}{0.267mS} \right) \right]} = 97.2 \frac{rad}{s}$$

$$f_L \cong \frac{1}{2\pi} (0.238 + 97.2) = 15.5 \text{ Hz}$$

17.23

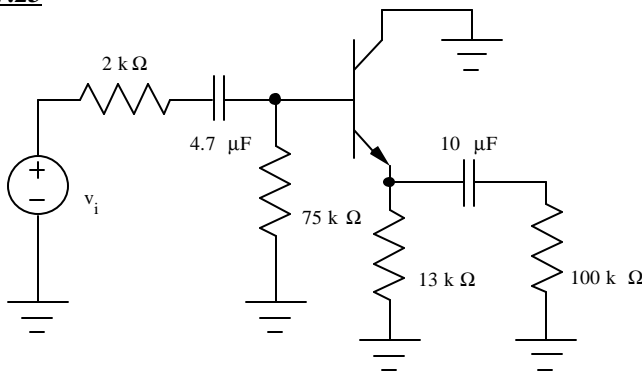

Low frequency

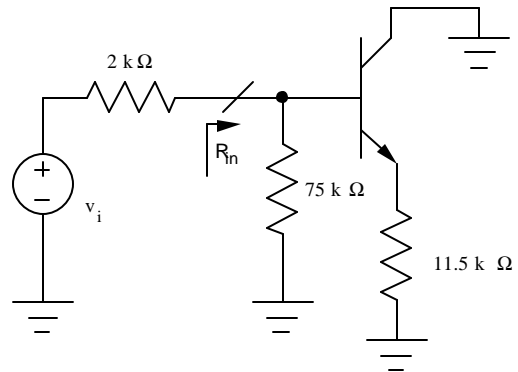

Mid-band

$$(b) R_{in} = R_1 \parallel R_2 \parallel r_p + (\mathbf{b}_o + 1)R_L \mid R_L = 13k\Omega \parallel 100k\Omega = 11.5k\Omega \mid r_p = \frac{100}{40(0.25mA)} = 10.0k\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel [r_p + (\mathbf{b}_o + 1)R_L] = 100k\Omega \parallel 300k\Omega \parallel [10.0k\Omega + (101)11.5k\Omega] = 70.5k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} \frac{(\mathbf{b}_o + 1)R_L}{R_{in}} = 0.972 \frac{101(11.5k\Omega)}{[2 + 10.0 + 101(11.5)]k\Omega} = 0.963 \mid R_B = R_1 \parallel R_2 = 75k\Omega$$

$$R_{is} = R_I + R_B \parallel [r_p + (\mathbf{b}_o + 1)R_L] = 2k\Omega + 75k\Omega \parallel [10.0k\Omega + (101)11.5k\Omega] = 72.5k\Omega$$

$$\mathbf{w}_1 = \frac{1}{(72.5k\Omega)4.7 \times 10^{-6}} = 2.94 \frac{rad}{s}$$

$$R_{3s} = R_7 + R_E \parallel \left[\frac{R_B \parallel R_I + r_p}{(\mathbf{b}_o + 1)} \right] = 100k\Omega + 13k\Omega \parallel \frac{1.95k\Omega + 10.0k\Omega}{101} = 100k\Omega$$

$$\mathbf{w}_3 = \frac{1}{10^{-5}(10^5)} = 1 \frac{rad}{s} \quad f_L \cong \frac{(2.94 + 1)}{2\mathbf{p}} = 0.627Hz$$

17.24

$$\text{SCTC requires : } \mathbf{w}_L \cong \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2\mathbf{p}(500) = 3140 \frac{rad}{s}$$

$$\mathbf{w}_1 = \frac{1}{(10^{-7}F)(2.43M\Omega + 1k\Omega)} = 4.11 \frac{rad}{s} \mid \mathbf{w}_2 = \frac{1}{(10^{-7}F)(43k\Omega + 1M\Omega)} = 9.59 \frac{rad}{s}$$

$$\mathbf{w}_1 + \mathbf{w}_2 \ll \mathbf{w}_L \mid \mathbf{w}_3 \text{ will be dominant} \rightarrow \mathbf{w}_3 \cong \mathbf{w}_L$$

$$\mathbf{w}_3 = \frac{1}{C_3 \left(R_S \parallel \frac{1}{g_m} \right)} \mid g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.2mA)}{1V} = 0.400mS \mid \frac{1}{g_m} = 2.50k\Omega$$

$$C_3 = \frac{1}{3140(13k\Omega \parallel 2.5k\Omega)} = 0.152 \text{ } \mu\mathbf{F} \rightarrow 0.15 \text{ } \mu\mathbf{F} \text{ from Appendix C}$$

17.25

SCTC requires : $w_L \cong \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2p(100) = 628 \frac{rad}{s}$

$$w_2 = \frac{1}{C_2(R_C + R_3)} = \frac{1}{(10^{-6}F)(2.2k\Omega + 51k\Omega)} = 18.8 \frac{rad}{s} \ll w_L \quad | \quad w_1 \text{ will be dominant} \rightarrow w_L \cong w_1$$

$$w_1 = \frac{1}{C_1 \left(R_I + R_E \parallel \frac{1}{g_m} \right)} \quad | \quad \frac{1}{g_m} = \frac{1}{40(10^{-3})} = 25\Omega$$

$$C_1 = \frac{1}{628(200\Omega + 4.3k\Omega \parallel 25\Omega)} = 7.08 \text{ } \mu F \rightarrow 6.8 \text{ } \mu F \text{ nearest value in Appendix C}$$

Note : We might want to choose 8.2 μF to insure that $f_L \leq 100 \text{ Hz}$.

(b) SCTC requires : $w_L \cong \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2p(100) = 628 \frac{rad}{s}$

$$w_2 = \frac{1}{(10^{-6}F)(220k\Omega + 510k\Omega)} = 1.37 \frac{rad}{s} \quad | \quad w_1 \text{ will be dominant} \rightarrow w_L \cong w_1$$

$$w_1 = \frac{1}{C_1 \left(R_I + R_E \parallel \frac{1}{g_m} \right)} \quad | \quad \frac{1}{g_m} = \frac{1}{40(10^{-5})} = 2.5k\Omega$$

$$C_1 = \frac{1}{628(200\Omega + 430k\Omega \parallel 2.5k\Omega)} = 0.592 \text{ } \mu F \rightarrow 0.56 \text{ } \mu F \text{ nearest value in Appendix C}$$

Note : We might want to use 0.68 μF to insure that $f_L \leq 100 \text{ Hz}$.

17.26

$$g_m = 40I_C = 40(0.164mA) = 6.56mS \quad | \quad r_p = \frac{b_o}{g_m} = \frac{100}{6.56mS} = 15.2k\Omega \quad | \quad r_o = \infty \text{ (} V_A \text{ not given)}$$

SCTC requires : $\sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2p(20) = 126 \frac{rad}{s}$

$$R_{1s} = R_I + (R_B \parallel r_p) = 1k\Omega + (75k\Omega \parallel 15.2k\Omega) = 13.6k\Omega \quad | \quad w_1 = \frac{1}{5 \times 10^{-6}(13.6k\Omega)} = 14.7$$

$$R_{3s} = R_C + R_3 = 43k\Omega + 43k\Omega = 86k\Omega \quad | \quad w_3 = \frac{1}{1 \times 10^{-6}(86k\Omega)} = 11.6$$

$$w_2 = 126 - 14.7 - 11.6 = 99.7 \frac{rad}{s} \quad | \quad R_{2s} = R_E \parallel \left(\frac{(R_B \parallel R_I) + r_p}{b_o + 1} \right) = 13k\Omega \parallel \frac{987\Omega + 15.2k\Omega}{101} = 158\Omega$$

$$C_2 \cong \frac{1}{99.7(158)} = 63.5 \text{ } \mu F \rightarrow 68 \text{ } \mu F \text{ from Appendix C}$$

17.27

$$\text{SCTC requires : } \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2\mathbf{p}(1) = 6.28 \frac{\text{rad}}{s}$$

$$\text{However, } R_{3s} = R_3 + R_7 = 22k\Omega + 100k\Omega = 122k\Omega$$

$$\mathbf{w}_3 = \frac{1}{1 \times 10^{-7}(122k\Omega)} = 82.0 \frac{\text{rad}}{s} > 6.28 \frac{\text{rad}}{s} \quad | \quad \text{The design goal cannot be met.}$$

It is not possible to force f_L below the limit set by C_3 .

17.28

$$\text{SCTC requires : } \mathbf{w}_L \cong \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2\mathbf{p}(10) = 62.8 \frac{\text{rad}}{s} \quad | \quad R_G = R_1 \parallel R_2 = 892k\Omega$$

$$\mathbf{w}_1 = \frac{1}{C_1(R_I + R_G)} = \frac{1}{4.7 \times 10^{-6}(2k\Omega + 892k\Omega)} = 0.238 \frac{\text{rad}}{s} \quad | \quad \mathbf{w}_L \gg \mathbf{w}_1 \rightarrow \mathbf{w}_3 \text{ is dominant}$$

$$\mathbf{w}_L \cong \mathbf{w}_3 = \frac{1}{C_3 \left[R_7 + \left(R_S \parallel \frac{1}{g_m} \right) \right]} \quad | \quad \frac{1}{g_m} = \frac{0.75V}{2(0.1mA)} = 3.75k\Omega$$

$$C_3 = \frac{1}{62.8[100k\Omega + (12k\Omega \parallel 3.75k\Omega)]} = 0.155 \frac{\text{rad}}{s} \rightarrow 0.15 \text{ } \mu\text{F} \text{ using Appendix C}$$

17.29

$$\text{SCTC requires : } \mathbf{w}_L \cong \sum_{i=1}^3 \frac{1}{R_{is}C_i} = 2\mathbf{p}(5) = 31.4 \frac{\text{rad}}{s}$$

$$R_L = 13k\Omega \parallel 100k\Omega = 11.5k\Omega \quad | \quad r_p = \frac{100}{40(0.25mA)} = 10.0k\Omega$$

$$R_{1s} = R_I + R_B \parallel [r_p + (b_o + 1)R_L] = 2k\Omega + 75k\Omega \parallel [10.0k\Omega + (101)11.5k\Omega] = 72.5k\Omega$$

$$\mathbf{w}_1 = \frac{1}{(72.5k\Omega)4.7 \times 10^{-6}} = 2.94 \frac{\text{rad}}{s} \quad | \quad \mathbf{w}_3 = 31.4 - 2.94 = 28.5 \frac{\text{rad}}{s}$$

$$R_{3s} = R_7 + R_E \parallel \left[\frac{(R_B \parallel R_I) + r_p}{(b_o + 1)} \right] = 100k\Omega + 13k\Omega \parallel \frac{1.95k\Omega + 10.0k\Omega}{101} = 100k\Omega$$

$$C_3 = \frac{1}{28.5(100k\Omega)} = 0.351 \text{ } \mu\text{F} \rightarrow 0.39 \text{ } \mu\text{F} \text{ using the values from Appendix C.}$$

17.30

$$f_T = \frac{1}{2p} \left(\frac{g_m}{C_p + C_m} \right) \mid C_p = \frac{g_m}{2pf_T} - C_m \mid g_m = 40I_C$$

I_C	f_T	C_π	C_μ	$1/2\pi f_T C_\mu$
10 μA	50 MHz	0.733 pF	0.5 pF	1.27 GHz
100 μA	300 MHz	0.75 pF	1.37 pF	465 MHz
50 μA	1 GHz	2.93 pF	0.25 pF	2.55 GHz
10 mA	6.12 GHz	10 pF	0.400 pF	1.59 GHz
1 μA	3.18 MHz	1 pF	1 pF	636 MHz
1.18 mA	5 GHz	1 pF	0.5 pF	1.27 GHz

17.31

$$C_p = g_m t_F \mid C_p = \frac{g_m}{\omega_T} - C_m \mid V_{CB} = 5 - 0.7 = 4.3V \mid C_m = \frac{C_{m0}}{\sqrt{1 + \frac{V_{CB}}{f_{jc}}}} = \frac{2pF}{\sqrt{1 + \frac{4.3V}{0.9V}}} = 0.832 pF$$

$$C_p = \frac{40(2 \times 10^{-3})}{2p(5 \times 10^8)} - 0.832 pF = 24.6 pF \mid t_F = \frac{C_p}{g_m} = \frac{24.6 \times 10^{-12}}{40(2 \times 10^{-3})} = 0.308 ns = 308 ps$$

17.32

$$f_T = \frac{1}{2p} \left(\frac{g_m}{C_{GS} + C_{GD}} \right) \mid g_m = \sqrt{2K_n I_D}$$

I_D	f_T	C_{GS}	C_{GD}
10 μA	11.3 MHz	1.5 pF	0.5 pF
250 μA	56.3 MHz	1.5 pF	0.5 pF
4.93 mA	250 MHz	1.5 pF	0.5 pF

17.33

$$(a) f_T = \frac{3}{2} \frac{m_n (V_{GS} - V_{TN})}{L^2} = \frac{3}{2} \frac{600(0.25V)}{(10^{-4})^2} \frac{cm^2}{V-s} = 22.5 GHz$$

$$(b) f_T = \frac{3}{2} \frac{m_h (V_{GS} - V_{TN})}{L^2} = \frac{3}{2} \frac{250(0.25V)}{(10^{-4})^2} \frac{cm^2}{V-s} = 9.38 GHz$$

$$(c) \text{ NMOS: } f_T = \frac{3}{2} \frac{m_n (V_{GS} - V_{TN})}{L^2} = \frac{3}{2} \frac{600(0.25V)}{(10^{-5})^2} \frac{cm^2}{V-s} = 2.25 THz$$

$$\text{ PMOS: } f_T = \frac{3}{2} \frac{m_h (V_{GS} - V_{TN})}{L^2} = \frac{3}{2} \frac{250(0.25V)}{(10^{-5})^2} \frac{cm^2}{V-s} = 938 GHz$$

17.34

$$(a) r_p = \frac{100(0.025V)}{1mA} = 2.5k\Omega \quad | \quad R_{in} = 7.5k\Omega \parallel (r_x + r_p) = 2.01k\Omega \quad | \quad R_L = 4.3k\Omega \parallel 100k\Omega = 4.12k\Omega$$

$$g_m = 40(10^{-3}) = 40mS \quad | \quad A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\left(\frac{2.01k\Omega}{1k\Omega + 2.01k\Omega}\right)(40mS)(4.12k\Omega) = -110$$

$$(b) R_{in} = 7.5k\Omega \parallel r_p = 1.88k\Omega \quad | \quad A_{mid} = -\left(\frac{1.88k\Omega}{1k\Omega + 1.88k\Omega}\right)(40mS)(4.12k\Omega) = -108$$

17.35

$$r_p = \frac{100(0.025V)}{0.1mA} = 25k\Omega \quad | \quad g_m = 40(0.1mA) = 4mS$$

$$R_{in} = R_E \parallel \frac{r_x + r_p}{b_o + 1} = 43k\Omega \parallel \frac{250\Omega + 25k\Omega}{101} = 249\Omega \quad | \quad R_L = 22k\Omega \parallel 75k\Omega = 17.0k\Omega$$

$$(a) A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{249\Omega}{100\Omega + 249\Omega} (4mS)(17.0k\Omega) = 48.5$$

$$(b) R_{in} = R_E \parallel \frac{r_p}{b_o + 1} = 43k\Omega \parallel \frac{25k\Omega}{101} = 248\Omega \quad | \quad A_{mid} = \frac{248\Omega}{100\Omega + 248\Omega} (4mS)(17.0k\Omega) = 48.5$$

17.36

$$r_p = \frac{100(0.025V)}{1mA} = 2.5k\Omega \quad | \quad g_m = 40(1mA) = 40mS \quad | \quad R_L = 3k\Omega \parallel 47k\Omega = 2.82k\Omega$$

$$R_{in} = R_B \parallel [r_x + r_p + (b_o + 1)R_L] = 100k\Omega \parallel [0.25k\Omega + 2.5k\Omega + (101)2.82k\Omega] = 74.2k\Omega$$

$$(a) A_{mid} = A_{mid} = \frac{R_{in}}{R_I + R_{in}} \left[\frac{(b_o + 1)R_L}{r_x + r_p + (b_o + 1)R_L} \right] = \frac{74.2k\Omega}{1k\Omega + 74.2k\Omega} \left[\frac{101(2820)}{250 + 2500 + 101(2820)} \right] = 0.977$$

$$(b) R_{in} = R_B \parallel [r_p + (b_o + 1)R_L] = 100k\Omega \parallel [2.5k\Omega + (101)2.82k\Omega] = 74.2k\Omega$$

$$A_{mid} = \frac{74.2k\Omega}{1k\Omega + 74.2k\Omega} \left[\frac{101(2820)}{250 + 2500 + 101(2820)} \right] = 0.977$$

17.37

$$(a) s^2 + 5100s + 500000 \quad | \quad s_1 \cong -\frac{5100}{1} = -5100 \quad | \quad s_2 \cong -\frac{5 \times 10^5}{5100} = -98.0$$

$$s = \frac{-5100 \pm \sqrt{5100^2 - 4(5 \times 10^5)}}{2} = \frac{-5100 \pm 4900}{2} \rightarrow -100, -5000 \quad | \quad 2\% \text{ error}$$

$$(b) 2s^2 + 700s + 30000 = 2(s^2 + 350s + 15000)$$

$$s_1 \cong -\frac{350}{1} = -350 \quad | \quad s_2 \cong -\frac{15000}{350} = -42.9$$

$$s = \frac{-350 \pm \sqrt{350^2 - 4(15000)}}{2} = \frac{-350 \pm 250}{2} \rightarrow -50, -300 \quad | \quad 14\% \text{ error}$$

$$(c) \quad 3s^2 + 3300s + 300000 \quad | \quad s_1 \cong -\frac{3300}{3} = -1100 \quad | \quad s_2 \cong -\frac{3 \times 10^5}{3300} = -90.9$$

$$s = \frac{-3300 \pm \sqrt{3300^2 - 4(3)(3 \times 10^5)}}{6} = \frac{-3300 \pm 2700}{6} \rightarrow -100, -1000 \quad | \quad 11\% \text{ error}$$

$$(d) \quad 0.5s^2 + 300s + 40000 = 0.5(s^2 + 600s + 80000)$$

$$s_1 \cong -\frac{600}{1} = -600 \quad | \quad s_2 \cong -\frac{80000}{600} = -133$$

$$s = \frac{-600 \pm \sqrt{600^2 - 4(80000)}}{2} = \frac{-600 \pm 200}{2} \rightarrow -200, -400 \quad | \quad 34\%, 50\% \text{ error}$$

17.38

$$s^3 + 1110s^2 + 111000s + 1000000$$

$$s_1 \cong -\frac{1110}{1} = -1110 \quad | \quad s_2 \cong -\frac{111000}{1110} = -100 \quad | \quad s_3 \cong -\frac{1000000}{111000} = -9.01$$

Factoring the polynomial : $s^3 + 1110s^2 + 111000s + 1000000 = (s+10)(s+100)(s+1000)$

$s = -1000, -100, -10 \quad | \quad 11\% \text{ error in } s_1, 10\% \text{ error in } s_3$

In MATLAB: `roots([1 1110 111000 1000000])`

17.39

$$f(s) = s^6 + 138s^5 + 4263s^4 + 4760s^3 + 235550s^2 + 94000s + 300000$$

$$f'(s) = 6s^5 + 690s^4 + 17052s^3 + 14280s^2 + 471100s + 94000$$

$$s^{i+1} = s^i - \frac{f(s^i)}{f'(s^i)} \quad | \quad \text{Using a spreadsheet, two real roots are found : } -46.7962, -91.8478$$


Using MATLAB: `roots([1 138 4263 4760 235550 94000 300000])`

`ans = -91.8478, -46.7962, 0.5189 + 7.2789i, 0.5189 - 7.2789i, -0.1970 + 1.1278i, -0.1970 - 1.1278i`

A better polynomial : $f(s) = s^6 + 142s^5 + 4757s^4 + 58230s^3 + 256950s^2 + 398000s + 300000$

Roots: -100, -20, -15, -5, -1+i, -1-i

17.40

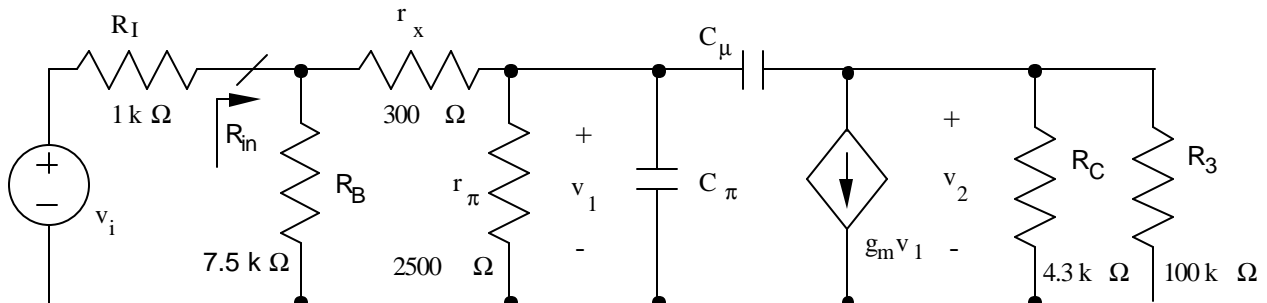

$$(a) r_p = \frac{100(0.025)}{0.001} = 2500\Omega \quad | \quad C_m = 0.75 \text{ pF} \quad | \quad C_p = \frac{40(10^{-3})}{2p(5 \times 10^8)} - 0.75 \text{ pF} = 12.0 \text{ pF}$$

$$R_{in} = 7.5k\Omega \parallel (r_x + r_p) = 2.03k\Omega \quad | \quad R_L = 4.3k\Omega \parallel 100k\Omega = 4.12k\Omega$$


$$g_m = 40(10^{-3}) = 40 \text{ mS} \quad | \quad A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\left(\frac{2.03k\Omega}{1k\Omega + 2.03k\Omega}\right)(40 \text{ mS})(4.12k\Omega) = -110$$

$$w_H = \frac{1}{r_{po} C_T} \quad | \quad r_{po} = r_p \parallel [r_x + (R_B \parallel R_I)] = 2500 \parallel [300 + (7500 \parallel 1000)] = 803 \Omega$$

$$C_T = 12.0 + 0.75 \left[1 + 40(10^{-3})(4120) + \frac{4120}{803} \right] = 140 \text{ pF} \quad | \quad f_H = \frac{1}{2p(803)(1.4 \times 10^{-10})} = 1.42 \text{ MHz}$$

$$(b) GBW = 110(1.42 \text{ MHz}) = 142 \text{ MHz} \quad | \quad GBW \leq \frac{1}{2p} \left(\frac{1}{r_x C_m} \right) = \frac{1}{2p(300\Omega)(0.75 \text{ pF})} = 707 \text{ MHz}$$

17.41

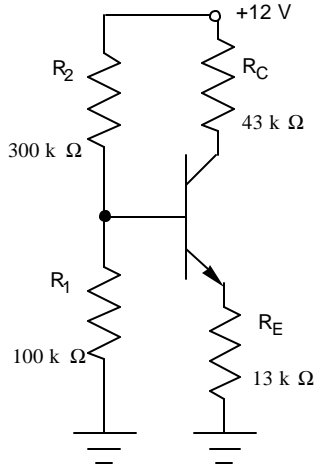


$$V_{EQ} = 12V \frac{100k\Omega}{100k\Omega + 300k\Omega} = 3V \quad | \quad R_{EQ} = 100k\Omega \parallel 300k\Omega = 75k\Omega$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_E} = 100 \frac{(3 - 0.7)V}{75k\Omega + (101)13k\Omega} = 166 \text{ }\mu\text{A}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 12 - (166\mu\text{A}) \left(43k\Omega + \frac{101}{100} 13k\Omega \right) = 2.68 \text{ V}$$

Q - Point : (166 μA , 2.68 V)

(b)

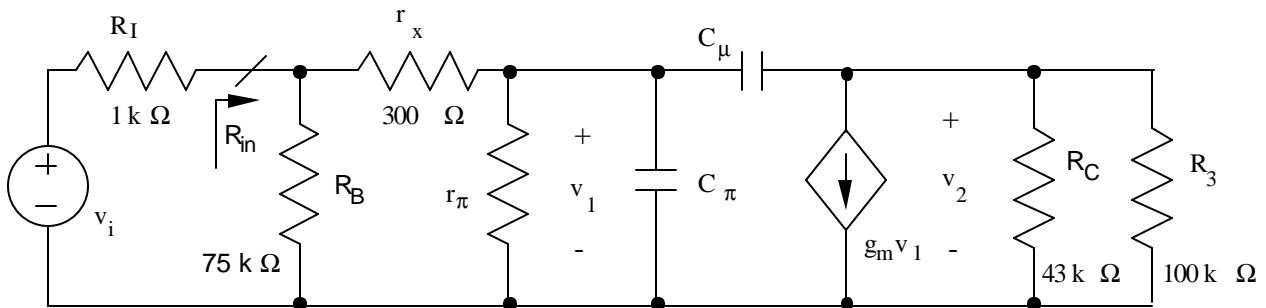

Note: As designers, we are free to change the amplifier design, but we typically cannot change the characteristics of the source and load resistances.

$$r_p = \frac{100(0.025)}{0.166mA} = 15.1k\Omega \quad | \quad C_m = 0.75 pF \quad | \quad C_p = \frac{40(0.166 \times 10^{-3})}{2p(5 \times 10^8)} - 0.75 pF = 1.36 pF$$

$$R_{in} = 75k\Omega \parallel (r_x + r_p) = 12.8k\Omega \quad | \quad R_L = 43k\Omega \parallel 100k\Omega = 30.1k\Omega$$


$$g_m = 40(0.166 \times 10^{-3}) = 6.64mS \quad | \quad A_{mid} = -\frac{R_{in}}{R_L + R_{in}} g_m R_L = -\left(\frac{12.8k\Omega}{1k\Omega + 12.8k\Omega}\right)(6.64mS)(30.1k\Omega) = -185$$

$$w_H = \frac{1}{r_{po} C_T} \quad | \quad r_{po} = r_p \parallel [r_x + (R_B \parallel R_L)] = 15.1k\Omega \parallel [300 + (75k\Omega \parallel 1k\Omega)] = 1.19k\Omega$$

$$C_T = 1.36 + 0.75 \left[1 + (6.64mS)(30.1k\Omega) + \frac{30.1k\Omega}{1.19k\Omega} \right] = 171pF \quad | \quad f_H = \frac{1}{2p(1190)(1.71 \times 10^{-10})} = 0.782 MHz$$

$$(c) GBW = 185(0.782MHz) = 145 MHz \quad | \quad GBW \leq \frac{1}{2p} \left(\frac{1}{r_x C_m} \right) = \frac{1}{2p(300\Omega)(0.75pF)} = 707 MHz$$

17.42 (a)

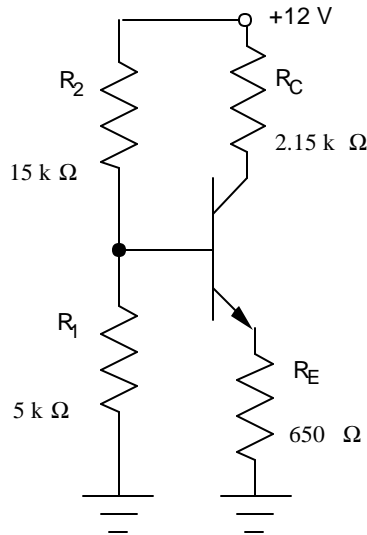


$$V_{EQ} = 12V \frac{5k\Omega}{5k\Omega + 15k\Omega} = 3V \quad | \quad R_{EQ} = 5k\Omega \parallel 15k\Omega = 3.75k\Omega$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{EQ} - V_{BE}}{R_{EQ} + (\beta_F + 1)R_E} = 100 \frac{(3 - 0.7)V}{3.75k\Omega + (101)(0.65k\Omega)} = 3.31 mA$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 12 - (3.31mA) \left(2.15k\Omega + \frac{101}{100} 0.65k\Omega \right) = 2.71 V \quad | \quad Q\text{-Point} : (3.31 mA, 2.71 V)$$

(b)

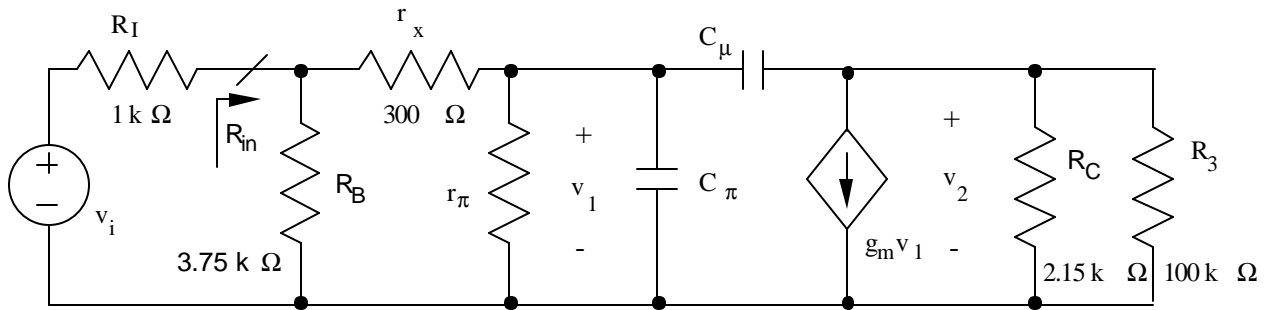

Note: As designers, we are free to change the amplifier design, but we typically cannot change the characteristics of the source and load resistances.

$$r_p = \frac{100(0.025)}{3.31 \text{ mA}} = 755 \Omega \quad | \quad C_m = 0.75 \text{ pF} \quad | \quad C_p = \frac{40(3.31 \times 10^{-3})}{2p(5 \times 10^8)} - 0.75 \text{ pF} = 41.4 \text{ pF}$$

$$R_{in} = 3.75 \text{ k}\Omega \parallel (r_x + r_p) = 823 \Omega \quad | \quad R_L = 2.15 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 2.11 \text{ k}\Omega$$

$$g_m = 40(3.31 \times 10^{-3}) = 132 \text{ mS} \quad | \quad A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\left(\frac{823 \Omega}{1000 \Omega + 823 \Omega}\right)(132 \text{ mS})(2.11 \text{ k}\Omega) = -126$$

$$w_H = \frac{1}{r_{po} C_T} \quad | \quad r_{po} = r_p \parallel [r_x + (R_B \parallel R_I)] = 755 \Omega \parallel [300 + (3.75 \text{ k}\Omega \parallel 1 \text{ k}\Omega)] = 260 \Omega$$

$$C_T = 41.4 + 0.75 \left[1 + (132 \text{ mS})(2.11 \text{ k}\Omega) + \frac{2.11 \text{ k}\Omega}{0.260 \text{ k}\Omega} \right] = 312 \text{ pF} \quad | \quad f_H = \frac{1}{2p(260 \Omega)(3.12 \times 10^{-10} \text{ F})} = 1.96 \text{ MHz}$$

$$(c) \text{ GBW} = 126(1.96 \text{ MHz}) = 247 \text{ MHz} \quad | \quad \text{GBW} \leq \frac{1}{2p} \left(\frac{1}{r_x C_m} \right) = \frac{1}{2p(300 \Omega)(0.75 \text{ pF})} = 707 \text{ MHz}$$

17.43

$$R_{in} = R_1 \parallel R_2 = 4.3 \text{ M}\Omega \parallel 5.6 \text{ M}\Omega = 2.43 \text{ M}\Omega \quad | \quad R_L = 43 \text{ k}\Omega \parallel 1 \text{ M}\Omega = 41.2 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.2 \text{ mA})}{1} = 0.400 \text{ mS} \quad |$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\frac{2.43 \text{ M}\Omega}{1 \text{ k}\Omega + 2.43 \text{ M}\Omega} 0.400 \text{ mS}(41.2 \text{ k}\Omega) = -16.5$$

$$f_H = \frac{1}{2p r_{po} C_T} \quad | \quad r_{po} = R_1 \parallel R_2 \parallel R_I = 1.00 \text{ k}\Omega$$

$$C_T = 2.5 \text{ pF} + 2.5 \text{ pF} \left[1 + (0.400 \text{ mS})(41.2 \text{ k}\Omega) + \frac{41.2 \text{ k}\Omega}{1 \text{ k}\Omega} \right] = 149 \text{ pF}$$

$$f_H = \frac{1}{2p(1 \text{ k}\Omega)(1.49 \times 10^{-10} \text{ F})} = 1.07 \text{ MHz}$$

17.44

*Problem 17.44 - Common-Source Amplifier

VDD 7 0 DC 0

VS 1 0 AC 1

RS 1 2 1K

C1 2 3 0.1UF

R1 3 0 4.3MEG

R2 3 7 5.6MEG

RD 7 5 43K

R4 4 0 13K

C3 4 0 10UF

C2 5 6 0.1UF

R3 6 0 1MEG

*Small-Signal FET Model

GM 5 4 3 4 0.4MS

CGS 3 4 2.5PF

CGD 3 5 2.5PF


*

.AC DEC 20 1 10MEG

.PRINT AC VM(6)

.PROBE

.END

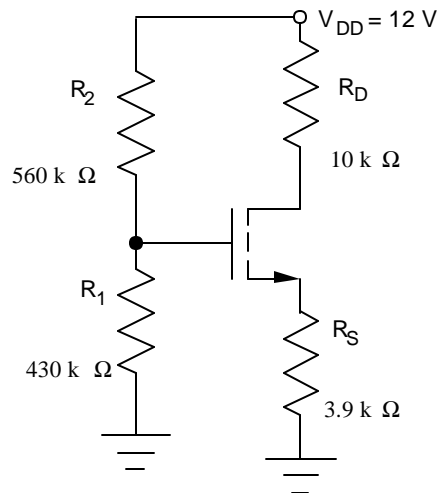Results: $A_{mid} = -16.5$, $f_L = 7.9$ Hz, $f_H = 1.06$ MHz**17.45** (a) Use $V_{DD} = 12$ V and $R_D = 10$ k Ω .

$$V_{EQ} = 12V \frac{430k\Omega}{430k\Omega + 560k\Omega} = 5.21V \quad | \quad R_{EQ} = 430k\Omega || 560k\Omega = 243k\Omega$$


$$\text{Assume active region operation : } I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \quad | \quad V_{EQ} = V_{GS} + I_D R_S$$

$$5.21 = V_{GS} + 3.9k\Omega \left(\frac{0.5mA}{2} \right) (V_{GS} - 1)^2 \rightarrow V_{GS} = 2.629V \text{ and } I_D = 663\mu A$$

$$V_{DS} = V_{DD} - I_D R_D - I_S R_S = 12 - (663\mu A)(13k\Omega + 3.9k\Omega) = 0.795 V$$

The transistor is not in pinch off! Reduce R_D to 10 k Ω .
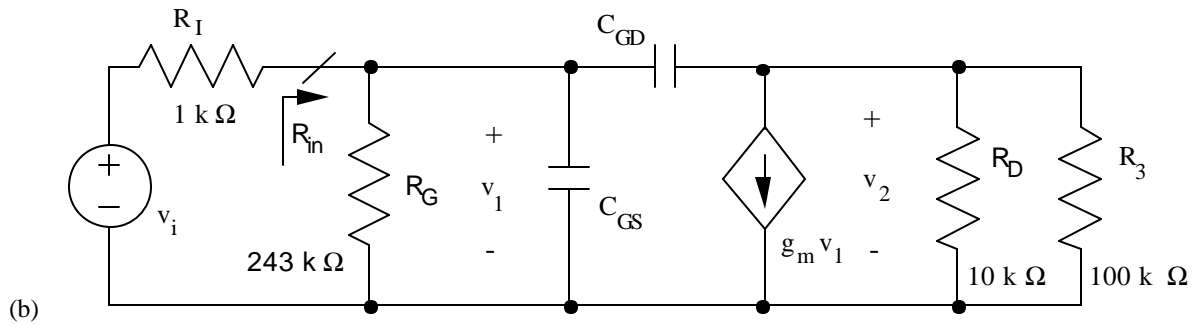
$$V_{DS} = V_{DD} - I_D R_D - I_S R_S = 12 - (663\mu A)(10k\Omega + 3.9k\Omega) = 2.78 V \text{ - Active region is correct.}$$



$$R_{in} = R_1 \parallel R_2 = 430k\Omega \parallel 560k\Omega = 243k\Omega \quad | \quad R_L = 10k\Omega \parallel 100k\Omega = 9.09k\Omega$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.663mA)}{1} = 1.33mS$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\frac{243k\Omega}{1k\Omega + 243k\Omega} (1.33mS)(9.09k\Omega) = -12.0$$


$$f_H = \frac{1}{2\pi r_{po} C_T} \quad | \quad r_{po} = R_1 \parallel R_2 \parallel R_I = 243k\Omega \parallel 1k\Omega = 0.996k\Omega$$

$$C_T = 2.5pF + 2.5pF \left[1 + (1.33mS)(9.09k\Omega) + \frac{9.09k\Omega}{0.996k\Omega} \right] = 58.1pF$$

$$f_H = \frac{1}{2\pi (0.996k\Omega)(58.1 \times 10^{-11}F)} = 2.75 MHz$$

$$(c) GBW = 12.0(2.75 MHz) = 33 MHz$$

17.46

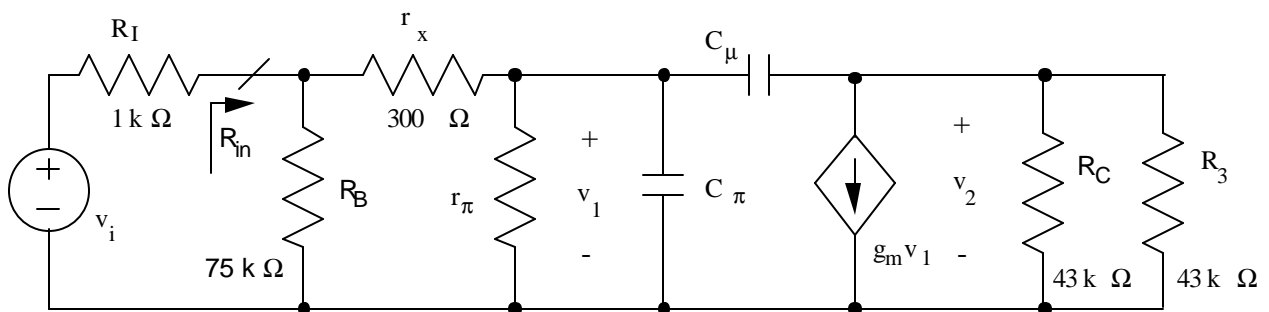

$$g_m = 40I_C = 40(0.164mA) = 6.56mS \quad | \quad r_p = \frac{b_o}{g_m} = \frac{100}{6.56mS} = 15.2k\Omega \quad | \quad r_o = \infty \quad (V_A \text{ not given})$$

$$R_{in} = R_1 \parallel R_2 \parallel r_p = 100k\Omega \parallel 300k\Omega \parallel 15.2k\Omega = 12.6k\Omega \quad | \quad R_L = R_C \parallel R_3 = 43k\Omega \parallel 43k\Omega = 21.5k\Omega$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\frac{12.6k\Omega}{1k\Omega + 12.6k\Omega} (6.56mS)(21.5k\Omega) = -131$$

$$C_p = \frac{g_m}{w_T} - C_m = \frac{6.56mS}{2p(5 \times 10^8 Hz)} - 0.75 = 1.34 pF$$

$$w_H = \frac{1}{r_{po} C_T} \quad | \quad r_{po} = r_p \parallel (r_x + R_1 \parallel R_2 \parallel R_l) = 15.2 k\Omega \parallel (300 + 987) = 1.19 k\Omega$$

$$C_T = C_p + C_m \left(1 + g_m R_L + \frac{R_L}{r_{po}} \right) = 1.34 pF + 0.75 pF \left[1 + 6.56mS(21.5k\Omega) + \frac{21.5k\Omega}{1.19k\Omega} \right] = 121 pF$$

$$f_H \cong \frac{1}{2p(1.19k\Omega)(1.21 \times 10^{-10} F)} = 1.10 MHz$$

17.47

*Problem 17.47 - Common-Emitter Amplifier

VCC 7 0 DC 0

VS 1 0 AC 1

RS 1 2 1K

C1 2 3 5UF

R1 3 0 300K

R2 3 7 100K

RC 5 0 43K

R4 7 4 13K

C2 7 4 22UF

C3 5 6 1UF

R3 6 0 43K

*Small-signal Model for the BJT

GM 5 4 8 4 6.56MS

RX 3 8 0.3K

RPI 8 4 15.24K

CPI 8 4 1.34PF

CU 8 5 0.75PF

*

.AC DEC 100 1 10MEG

.PRINT AC VM(6)

.PROBE

.END

Results: $A_{mid} = -128$, $f_L = 47 Hz$, $f_H = 1.10 MHz$

17.48

(a) See Eqs. (17.74 - 17.83).

$$\begin{bmatrix} I_s(s) \\ 0 \end{bmatrix} = \begin{bmatrix} s(C_p + C_m) + g_{p0} & -sC_m \\ -(sC_m - g_m) & s(C_m + C_L) + g_L \end{bmatrix} \begin{bmatrix} V_1(s) \\ V_2(s) \end{bmatrix}$$

$$\Delta = s^2 [C_p (C_m + C_L) + C_m C_L] + s [C_p g_L + C_m (g_m + g_{p0} + g_L) + C_L g_{p0}] + g_L g_{p0}$$

$$(b) w_{p1} \cong \frac{g_L g_{p0}}{C_p g_L + C_m (g_m + g_{p0} + g_L) + C_L g_{p0}} = \frac{1}{r_{p0} \left[C_p + C_m (1 + g_m R_L) + (C_m + C_L) \frac{R_L}{r_{p0}} \right]}$$

$$w_{p2} \cong \frac{C_p g_L + C_m (g_m + g_{p0} + g_L) + C_L g_{p0}}{C_p (C_m + C_L) + C_m C_L} = \frac{g_m}{C_p \left(1 + \frac{C_L}{C_m} \right) + C_L}$$

(c) The three capacitors form a loop and there are only two independent voltage among the three capacitors.

17.49

$$C_T = C_p + C_m (1 + g_m R_L) = 20 \text{ pF} + 0.5 \text{ pF} [1 + 40(1 \text{ mA})(1 \text{ k}\Omega)] = 40.5 \text{ pF}$$

$$f_T = \frac{1}{2p} \left(\frac{g_m}{C_p + C_m} \right) = \frac{1}{2p} \left[\frac{40(1 \text{ mA})}{20 \text{ pF} + 0.5 \text{ pF}} \right] = 311 \text{ MHz}$$

17.50 Using Eq. (17.98),

$$A_v(s) = \frac{\left(\frac{1}{RC} \right) \frac{A(s)}{1 + A(s)}}{s + \frac{1}{RC [1 + A(s)]}} \quad | \quad A(s) = \frac{10A_o}{s + 10} \quad | \quad A_v(s) = \left(\frac{1}{RC} \right) \frac{1 + \frac{10A_o}{s + 10}}{s + \frac{1}{RC \left(1 + \frac{10A_o}{s + 10} \right)}}$$

$$A_v(s) = \left(\frac{1}{RC} \right) \frac{10A_o}{s^2 + s(1 + A_o)10 + \frac{s + 10}{RC}} = \frac{\left(\frac{10A_o}{RC} \right)}{s^2 + s \left[\frac{1}{RC} + 10(1 + A_o) \right] + \frac{10}{RC}}$$

$$(a) A_v(s) = \frac{\left(\frac{10^6}{RC} \right)}{s^2 + s \left[\frac{1}{RC} + 10^6 \right] + \frac{10}{RC}} \cong \frac{\left(\frac{10^6}{RC} \right)}{(s + 10^6) \left(s + \frac{1}{10^5 RC} \right)}; w_L = \frac{1}{10^5 RC}$$

$$(b) A_v(s) = \frac{\left(\frac{10^7}{RC} \right)}{s^2 + s \left[\frac{1}{RC} + 10^7 \right] + \frac{10}{RC}} \cong \frac{\left(\frac{10^6}{RC} \right)}{(s + 10^7) \left(s + \frac{1}{10^6 RC} \right)}; w_L = \frac{1}{10^6 RC}$$

$$(c) \lim_{A_o \rightarrow \infty} A_v(s) = \frac{\left(\frac{10A_o}{RC} \right)}{10A_o s} = \frac{1}{sRC}$$

17.51


$$(a) Y_{in} = \frac{1+A}{Z(s)} = \frac{1+A}{\frac{1}{sC}} = sC(1+A) \quad | \quad C_{in} = C(1+A) = 10^{-10} F (1+10^5) = 10 \text{ } \mu F$$

$$(b) Z_{in} = \frac{1}{Y_{in}} = \frac{Z(s)}{1+A(s)} = \frac{10^5}{1 + \frac{10^6}{s+10}} = 10^5 \frac{s+10}{s+10+10^6} \cong 10^5 \frac{s+10}{s+10^6}$$

$$\text{Using MATLAB : } Z_{in}(j2000 \text{ } \mu F) = (4.95 + j6.28) \Omega$$

$$Z_{in}(j10^5 \text{ } \mu F) = (8.98 + j28.6) \text{ } k\Omega \quad | \quad Z_{in}(j2 \text{ } \mu F) = (97.5 + j15.5) \text{ } k\Omega$$

17.52

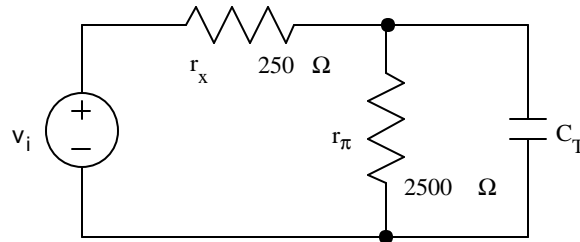

$$r_{po} = 2500 \Omega || 250 \Omega = 227 \Omega \quad | \quad C_T = 15 + 1 \left[1 + 0.04(2500) + \frac{2500}{227} \right] = 127 \text{ } pF$$

$$(a) \text{ At 1 kHz, } Z_C = \frac{1}{j(2 \text{ } \mu F)(10^3)(127 \text{ } pF)} = -j(1.25 \times 10^6)$$

$$\text{Using MATLAB : } Z = 250 + \frac{2500 Z_C}{2500 + Z_C} = (2750 - j4.99) \Omega \quad | \quad \text{SPICE : } (2750 - j4.56) \Omega$$

$$(b) \text{ At 50 kHz, } Z_C = \frac{1}{j(2 \text{ } \mu F)(5 \times 10^4)(127 \text{ } pF)} = -j2.51 \times 10^4 \Omega$$

$$\text{Using MATLAB : } Z = 250 + \frac{2500 Z_C}{2500 + Z_C} = (2730 - j247) \Omega \quad | \quad \text{SPICE : } (2730 - j226) \Omega$$

$$(c) \text{ At 1 MHz, } Z_C = \frac{1}{j(2 \text{ } \mu F)(10^6)(127 \text{ } pF)} = -j(12.53)$$

$$\text{Using MATLAB : } Z = 250 + \frac{2500 Z_C}{2500 + Z_C} = (752 - j1000) \Omega \quad | \quad \text{SPICE : } (836 - j1040) \Omega$$

(d) *Problem 17.52 - Common-Emitter Amplifier

```
IS 0 1 AC 1
RX 1 2 0.25K
RPI 2 0 2.5K
CPI 2 0 15PF
CU 2 3 1PF
GM 3 0 2 0 40MS
```

```

RL 3 0 2.5K
.AC LIN 1 1KHZ 1KHZ
*.AC LIN 1 50KHZ 50KHZ
*.AC LIN 1 1MEG 1MEG
.PRINT AC VR(1) VI(1) VM(1) VP(1)
.END

```

Note that the C_T approximation does not provide as good an estimate of Z_{in} at high frequencies (note the discrepancy at 1 MHz).

17.53

$$(a) g_m = 40 I_C = 40(1mA) = 40.0mS \quad | \quad r_p = \frac{b_o V_T}{I_C} = \frac{100(0.025)}{1mA} = 2.5k\Omega \quad | \quad r_o = \infty \quad (V_A \text{ not given})$$

$$r_{po} = r_p \parallel [r_x + (R_B \parallel R_I)] = 2.5k\Omega \parallel (250 + (7.5k\Omega \parallel 1k\Omega)) = 779\Omega \quad | \quad R_L = R_C \parallel R_3 = 4.3k\Omega \parallel 100k\Omega = 4.12k\Omega$$

$$C_p = \frac{g_m}{\omega_T} - C_m = \frac{40.0mS}{2\pi(5 \times 10^8 \text{ Hz})} - 0.75pF = 12.0pF \quad | \quad f_H \cong \frac{1}{2\pi r_{po} C_T}$$

$$C_T = C_p + C_m \left(1 + g_m R_L + \frac{R_L}{r_{po}} \right) = 12.0pF + 0.75pF \left[1 + 40.0mS(4.12k\Omega) + \frac{4.12k\Omega}{0.779k\Omega} \right] = 140pF$$


$$f_H \cong \frac{1}{2\pi(779\Omega)(1.40 \times 10^{-10} F)} = 1.46 \text{ MHz}$$

$$(b) r_{po} = r_p \parallel [r_x + (R_B \parallel R_I)] = 2.5k\Omega \parallel (0 + (7.5k\Omega \parallel 1k\Omega)) = 652\Omega$$

$$C_T = 12.0pF + 0.75pF \left[1 + 40.0mS(4.12k\Omega) + \frac{4.12k\Omega}{0.652k\Omega} \right] = 141pF$$

$$f_H \cong \frac{1}{2\pi(652\Omega)(1.41 \times 10^{-10} F)} = 1.73 \text{ MHz}$$

17.54

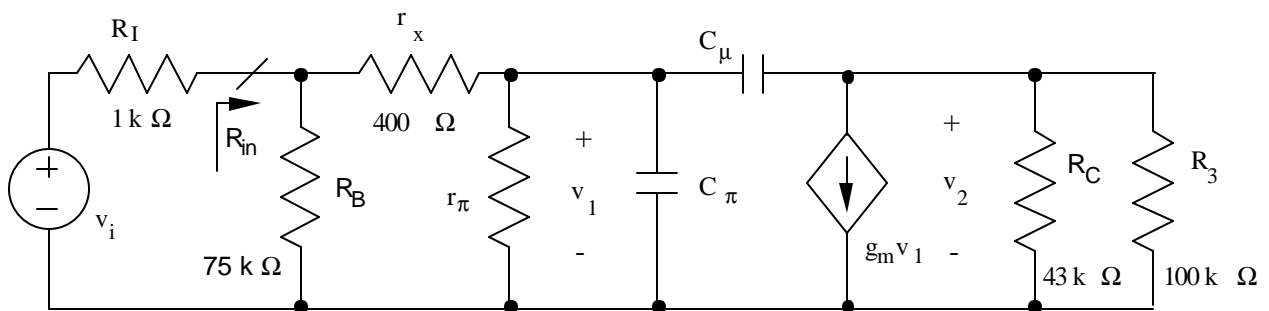

$$(a) g_m = 40 I_C = 40(0.1mA) = 4.00 mS \quad | \quad r_p = \frac{b_o V_T}{I_C} = \frac{100(0.025)}{0.1mA} = 25 k\Omega \quad | \quad r_o = \infty \quad (V_A \text{ not given})$$

$$r_{po} = r_p \parallel [r_x + (R_B \parallel R_1)] = 25 k\Omega \parallel (400 + (75 k\Omega \parallel 1 k\Omega)) = 1.31 k\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel (r_x + r_p) = 100 k\Omega \parallel 300 k\Omega \parallel 25.4 k\Omega = 19.0 k\Omega \quad | \quad R_L = R_C \parallel R_3 = 43 k\Omega \parallel 100 k\Omega = 30.1 k\Omega$$

$$A_{mid} = -\frac{R_{in}}{R_1 + R_{in}} g_m R_L = -\frac{19.0 k\Omega}{1 k\Omega + 19.0 k\Omega} (4.00 mS)(30.1 k\Omega) = -114$$

$$C_p = \frac{g_m}{w_T} - C_m = \frac{4.00 mS}{2p(5 \times 10^8 Hz)} - 0.75 pF = 0.523 pF \quad | \quad f_H \cong \frac{1}{2p r_{po} C_T}$$

$$C_T = C_p + C_m \left(1 + g_m R_L + \frac{R_L}{r_{po}} \right) = 0.523 pF + 0.75 pF \left[1 + 4.00 mS(30.1 k\Omega) + \frac{30.1 k\Omega}{1.31 k\Omega} \right] = 109 pF$$

$$f_H \cong \frac{1}{2p(1.31 k\Omega)(1.09 \times 10^{-10} F)} = 1.12 MHz$$

$$(b) GBW = 114(1.12 MHz) = 128 MHz \quad | \quad \frac{1}{2p r_x C_m} = \frac{1}{2p(400 \Omega)(0.75 pF)} = 531 MHz$$

$$\text{Note : } \frac{1}{2p(R_s + r_x)C_m} = \frac{1}{2p(1.71 k\Omega)(0.75 pF)} = 124 MHz$$

17.55

$$A_{mid} = 39.2 \text{ dB}, f_L = 0 \text{ Hz}, f_H = 5.53 \text{ MHz}$$

17.56

$$R_{in} = R_1 \| R_2 = 4.3 \text{ M}\Omega \| 5.6 \text{ M}\Omega = 2.43 \text{ M}\Omega \quad | \quad R_L = 43 \text{ k}\Omega \| 1 \text{ M}\Omega = 41.2 \text{ k}\Omega$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2(0.2 \text{ mA})}{1} = 0.400 \text{ mS} \quad |$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} g_m R_L = -\frac{2.43 \text{ M}\Omega}{1 \text{ k}\Omega + 2.43 \text{ M}\Omega} 0.400 \text{ mS} (41.2 \text{ k}\Omega) = -16.5$$

$$f_H = \frac{1}{2\pi r_{po} C_T} \quad | \quad r_{po} = R_1 \| R_2 \| R_I = 1.00 \text{ k}\Omega$$

$$C_T = 5 \text{ pF} + 2 \text{ pF} \left[1 + (0.400 \text{ mS})(41.2 \text{ k}\Omega) + \frac{41.2 \text{ k}\Omega}{1 \text{ k}\Omega} \right] = 122 \text{ pF}$$

$$f_H = \frac{1}{2\pi (1 \text{ k}\Omega)(1.22 \times 10^{-10} \text{ F})} = 1.31 \text{ MHz} \quad | \quad GBW = 16.5(1.31 \text{ MHz}) = 21.5 \text{ MHz}$$

17.57

$$f_H = \frac{1}{2\pi r_{po} C_T} = \frac{1}{2\pi (656 \Omega) C_T} \quad | \quad C_T = \frac{1}{2\pi (656 \Omega)(5 \text{ MHz})} = 48.5 \text{ pF}$$

$$C_T = C_p + C_m \left[1 + g_m R_L + \frac{R_L}{r_{po}} \right] \quad | \quad R_L \left(g_m + \frac{1}{r_{po}} \right) = \frac{C_T - C_p}{C_m} - 1 = \frac{48.5 \text{ pF} - 19.9 \text{ pF}}{0.5 \text{ pF}} - 1 = 56.2$$

$$R_L = \frac{56.2}{\left(0.064 \text{ S} + \frac{1}{656 \Omega} \right)} = 858 \Omega \quad | \quad R_L = R_C \| 100 \text{ k}\Omega \rightarrow R_C = 865 \Omega$$


$$A_{mid} = -\frac{100(858 \Omega)}{882 \Omega + 250 \Omega + 1560 \Omega} = -31.9 \quad | \quad GBW = 31.9(5 \text{ MHz}) = 160 \text{ MHz}$$

$$\text{The nearest 5\% value is } R_C = 820 \Omega \quad | \quad R_L = 820 \Omega \| 100 \text{ k}\Omega = 813 \Omega$$

$$A_{mid} = -\frac{100(813 \Omega)}{882 \Omega + 250 \Omega + 1560 \Omega} = -30.2 \quad | \quad C_T = 19.9 + 0.5 \left[1 + 0.064(813) + \frac{813}{656} \right] = 47.0 \text{ pF}$$

$$f_H = \frac{1}{2\pi r_{po} C_T} = \frac{1}{2\pi (656 \Omega)(47.0 \text{ pF})} = 5.16 \text{ MHz} \quad | \quad GBW = 156 \text{ MHz}$$

17.58

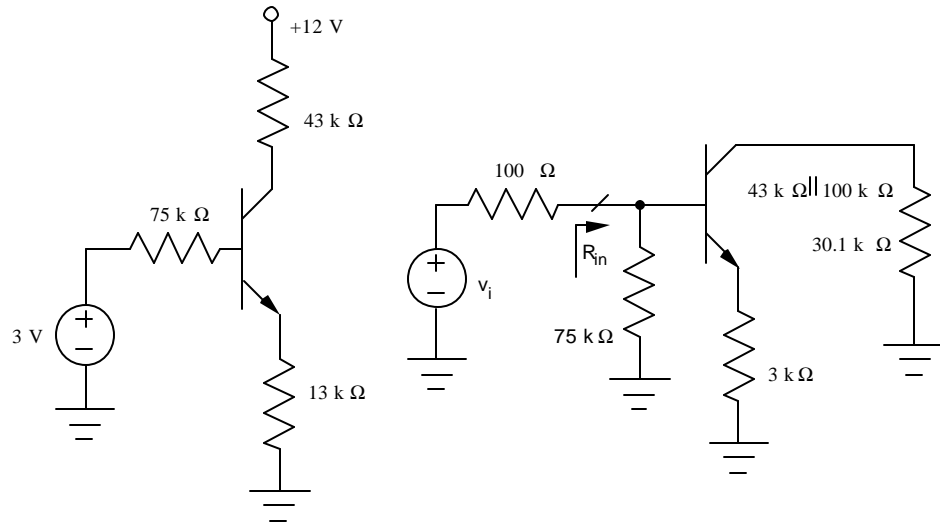

Short-Circuit Time Constants

$$R_{1s} = 100\Omega + 75k\Omega \parallel [300\Omega + 15.1k\Omega + 101(3k\Omega)] = 60.8k\Omega$$

$$R_{2s} = 43k\Omega + 100k\Omega = 143k\Omega$$

$$R_{3s} = 10k\Omega \parallel \left(3k\Omega + \frac{15.1k\Omega + 99.9\Omega}{101} \right) = 2.40k\Omega$$

$$f_L \approx \frac{1}{2p} \left[\frac{1}{(60.8k\Omega)(1mF)} + \frac{1}{(143k\Omega)(0.1mF)} + \frac{1}{(2.40k\Omega)(2.2mF)} \right] = 43.9Hz$$

Open-Circuit Time Constants

Using the results from Table 17.2 on page 1334 : $R_{th} + r_x = 99.9\Omega + 300\Omega = 400\Omega$

$$C_{TB} = \frac{3.02pF}{1 + (6.63mS)(3k\Omega)} \left(1 + \frac{3k\Omega}{400\Omega} \right) + 0.5pF \left[1 + \frac{(6.63mS)(30.1k\Omega)}{1 + (6.63mS)(3k\Omega)} + \frac{30.1k\Omega}{400\Omega} \right]$$

$$C_{TB} = 44.1pF \quad | \quad f_H = \frac{1}{2p(400\Omega)(44.1pF)} = 9.02MHz$$

$$(b) GBW = 9.45(9.02MHz - 43.9Hz) = 85.2MHz$$

17.59

Using the results from Table 17.2 on page 1334 : $R_{th} + r_x = 99.9\Omega + 300\Omega = 400\Omega$

$$C_{TB} = \frac{1}{2\pi(400\Omega)(7.5\text{MHz})} = 53.1\text{ pF}$$

$$C_{TB} = \frac{3.02\text{ pF}}{1 + (6.63\text{mS})R_E} \left(1 + \frac{R_E}{400\Omega}\right) + 0.5\text{ pF} \left[1 + \frac{(6.63\text{mS})(30.1\text{k}\Omega)}{1 + (6.63\text{mS})R_E} + \frac{30.1\text{k}\Omega}{400\Omega}\right] = 53.1\text{ pF}$$

Using MATLAB : $R_E = 957\ \Omega$

$$A_{mid} = 0.999 \frac{-100(30.1\text{k}\Omega)}{99.9\Omega + 300\Omega + 15.1\text{k}\Omega + 101(957\Omega)} = -26.8 \quad | \quad GBW = 201\text{ MHz}$$

The closest 5% resistor values are $R_E = 1\text{ k}\Omega$ and $R_6 = 12\text{ k}\Omega$

$$C_{TB} = \frac{3.02\text{ pF}}{1 + (6.63\text{mS})1\text{k}\Omega} \left(1 + \frac{1\text{k}\Omega}{400\Omega}\right) + 0.5\text{ pF} \left[1 + \frac{(6.63\text{mS})(30.1\text{k}\Omega)}{1 + (6.63\text{mS})1\text{k}\Omega} + \frac{30.1\text{k}\Omega}{400\Omega}\right] = 52.6\text{ pF}$$

$$f_H = \frac{1}{2\pi(400\Omega)(52.6\text{ pF})} = 7.56\text{ MHz}$$


$$A_{mid} = 0.999 \frac{-100(30.1\text{k}\Omega)}{99.9\Omega + 300\Omega + 15.1\text{k}\Omega + 101(1\text{k}\Omega)} = -25.8 \quad | \quad GBW = 195\text{ MHz}$$

17.60 (a)

$$I_C = 100 \left[\frac{3 - 0.7}{7.5\text{k}\Omega + 101(1.3\text{k}\Omega)} \right] = 1.66\text{ mA} \quad | \quad V_{CE} = 12 - 4.3\text{k}\Omega(I_C) - 1.3\text{k}\Omega \left(\frac{I_C}{\beta_F} \right) = 2.69\text{ V}$$

$$2.69\text{ V} \geq 0.7\text{ V} \quad \text{Active region operation is correct.} \quad | \quad r_p = \frac{100(0.025)}{1.66\text{ mA}} = 1.51\text{ k}\Omega$$

$$g_m = 40(1.66\text{ mA}) = 66.4\text{ mS} \quad | \quad C_p = \frac{66.4\text{ mS}}{2\pi(2 \times 10^8)} - 1 = 51.8\text{ pF} \quad | \quad r_x = 300\Omega \quad | \quad C_m = 1.0\text{ pF}$$

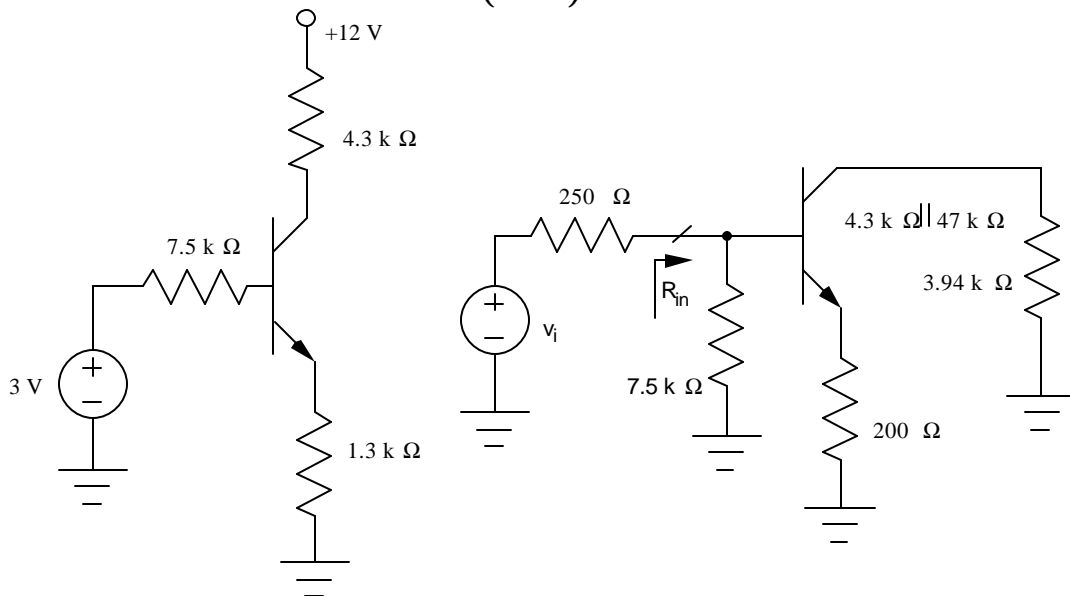

$$R_{in} = R_1 \| R_2 \| [r_x + r_p + (b_o + 1)R_{E1}] = 10k\Omega \| 30k\Omega \| [0.300k\Omega + 1.51k\Omega + (101)200\Omega] = 5.59 k\Omega$$

$$R_{th} = 7.5k\Omega \| 250\Omega = 242\Omega \quad | \quad R_L = 4.3k\Omega \| 47k\Omega = 3.94k\Omega$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} \left[\frac{b_o R_L}{r_x + r_p + (b_o + 1)R_{E1}} \right] = -\frac{5.59k\Omega}{250\Omega + 5.59k\Omega} \left[\frac{100(3.94k\Omega)}{22.0k\Omega} \right] = -17.1$$

(b) Using the Short-Circuit Time Constants:

$$R_{1S} = 250\Omega + 7.5k\Omega \| [300\Omega + 1.51k\Omega + 101(200\Omega)] = 5.84k\Omega$$

$$R_{2S} = 4.3k\Omega + 43k\Omega = 47.3k\Omega$$

$$R_{3S} = 1.1k\Omega \| \left(200\Omega + \frac{1.51k\Omega + 300 + 242\Omega}{101} \right) = 184\Omega$$

$$f_L \cong \frac{1}{2p} \left[\frac{1}{(5.84k\Omega)(5mF)} + \frac{1}{(47.3k\Omega)(1mF)} + \frac{1}{(184\Omega)(4.7mF)} \right] = 193Hz$$

(c) Using the Open-Circuit Time Constants:

$$\text{Using the results from Table 17.2 on page 1334} \quad : \quad R_{th} + r_x = 242\Omega + 300\Omega = 542\Omega$$

$$C_{TB} = \frac{51.8pF}{1 + (66.4mS)(200\Omega)} \left(1 + \frac{200\Omega}{542\Omega} \right) + 1pF \left[1 + \frac{(66.4mS)(3.94k\Omega)}{1 + (66.4mS)(200\Omega)} + \frac{3.94k\Omega}{542\Omega} \right]$$

$$C_{TB} = 31.6pF \quad f_L = \frac{1}{2p(542\Omega)(31.6pF)} = 9.29 MHz$$

17.61

Using the results in Table 17.2 on page 1334 and the values from Prob. 17.43 :

$$R_{th} + r_x = 242\Omega + 300\Omega = 542\Omega \quad | \quad C_{TB} = \frac{1}{2p(542\Omega)(10MHz)} = 29.4 pF$$

$$C_{TB} = \frac{51.8}{1 + (66.4mS)R_E} \left(1 + \frac{R_E}{542\Omega} \right) + 1pF \left[1 + \frac{(66.4mS)(3.94k\Omega)}{1 + (66.4mS)R_E} + \frac{3.94k\Omega}{542\Omega} \right] = 29.4 pF$$

Using MATLAB : $R_E = 224 \Omega$

The closest 5% resistor values are $R_E = 220 \Omega$ and $R_6 = 1.1 k\Omega$

$$C_{TB} = \frac{51.8pF}{1 + (66.4mS)220\Omega} \left(1 + \frac{220\Omega}{542\Omega} \right) + 1pF \left[1 + \frac{(66.4mS)(3.94k\Omega)}{1 + (66.4mS)220\Omega} + \frac{3.94k\Omega}{542\Omega} \right] = 29.7 pF$$


$$f_H = \frac{1}{2p(542\Omega)(29.7pF)} = 9.89MHz$$

$$R_{in} = R_1 \| R_2 \| [r_x + r_p + (b_o + 1)R_{E1}] = 10k\Omega \| 30k\Omega \| [0.300k\Omega + 1.51k\Omega + (101)220\Omega] = 5.72 k\Omega$$

$$R_{th} = 7.5k\Omega \| 250\Omega = 242\Omega \quad | \quad R_L = 4.3k\Omega \| 47k\Omega = 3.94k\Omega$$

$$A_{mid} = -\frac{R_{in}}{R_I + R_{in}} \left[\frac{b_o R_L}{r_x + r_p + (b_o + 1)R_{E1}} \right] = -\frac{5.72k\Omega}{250\Omega + 5.72k\Omega} \left[\frac{100(3.94k\Omega)}{24.0k\Omega} \right] = -15.7$$

17.62

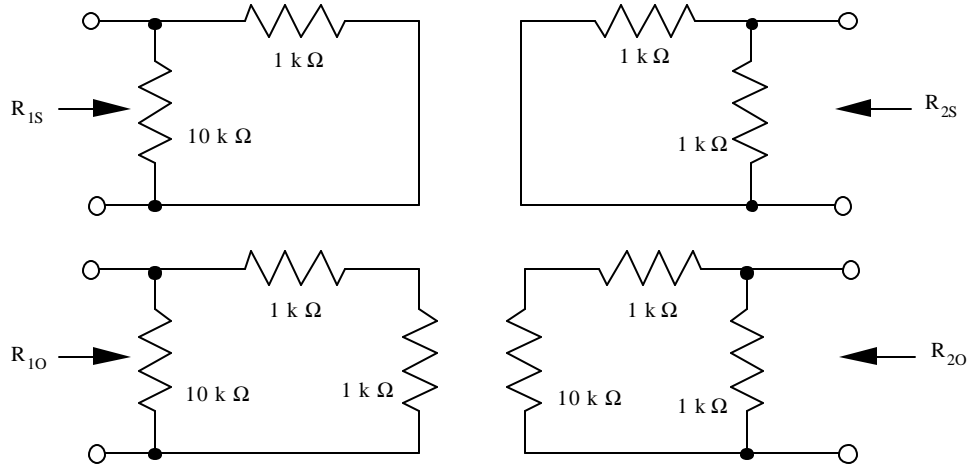

(a) SCTC:

$$R_{1s} = 10k\Omega \parallel 1k\Omega = 909\Omega \quad | \quad R_{2s} = 1k\Omega \parallel 1k\Omega = 500\Omega \quad | \quad w_L = \frac{1}{909(10^{-6})} + \frac{1}{500(10^{-5})} = 1300 \frac{rad}{s}$$

(b) OCTC:

$$R_{1o} = 10k\Omega \parallel 2k\Omega = 1.67k\Omega \quad | \quad R_{2o} = 1k\Omega \parallel 11k\Omega = 917\Omega \quad | \quad w_L = \frac{1}{1670(10^{-6}) + 917(10^{-5})} = 92.3 \frac{rad}{s}$$

(c) There are two poles. The SCTC technique assumes both are at low frequency and yields the largest pole. The OCTC assumes both are at high frequency and yields the smallest pole.


$$(d) \begin{bmatrix} (sC_1 + G_1 + G_2) & -G_2 \\ -G_2 & (sC_2 + G_2 + G_3) \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = 0$$

$$\Delta = s^2 C_1 C_2 + s[C_2(G_1 + G_2) + C_1(G_2 + G_3)] + G_1 G_2 + G_2 G_3 + G_1 G_3$$

$$\Delta = s^2 10^{-11} + s(1.30 \times 10^{-8}) + 1.20 \times 10^{-6}$$

$$\Delta = s^2 + 1300s + 1.20 \times 10^5 \rightarrow s = -1200, -100 \frac{rad}{s}$$

17.63

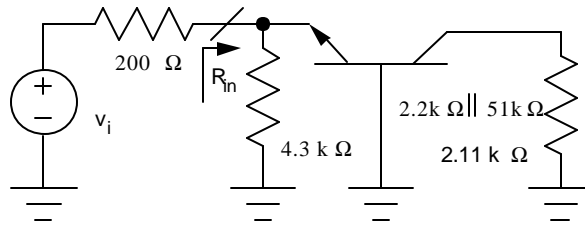

$$g_m = 40(1 \text{ mA}) = 0.04 \text{ S} \quad | \quad r_x = 300\Omega \quad | \quad r_p = \frac{100(0.025)}{1 \text{ mA}} = 2.50k\Omega \quad | \quad C_m = 0.6 \text{ pF}$$

$$C_p = \frac{40(10^{-3})}{2\pi(5 \times 10^8)} - 0.6 = 12.1 \text{ pF} \quad | \quad R_{th} = 4.3k\Omega \parallel 200\Omega = 191\Omega \quad | \quad R_L = 2.2k\Omega \parallel 51k\Omega = 2.11k\Omega$$

$$R_{in} = R_E \parallel \frac{(r_x + r_p)}{b_o + 1} = 4.3k\Omega \parallel \frac{(0.3k\Omega + 2.50k\Omega)}{101} = 27.6\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} \left(\frac{b_o R_L}{r_x + r_p} \right) = \frac{27.6\Omega}{200\Omega + 27.6\Omega} \frac{100(2.1k\Omega)}{2.80k\Omega} = +9.14$$

$$w_H = \frac{1}{191 \frac{12.1pF}{1+0.04(191)} \left(1 + \frac{300}{191} \right) + 0.6pF(300\Omega) \left[1 + \frac{0.04(2110)}{1+0.04(191)} \right] + 0.6pF(2110\Omega)}$$

$$f_H = \frac{1}{2p} \left(\frac{1}{6.876 \times 10^{-10} + 1.938 \times 10^{-9} + 1.266 \times 10^{-9}} \right) = 40.9 MHz$$

17.64 First, estimate the required SPICE parameters:

$$C_m = \frac{CJC}{\left(1 + \frac{V_{CB}}{PHIE} \right)^{ME}} \quad | \quad CJC = CJC = 0.6pF \left(1 + \frac{2.8}{0.75} \right)^{0.333} \cong 1.01pF$$


$$t_F = \frac{C_p}{g_m} = \frac{1}{w_T} - \frac{C_m}{g_m} = \frac{1}{10^9 p} - \frac{0.6pF}{40(1mA)} = 303 ps$$

*Figure 17.94 - Common-Base Amplifier

```
VCC 6 0 DC 5
VEE 7 0 DC -5
VI 1 0 AC 1
RI 1 2 200
C1 2 3 4.7UF
RE 3 7 4.3K
Q1 4 0 3 NBJT
RC 4 6 2.2K
C2 4 5 1UF
R3 5 0 51K
.MODEL NBJT NPN BF=100 RB=300 CJC=1.01PF TF=303PS
.OP
.AC DEC 50 1 50MEG
.PRINT AC VM(5)
.PROBE
.END
```

Results: $A_{mid} = 19.1 \text{ dB}$, $f_L = 149 \text{ Hz}$, $f_H = 43.8 \text{ MHz}$

17.65

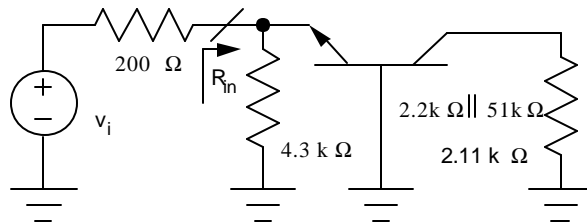

$$I_C = \alpha_F I_E = \frac{100}{101} \left[\frac{-0.7 - (-10)}{4300} \right] = 2.14 \text{ mA} \quad | \quad V_{CE} = 10 - (2.14 \text{ mA})(2.2k\Omega) - (-0.7) = 5.99 \text{ V}$$

$$g_m = 40(2.14 \text{ mA}) = 85.6 \text{ mS} \quad | \quad r_x = 300\Omega \quad | \quad r_p = \frac{100(0.025)}{2.14 \text{ mA}} = 1.17k\Omega \quad | \quad C_m = 0.6pF$$

$$C_p = \frac{85.6mS}{2p(5 \times 10^8)} - 0.6 = 26.7 pF \quad | \quad R_{th} = 4.3k\Omega \parallel 200\Omega = 191\Omega \quad | \quad R_L = 2.2k\Omega \parallel 51k\Omega = 2.11k\Omega$$


$$R_{in} = R_E \parallel \frac{(r_x + r_p)}{b_o + 1} = 4.3k\Omega \parallel \frac{(0.3k\Omega + 1.17k\Omega)}{101} = 14.5\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} \left(\frac{b_o R_L}{r_x + r_p} \right) = \frac{14.5\Omega}{200\Omega + 14.5\Omega} \frac{100(2.11k\Omega)}{1.47k\Omega} = +9.70$$

$$w_H = \frac{1}{191 \frac{26.7pF}{1 + 0.0856(191)} \left(1 + \frac{300}{191} \right) + 0.6pF(300\Omega) \left[1 + \frac{0.0856(2110)}{1 + 0.0856(191)} \right] + 0.6pF(2110\Omega)}$$

$$f_H = \frac{1}{2p} \left(\frac{1}{7.556 \times 10^{-10} + 2.054 \times 10^{-9} + 1.266 \times 10^{-9}} \right) = 39.1 MHz$$

17.66

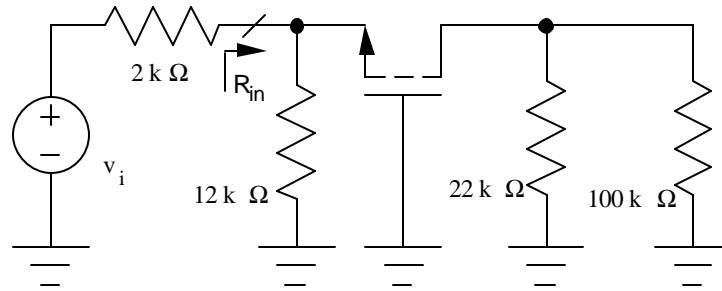

$$R_{th} = 12k\Omega \parallel 2k\Omega = 1.71k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0k\Omega \quad | \quad C_{GS} = 3.0pF \quad | \quad C_{GD} = 0.6pF$$

$$g_m = \frac{2(0.1mA)}{1V} = 0.2mS \quad | \quad R_{in} = 12k\Omega \parallel \frac{1}{g_m} = 12k\Omega \parallel \frac{1}{0.2mS} = 3.53k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{3.53k\Omega}{2k\Omega + 3.53k\Omega} (0.2mS)(18.0k\Omega) = +2.30$$

$$f_H = \frac{1}{2p} \left(\frac{1}{\frac{C_{GS}}{G_{th} + g_m} + C_{GD} R_L} \right) = \frac{1}{2p} \left(\frac{1}{\frac{3.0pF}{(0.5848 + 0.2)mS} + 0.6pF(18.0k\Omega)} \right) = 10.9 MHz$$

17.67 First, calculate the SPICE parameters require to achieve $I_D = 0.1mA$:

$$V_{GG} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87V \quad | \quad V_{GG} - V_{GS} = 0.1mA(12k\Omega) \rightarrow V_{GS} = 3.67V$$

$$V_{GS} - V_{TN} = 1V \rightarrow V_{TN} = 2.67V \quad | \quad K_n = \frac{2I_D}{(V_{GS} - V_{TN})^2} = \frac{2(0.1mA)}{1^2} = 0.2mS$$

*Problem 17.21 - Common-Source Amplifier

VDD 7 0 DC 12

VS 1 0 AC 1

RS 1 2 2K

```

C1 2 3 4.7UF
R4 3 0 12K
R1 4 0 1.5MEG
R2 7 4 2.2MEG
C2 4 0 0.1UF
R3 7 5 22K
C3 5 6 0.1UF
R7 6 0 100K
M1 5 4 3 3 NFET
.MODEL NFET NMOS VTO=2.67 KP=0.200M CGSO=30NF CGDO=6NF
.OP
.AC DEC 100 1 50MEG
.PRINT AC VM(6) VP(6)
.END

```

Results: $A_{mid} = 2.30$, $f_L = 15.5$ Hz, $f_H = 13.2$ MHz

17.68

(a) First find V_{TN} and K_n based upon Problem 17.21


$$V_{GG} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 12V = 4.87V \quad | \quad V_{GG} - V_{GS} = 0.1mA(12k\Omega) \rightarrow V_{GS} = 3.67V$$

$$V_{GS} - V_{TN} = 1V \rightarrow V_{TN} = 2.67V \quad | \quad K_n = \frac{2I_D}{(V_{GS} - V_{TN})^2} = \frac{2(0.1mA)}{1^2} = 0.2mS$$

$$\text{Now, find the Q - point for } V_{DD} = 18V: V_{GG} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 18V = 7.30V$$

$$R_{GG} = 1.5M\Omega \parallel 2.2M\Omega = 892k\Omega \quad | \quad V_{GG} - V_{GS} = I_D R_S$$

$$7.30 - V_{GS} = (12k\Omega) \left(\frac{0.2mS}{2} \right) (V_{GS} - 2.67)^2 \rightarrow V_{GS} = 4.73V \quad | \quad I_D = 0.254 \text{ mA} \quad | \quad V_{DS} = 9.37V \text{ ok}$$

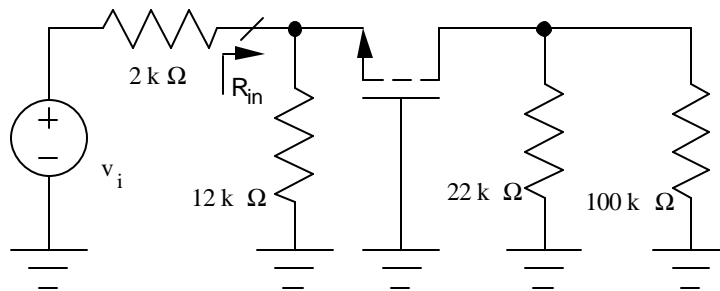

$$R_{th} = 12k\Omega \parallel 2k\Omega = 1.71k\Omega \quad | \quad R_L = 22k\Omega \parallel 100k\Omega = 18.0k\Omega \quad | \quad C_{GS} = 3.0pF \quad | \quad C_{GD} = 0.6pF$$

$$g_m = \frac{2(0.254mA)}{(4.26 - 2.67)V} = 0.320mS \quad | \quad R_{in} = 12k\Omega \parallel \frac{1}{g_m} = 12k\Omega \parallel \frac{1}{0.320mS} = 2.48k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L = \frac{2.48k\Omega}{2k\Omega + 2.48k\Omega} (0.320mS)(18.0k\Omega) = +3.19$$

$$f_H = \frac{1}{2p} \left(\frac{1}{\frac{C_{GS}}{G_{th} + g_m} + C_{GD}R_L} \right) = \frac{1}{2p} \left(\frac{1}{\frac{3.0pF}{(0.5848 + 0.32)mS} + 0.6pF(18.0k\Omega)} \right) = 11.3 MHz$$

17.69 First, calculate the SPICE parameters required to achieve $I_D = 0.1mA$:

$$V_{GG} = \frac{1.5M\Omega}{1.5M\Omega + 2.2M\Omega} 10V = 4.05V \quad | \quad V_{GG} - V_{GS} = 0.1mA(12k\Omega) \rightarrow V_{GS} = 2.85V$$

$$V_{GS} - V_{TN} = 0.75V \rightarrow V_{TN} = 2.10V \quad | \quad K_n = \frac{2I_D}{(V_{GS} - V_{TN})^2} = \frac{2(0.1mA)}{(0.75)^2} = 0.356 \frac{mA}{V^2}$$

$$g_m = \frac{2(0.1mA)}{0.75V} = 0.267mS \quad | \quad R_{in} = R_1 \parallel R_2 = 892k\Omega \quad | \quad R_L = 12k\Omega \parallel 100k\Omega = 10.7k\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} \frac{g_m R_L}{1 + g_m R_L} = 0.998 \frac{(0.267mS)(10.7k\Omega)}{1 + (0.267mS)(10.7k\Omega)} = +0.739 \quad (-2.62 dB)$$

$$\text{From Table 17.2 on page 1334 : } f_H = \frac{1}{2p(2k\Omega \parallel 892k\Omega) \left[\frac{3pF}{1 + (0.267mS)(10.7k\Omega)} + 0.6pF \right]} = 57.9 MHz$$

Note that a low frequency RHP zero makes the calculation of f_H a very poor estimate for the FET case. See the analysis in Prob. 17.73 which shows $\omega_z = -g_m/C_{GS}$.

*Problem 17.69 - Common-Drain Amplifier

VDD 6 0 DC 10

VS 1 0 AC 1

RS 1 2 2K

C1 2 3 4.7UF

R1 3 0 1.5MEG

R2 6 3 2.2MEG

M1 6 3 4 4 NFET

R4 4 0 12K

C3 4 5 0.1UF

R7 5 0 100K

.MODEL NFET NMOS VTO=2.10 KP=0.356MS CGSO=30NF CGDO=6NF

.OP

.AC DEC 100 1 500MEG

.PRINT AC VM(5) VP(5)

.END

Results: $A_{mid} = 0.740$, $f_L = 15.5 Hz$, $f_H = 195MHz$ - Note that there is peaking in the response.

17.70

First find V_{DD} , V_{TN} and K_n from Prob. 17.22: $V_{DD} = V_{DS} + I_D R_S = 10 \text{ V}$

$$V_{GG} = \frac{1.5 \text{ M}\Omega}{1.5 \text{ M}\Omega + 2.2 \text{ M}\Omega} 10 \text{ V} = 4.05 \text{ V} \quad | \quad V_{GG} - V_{GS} = 0.1 \text{ mA}(12 \text{ k}\Omega) \rightarrow V_{GS} = 2.85 \text{ V}$$

$$V_{GS} - V_{TN} = 0.75 \text{ V} \rightarrow V_{TN} = 2.10 \text{ V} \quad | \quad K_n = \frac{2I_D}{(V_{GS} - V_{TN})^2} = \frac{2(0.1 \text{ mA})}{(0.75)^2} = 0.356 \frac{\text{mA}}{\text{V}^2}$$

Now find the new Q - point with $V_{DD} = 18 \text{ V}$.

$$V_{GG} = \frac{1.5 \text{ M}\Omega}{1.5 \text{ M}\Omega + 2.2 \text{ M}\Omega} 18 \text{ V} = 7.30 \text{ V} \quad | \quad R_{GG} = 1.5 \text{ M}\Omega \parallel 2.2 \text{ M}\Omega = 892 \text{ k}\Omega \quad | \quad V_{GG} - V_{GS} = I_D R_S$$

$$7.30 - V_{GS} = (12 \text{ k}\Omega) \left(\frac{0.356 \text{ mA}}{2 \text{ V}^2} \right) (V_{GS} - 2.10)^2 \rightarrow V_{GS} = 3.44 \text{ V} \quad | \quad I_D = 0.321 \text{ mA} \quad | \quad V_{DS} = 14.2 \text{ V} \text{ ok}$$

$$g_m = \frac{2(0.321 \text{ mA})}{(3.44 - 2.10) \text{ V}} = 0.479 \text{ mS} \quad | \quad R_{in} = R_1 \parallel R_2 = 892 \text{ k}\Omega \quad | \quad R_L = 12 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 10.7 \text{ k}\Omega$$

$$A_{mid} = \frac{R_{in}}{R_I + R_{in}} \frac{g_m R_L}{1 + g_m R_L} = 0.998 \frac{(0.479 \text{ mS})(10.7 \text{ k}\Omega)}{1 + (0.479 \text{ mS})(10.7 \text{ k}\Omega)} = +0.835 \quad (-1.57 \text{ dB})$$

$$\text{From Table 17.2 on page 1334: } f_H = \frac{1}{2p(2 \text{ k}\Omega \parallel 892 \text{ k}\Omega) \left[\frac{3 \text{ pF}}{1 + (0.479 \text{ mS})(10.7 \text{ k}\Omega)} + 0.6 \text{ pF} \right]} = 73.0 \text{ MHz}$$

17.71

$$g_m = 40(0.25 \text{ mA}) = 10.0 \text{ mS} \quad | \quad r_x = 300 \Omega \quad | \quad r_p = \frac{100(0.025)}{0.25 \text{ mA}} = 10.0 \text{ k}\Omega$$

$$C_m = 0.6 \text{ pF} \quad | \quad C_p = \frac{0.01}{2p(5 \times 10^8)} - 0.6 = 2.58 \text{ pF} \quad | \quad R_B = 100 \text{ k}\Omega \parallel 300 \text{ k}\Omega = 75.0 \text{ k}\Omega$$

$$R_L = 13 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 11.5 \text{ k}\Omega \quad | \quad R_{th} = 75 \text{ k}\Omega \parallel 2 \text{ k}\Omega = 1.95 \text{ k}\Omega$$

$$R_{in} = R_B \parallel [r_x + r_p + (b_o + 1)R_L] = 75.0 \text{ k}\Omega \parallel [300 \Omega + 10.0 \text{ k}\Omega + (101)(11.5 \text{ k}\Omega)] = 70.5 \text{ k}\Omega$$

$$A_{mid} = \left(\frac{R_{in}}{R_I + R_{in}} \right) \frac{(b_o + 1)R_L}{r_x + r_p + (b_o + 1)R_L} = 0.972 \frac{101(11.5 \text{ k}\Omega)}{[0.300 + 10.0 + 101(11.5)] \text{ k}\Omega} = 0.964$$

$$f_H \cong \frac{1}{2p} \frac{1}{(1950 + 300) \left[\frac{2.58 \text{ pF}}{1 + 10 \text{ mS}(11.5 \text{ k}\Omega)} + 0.6 \text{ pF} \right]} = \frac{1}{2p} \frac{1}{(2250)(0.622 \text{ pF})} = 114 \text{ MHz}$$

(b) Calculating the required SPICE parameters:

$$C_m = \frac{CJC}{\left(1 + \frac{V_{CB}}{PHIE} \right)^{ME}} \quad | \quad CJC = 0.6 \text{ pF} \left(1 + \frac{11.8}{0.75} \right)^{0.333} \cong 1.54 \text{ pF}$$

$$t_F = \frac{C_p}{g_m} = \frac{1}{w_T} - \frac{C_m}{g_m} = \frac{1}{10^9 \text{ p}} - \frac{0.6 \text{ pF}}{40(0.25 \text{ mA})} = 260 \text{ ps} \quad | \quad TF = 260 \text{ ps}$$

*Problem 17.71 - Common-Collector Amplifier

```

VCC 6 0 DC 15
VS 1 0 AC 1
RS 1 2 2K
C1 2 3 4.7UF
R1 3 0 100K
R2 6 3 300K
Q1 6 3 4 NBJT
R4 4 0 13K
C3 4 5 10UF
R7 5 0 100K
.MODEL NBJT NPN BF=100 TF=260PS CJC=1.54PF RB=300
.OP
.AC DEC 100 0.1 200MEG
.PRINT AC VM(5) VP(5)
.END

```

Results: $A_{mid} = 0.962$, $f_L = 0.52 \text{ Hz}$, $f_H = 110 \text{ MHz}$

17.72

$$V_{BB} = 9V \frac{100k\Omega}{100k\Omega + 300k\Omega} = 2.25V \quad | \quad R_B = 100k\Omega \parallel 300k\Omega = 75.0k\Omega$$

$$I_C = 100 \frac{(2.25 - 0.7)V}{75.0k\Omega + 101(13k\Omega)} = 0.251mA$$

$$g_m = 40(0.251mA) = 10.0mS \quad | \quad r_x = 300\Omega \quad | \quad r_p = \frac{100(0.025)}{0.251mA} = 9.96k\Omega$$

$$C_m = 0.6pF \quad | \quad C_p = \frac{0.01}{2\pi(5 \times 10^8)} - 0.6 = 2.58pF$$


$$R_L = 13k\Omega \parallel 100k\Omega = 11.5k\Omega \quad | \quad R_{th} = 75k\Omega \parallel 2k\Omega = 1.95k\Omega$$

$$R_{in} = R_B \parallel [r_x + r_p + (b_o + 1)R_L] = 75.0k\Omega \parallel [300\Omega + 9.96k\Omega + (101)11.5k\Omega] = 70.5k\Omega$$

$$A_{mid} = \left(\frac{R_{in}}{R_I + R_{in}} \right) \frac{(b_o + 1)R_L}{r_x + r_p + (b_o + 1)R_L} = 0.972 \frac{101(11.5k\Omega)}{[0.300 + 9.96 + 101(11.5)]k\Omega} = 0.964$$

$$f_H \cong \frac{1}{2\pi} \frac{1}{(1950 + 300) \left[\frac{2.58pF}{1 + 10mS(11.5k\Omega)} + 0.6pF \right]} = \frac{1}{2\pi} \frac{1}{(2250)(0.622pF)} = 114 \text{ MHz}$$

17.73

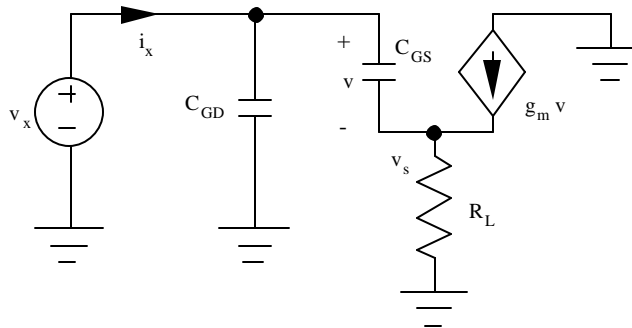


$$I_x = sC_{GD}V_x + sC_{GS}(V_x - V_s) \quad | \quad V_x = V + (sC_{GS}V + g_m V)R_L \quad | \quad V = \frac{V_x}{(1 + g_m R_L + sC_{GS}R_L)}$$

$$I_x = sC_{GD}V_x + sC_{GS} \frac{V_x}{(1 + g_m R_L + sC_{GS}R_L)} \quad | \quad \text{Note: } V_s = \frac{(sC_{GS} + g_m)R_L}{(1 + g_m R_L + sC_{GS}R_L)} V_x$$

$$\frac{I_x}{V_x} = s \left[C_{GD} + \frac{C_{GS}}{1 + g_m R_L} \frac{1}{1 + s \frac{C_{GS}R_L}{1 + g_m R_L}} \right] \quad | \quad \frac{C_{GS}R_L}{1 + g_m R_L} \approx \frac{C_{GS}R_L}{g_m R_L} = \frac{C_{GS}}{g_m} \quad \& \quad \frac{g_m}{C_{GS}} > \omega_T$$

$$\text{Assuming } \omega \ll \omega_T: \quad C_{IN} \approx C_{GD} + \frac{C_{GS}}{1 + g_m R_L} \quad | \quad \text{Note the zero in } V_s \text{ at } \omega_z = -\frac{g_m}{C_{GS}} \quad \underline{\hspace{10em}}$$

17.74

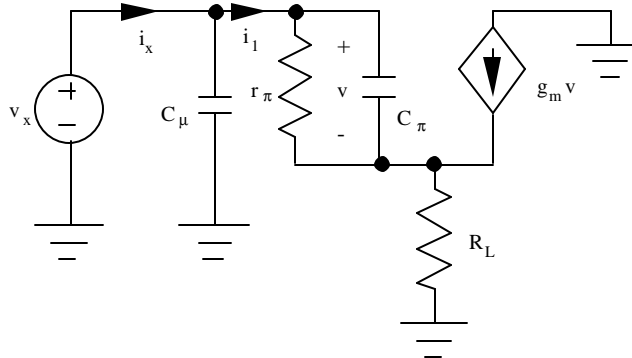

$$I_x = sC_\mu V_x + I_1 \quad | \quad V_x = \frac{I_1}{(sC_p + g_p)} + \left(I_1 + g_m \frac{I_1}{(sC_p + g_p)} \right) R_L$$

$$Z_1 = \frac{V_x}{I_1} = \frac{sC_p r_p R_L + R_L + r_p + b_o R_L}{sC_p r_p + 1} = \frac{sC_p r_p R_L + r_p + (b_o + 1)R_L}{sC_p r_p + 1}$$

$$Y_1 = \frac{1}{Z_1} = \frac{\frac{sC_p r_p}{r_p + (b_o + 1)R_L} + \frac{1}{r_p + (b_o + 1)R_L}}{s \frac{C_p r_p R_L}{r_p + (b_o + 1)R_L} + 1} \cong \frac{\frac{sC_p}{(1 + g_m R_L)} + \frac{1}{r_p + (b_o + 1)R_L}}{s \frac{C_p R_L}{(1 + g_m R_L)} + 1} \text{ for } b_o \gg 1$$

$$w \frac{C_p R_L}{(1 + g_m R_L)} \ll 1 \rightarrow w \ll \frac{1}{C_p} \left(\frac{1}{R_L} + g_m \right) \text{ but } \frac{1}{C_p} \left(\frac{1}{R_L} + g_m \right) > w_T$$

So, for $w \ll w_T$, $Y_1 \cong s \frac{C_p}{(1 + g_m R_L)} + \frac{1}{r_p + (b_o + 1)R_L}$

$$C_{in} = C_\mu + \frac{C_p}{(1 + g_m R_L)} \quad \text{and} \quad R_{in} = r_p + (b_o + 1)R_L$$

w_H is determined by the input capacitance C_{in} and the source resistance $R_{th} + r_x$.

17.75

$$w_H = \frac{g_{m1}}{C_{GS1} + C_{GS2} + C_{GD2}(1 + g_{m1}r_{o2} + g_{m2}r_{o2})}$$

$$g_{m1} = g_{m2} = \sqrt{2(25 \times 10^{-6}) \left(\frac{5}{1} \right) (10^{-4})} = 158 \text{ mS} \quad | \quad r_{o2} \cong \frac{50V}{0.1mA} = 500k\Omega$$

$$C_{GS1} = 3pF \quad | \quad C_{GS2} = 3pF \quad | \quad C_{GD1} = 0.5pF \quad | \quad C_{GD2} = 0.5pF$$

$$f_H = \frac{1}{2\pi} \frac{158mS}{3pF + 3pF + 0.5pF [1 + 2(0.158mS)500k\Omega]} = 294 \text{ kHz}$$

17.76

$$w_H = \frac{g_{m1}}{C_{GS1} + C_{GS2} + C_{GD2}(1 + g_{m1}r_{o2} + g_{m2}r_{o2})} \quad | \quad I_{D2} = 5I_{D1} = 1.00\text{mA} \quad | \quad r_{o2} = \frac{50\text{V}}{1\text{mA}} = 50\text{k}\Omega$$

$$g_{m1} = \sqrt{2(25 \times 10^{-6}) \left(\frac{5}{1} \right) (2 \times 10^{-4})} = 224 \mu\text{S} \quad | \quad g_{m2} = \sqrt{2(25 \times 10^{-6}) \left(\frac{25}{1} \right) (1 \times 10^{-3})} = 1.12\text{mS}$$

$$C_{GS} \text{ \& } C_{GD} \propto W : C_{GS1} = 3\text{pF} \quad | \quad C_{GS2} = 15\text{pF} \quad | \quad C_{GD1} = 1\text{pF} \quad | \quad C_{GD2} = 5\text{pF}$$

$$f_H = \frac{1}{2\text{p}} \frac{0.224\text{mS}}{3\text{pF} + 15\text{pF} + 5\text{pF} [1 + (1.12\text{mS} + 0.224\text{mS})50\text{k}\Omega]} = 99.3\text{kHz}$$

17.77 The most probable answer that will be produced is

$$w_H = \frac{g_{m1}}{C_{p1} + C_{p2} + C_{m2} [1 + (g_{m1} + g_{m2})r_{o2}]} \quad | \quad I_{C2} \cong 10I_{C1} = 1.00\text{mA} \quad | \quad r_{o2} = \frac{60\text{V}}{1.00\text{mA}} = 60\text{k}\Omega$$

$$C_{p1} = \frac{40(10^{-4})}{1.2 \times 10^9 \text{p}} - 0.5\text{pF} = 0.561\text{pF} \quad | \quad C_{p2} = \frac{40(10^{-3})}{1.2 \times 10^9 \text{p}} - 0.5\text{pF} = 10.1\text{pF}$$

$$f_H = \frac{1}{2\text{p}} \frac{40(10^{-4})}{0.561\text{pF} + 10.1\text{pF} + 0.5\text{pF} [1 + 40(1.1\text{mA})60\text{k}\Omega]} = 478\text{kHz}$$

However, C_μ should be approximately proportional to emitter area:

$$C_{m2} = 10C_{m1} = 5.00\text{pF} \quad | \quad C_{p2} = \frac{40(10^{-3})}{1.2 \times 10^9 \text{p}} - 5.00\text{pF} = 5.10\text{pF}$$

$$f_H = \frac{1}{2\text{p}} \frac{40(10^{-4})}{0.561\text{pF} + 5.10\text{pF} + 5.00\text{pF} [1 + 40(1.1\text{mA})60\text{k}\Omega]} = 48.2\text{kHz}$$


17.78

$$w_H = \frac{g_{m1}}{C_{p1} + C_{p2} + C_{m2} [1 + (g_{m1} + g_{m2})r_{o2}]} \quad | \quad I_{C2} \cong I_{C1} = 100\mu\text{A}$$

$$r_{o2} = \frac{60\text{V}}{100\mu\text{A}} = 600\text{k}\Omega \quad | \quad C_{p2} = C_{p1} = \frac{40(10^{-4})}{10^8 \text{p}} - 2\text{pF} = 10.7\text{pF}$$

$$f_H = \frac{1}{2\text{p}} \left[\frac{40(10^{-4})}{10.7\text{pF} + 10.7\text{pF} + 2\text{pF} (1 + 2(40)(0.100\text{mA})600\text{k}\Omega)} \right] = 66.2\text{kHz}$$

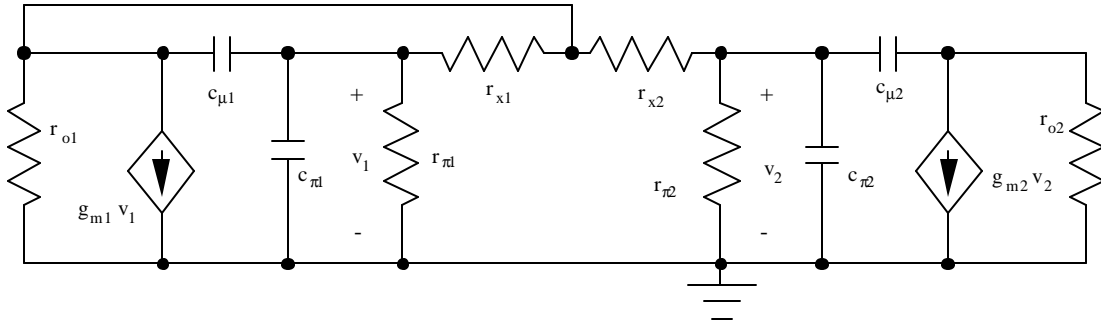17.79 With the addition of r_x , we must re-evaluate the open-circuit time constants.



Assume: $r_x \ll r_o$

$$C_{p2} \text{ \& } C_{m2} \text{ are part of a common - emitter stage with } r_{p2} = r_{p2} \left\| \left(r_{x2} + \frac{1}{g_{m1}} \right) \right\| \cong \frac{1 + g_{m1} r_{x2}}{g_{m1}}$$

$$C_{p1} : R_{p1o}^{-1} = g_{p1} + g_{x1} \left(1 + \frac{g_{m1}}{g_{x1} + g_{o1} + \frac{1}{r_{x2} + r_{p2}}} \right) \mid R_{p1o} \cong \frac{r_{x1}}{1 + g_{m1} r_{x1}} \cong \frac{1}{g_{m1}}$$

$$C_m : R_{mo} = \frac{r_{x1}}{1 + \frac{1}{b_o} + \frac{1}{g_m R}} \text{ with } R = r_{o1} \parallel (r_{x2} + r_{p2}) \mid R_{mo} \cong r_{x1}$$

$$w_H = \left\{ C_{p1} \frac{r_{x1}}{1 + g_{m1} r_{x1}} + C_{m1} r_{x1} + \frac{1 + g_{m1} r_{x2}}{g_{m1}} [C_{p2} + C_{m2} (1 + g_{m2} r_{o2})] \right\}^{-1}$$

$$\text{The last term will be dominant} : w_H \cong \frac{1}{\frac{1 + g_{m1} r_{x2}}{g_{m1}} C_{m2} (1 + g_{m2} r_{o2})}$$

The most probable answer that will be generated is

$$I_{C2} \cong 4I_{C1} = 1.00 \text{ mA} \mid r_{o2} = \frac{50 \text{ V}}{1.00 \text{ mA}} = 50 \text{ k}\Omega \mid g_{m2} = 40(0.001) = 40 \text{ mS}$$


$$C_{p1} = \frac{40(2.5 \times 10^{-4})}{10^9 \text{ p}} - 0.3 \text{ pF} = 2.88 \text{ pF} \mid C_{p2} = \frac{40(10^{-3})}{10^9 \text{ p}} - 0.3 \text{ pF} = 9.73 \text{ pF}$$

$$f_H \cong \frac{1}{2 \text{ p}} \frac{1}{\frac{1 + 0.01 \text{ S}(175 \Omega)}{0.01 \text{ S}} 0.3 \text{ pF} [1 + 40 \text{ mS}(50 \text{ k}\Omega)]} = 964 \text{ kHz}$$


However, C_μ should be approximately proportional to emitter area:

$$C_{m2} = 4C_m = 1.2 \text{ pF} \mid f_H \cong \frac{1}{2 \text{ p}} \frac{1}{\frac{1 + 0.01 \text{ S}(175 \Omega)}{0.01 \text{ S}} 1.2 \text{ pF} [1 + 40 \text{ mS}(50 \text{ k}\Omega)]} = 241 \text{ kHz}$$

17.80

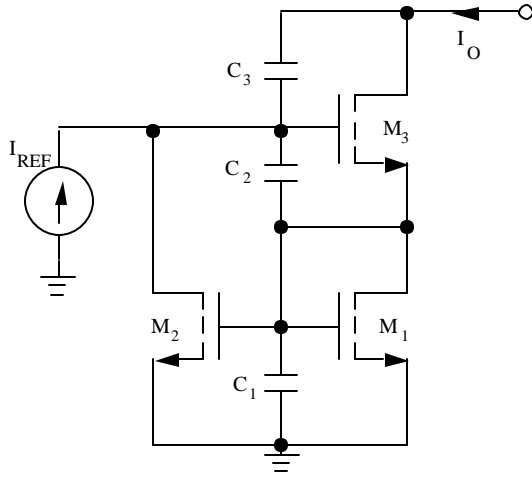


C1:

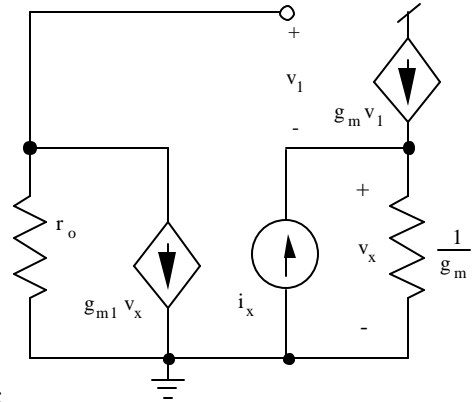


$$C_1 = C_{GS1} + C_{GS2} \quad | \quad C_2 = C_{GD2} + C_{GS3} \quad | \quad C_3 = C_{GD3}$$

$$R_{1O} : v_x = (i_x + g_m v_1) \frac{1}{g_m} \quad | \quad v_1 = -m_f v_x - v_x \quad | \quad R_{1O} = \frac{v_x}{i_x} = \frac{1}{g_m(m_f + 2)}$$

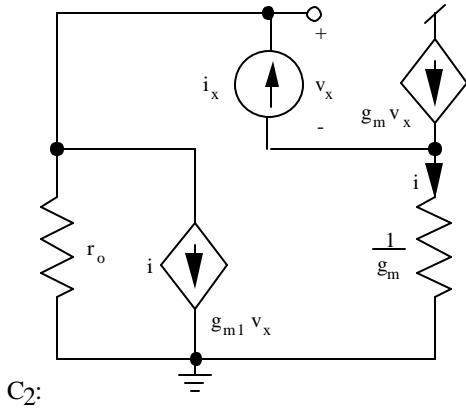

C2:

C3:

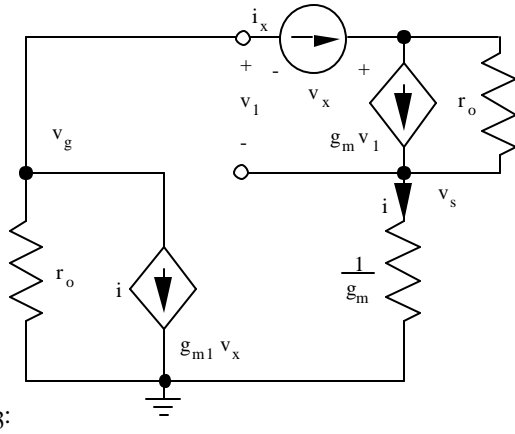

$$R_{2O} : v_x = (i_x - i)r_o - (g_m v_x - i_x) \frac{1}{g_m} \quad | \quad i = g_m v_x - i_x$$

$$2v_x = i_x \left(r_o + \frac{1}{g_m} \right) - r_o (g_m v_x - i_x) \quad | \quad R_{2O} = \frac{v_x}{i_x} = \frac{2r_o + \frac{1}{g_m}}{m_f + 2} \cong \frac{2}{g_m}$$

$$R_{3O}: v_x = (i_x - g_m v_1) r_o + \frac{i_x}{g_m} - (i_x + i) r_o \quad | \quad i = i_x \quad | \quad v_1 = -2i_x r_o - \frac{i_x}{g_m}$$

$$R_{3O} = \frac{v_x}{i_x} = 2m_f r_o + 4r_o + \frac{1}{g_m} \cong 2(m_f + 2)r_o \cong 2m_f r_o$$

$$w_H \cong \frac{1}{\frac{2C_{GS}}{g_m m_f} + 2\frac{C_{GS} + C_{GD}}{g_m} + 2m_f r_o C_{GD}} \cong \frac{1}{2m_f r_o C_{GD}} = \frac{1}{2g_m r_o^2 C_{GD}}$$

$$f_H \cong \frac{1}{2p} \frac{1}{2\sqrt{2(2.5 \times 10^{-4})(2.5 \times 10^{-4})} \left(\frac{50}{2.5 \times 10^{-4}} \right)^2 (10^{-12})} = 5.63 \text{ kHz}$$

Note: R_{3O} neglects any attached load resistance. If a load exists, essentially all of i_x will go through the load R_L , and the frequency response will significantly improve. For that case, $R_{3O} \sim R_L + r_o \sim r_o$.

17.81

$$(a) r_p = \frac{100(0.025)}{15 \times 10^{-6}} = 167 \text{ k}\Omega \quad | \quad C_m = 0.5 \text{ pF} \quad | \quad C_p = \frac{40(15 \times 10^{-6})}{2p(75 \times 10^6)} - 0.5 \text{ pF} = 0.773 \text{ pF}$$

$$r_{po} = r_p || r_x = 167 \text{ k}\Omega || 500 \Omega = 499 \Omega \quad | \quad g_m = 40(15 \times 10^{-6}) = 0.6 \text{ mS} \quad | \quad w_H = \frac{1}{r_{po} C_T} \quad |$$

$$C_T = 0.773 + 0.5 \left[1 + 0.6 \text{ mS}(430 \text{ k}\Omega) + \frac{430 \text{ k}\Omega}{499 \Omega} \right] = 561 \text{ pF} \quad | \quad f_H = \frac{1}{2p(499)(5.61 \times 10^{-10})} = 568 \text{ kHz}$$

$$(b) r_p = \frac{100(0.025)}{5 \times 10^{-5}} = 50.0 \text{ k}\Omega \quad | \quad C_m = 0.5 \text{ pF} \quad | \quad C_p = \frac{40(5 \times 10^{-5})}{2p(75 \times 10^6)} - 0.5 \text{ pF} = 3.74 \text{ pF}$$

$$r_{po} = r_p || r_x = 50 \text{ k}\Omega || 500 \Omega = 495 \Omega \quad | \quad g_m = 40(5 \times 10^{-5}) = 2.00 \text{ mS} \quad | \quad w_H = \frac{1}{r_{po} C_T} \quad |$$

$$C_T = 3.74 + 0.5 \left[1 + 2.0 \text{ mS}(140 \text{ k}\Omega) + \frac{140 \text{ k}\Omega}{495 \Omega} \right] = 285 \text{ pF} \quad | \quad f_H = \frac{1}{2p(495)(2.85 \times 10^{-10})} = 1.13 \text{ MHz}$$

17.82

$$(a) C_m = 1 \text{ pF} \quad | \quad C_p = \frac{40(125 \times 10^{-6})}{2p(100 \times 10^6)} - 1 \text{ pF} = 6.96 \text{ pF} \quad | \quad r_x = 500 \Omega \quad | \quad g_m = 40(125 \times 10^{-6}) = 5.00 \text{ mS}$$

$$C_T = 6.96 + 1.0 \left[2 + \frac{5.00 \text{ mS}(62 \text{ k}\Omega)}{2} + \frac{62 \text{ k}\Omega}{0.500 \text{ k}\Omega} \right] = 288 \text{ pF} \quad | \quad f_H = \frac{1}{2p(500)(2.88 \times 10^{-10})} = 1.11 \text{ MHz}$$

$$(b) C_p = \frac{40(1 \times 10^{-3})}{2p(100 \times 10^6)} - 1 \text{ pF} = 62.7 \text{ pF} \quad | \quad r_x = 500 \Omega \quad | \quad g_m = 40(1 \times 10^{-3}) = 40.0 \text{ mS}$$

$$C_T = 62.7 + 1.0 \left[2 + \frac{40.0 \text{ mS}(7.5 \text{ k}\Omega)}{2} + \frac{7.5 \text{ k}\Omega}{0.500 \text{ k}\Omega} \right] = 230 \text{ pF} \quad | \quad f_H = \frac{1}{2p(500)(2.30 \times 10^{-10})} = 1.39 \text{ MHz}$$

17.83

$$(a) C_m = 1 \text{ pF} \quad | \quad C_p = \frac{40(100 \times 10^{-6})}{2p(100 \times 10^6)} - 1 \text{ pF} = 5.37 \text{ pF} \quad | \quad r_x = 500 \Omega \quad | \quad g_m = 40(100 \times 10^{-6}) = 4.00 \text{ mS}$$

$$r_p = \frac{100(0.25)}{10^{-4}} = 25 \text{ k}\Omega \quad | \quad r_{po} = 500 \Omega \parallel 25 \text{ k}\Omega = 490 \Omega$$

$$f_H = \frac{1}{2p[(490 \Omega)(5.37 + 2) \text{ pF} + (500 + 75 \text{ k}\Omega) 1 \text{ pF}]} = 2.01 \text{ MHz}$$

$$(b) C_m = 1 \text{ pF} \quad | \quad C_p = \frac{40(1 \times 10^{-3})}{2p(100 \times 10^6)} - 1 \text{ pF} = 62.7 \text{ pF} \quad | \quad r_x = 500 \Omega \quad | \quad g_m = 40(1 \times 10^{-4}) = 40.0 \text{ mS}$$

$$r_p = \frac{100(0.25)}{10^{-3}} = 2.5 \text{ k}\Omega \quad | \quad r_{po} = 500 \Omega \parallel 2.5 \text{ k}\Omega = 417 \Omega$$

$$f_H = \frac{1}{2p[(417 \Omega)(62.7 + 2) \text{ pF} + (500 + 7.5 \text{ k}\Omega) 1 \text{ pF}]} = 4.55 \text{ MHz}$$

17.84

For A_{mid} , refer to Section 15.1.1 : $R_1 = 39k\Omega$, $R_2 = 11k\Omega$, $R_{E21} = 800\Omega$, $R_{C2} = 2.35k\Omega$

$$r_{p2} = \frac{2.39k\Omega}{2} = 1.40k\Omega \quad | \quad R_{i1} = 620\Omega \parallel 39k\Omega \parallel 11k\Omega = 578\Omega \quad | \quad A_{v1} = -10mS(578\Omega \parallel 1.20k\Omega) = -3.91$$

$$R_{i2} = 2.35k\Omega \parallel 51.8k\Omega = 2.25k\Omega \quad | \quad A_{v2} = -62.8mS(2.25k\Omega \parallel 19.8k\Omega) = -127 \quad | \quad A_{v3} \text{ doesn't change}$$

$$A_v = \frac{1M\Omega}{1.01M\Omega}(-3.91)(-127)(0.95) = +467 \text{ or } 53.4 \text{ dB}$$

For f_L , refer to Section 17.9.3

$$R_{3S} = (620\Omega \parallel 12.2k\Omega) + \left(\frac{17.2k\Omega}{2} \parallel \frac{2.39k\Omega}{2} \right) = 1.64k\Omega \quad | \quad R_{th} = \frac{17.2k\Omega}{2} \parallel 620\Omega \parallel 12.2k\Omega = 552\Omega$$

$$R_{4S} = 750\Omega \parallel \frac{552 + 1195}{151} = 11.4\Omega \quad | \quad R_{5S} = \left(\frac{R_{C2}}{2} \parallel \frac{r_{o2}}{2} \right) + (R_{B3} \parallel R_{in3}) = 16.3k\Omega$$

$$R_{th3} = 51.8k\Omega \parallel 2.35k\Omega \parallel 27.1k\Omega = 2.08k\Omega \quad | \quad R_{6S} = 250 + 3.3k\Omega \parallel \frac{2.08k\Omega + 1.00k\Omega}{81} = 288\Omega$$

$$f_L = \frac{1}{2p}(99 + 319 + 610 + 3987 + 61.4 + 158) = 833 \text{ Hz}$$

For f_H , refer to Section 17.9.3

$$R_{L1} = 598\Omega \parallel \frac{2.39k\Omega}{2} = 399\Omega \quad | \quad R_{th}C_{T1} = (9.9k\Omega) \left[5pF + 1pF \left(1 + 0.01S(399\Omega) + \frac{399\Omega}{9900\Omega} \right) \right] = 9.92 \times 10^{-8} s$$

$$R_{th2} = 598\Omega \parallel \frac{12.2k\Omega}{2} = 544\Omega \quad | \quad r_{p2} = R_{4S} = \frac{2.39k\Omega}{2} \parallel (544\Omega + 250\Omega) = 596\Omega$$

$$R_{L2} = 51.8k\Omega \parallel \frac{4.7k\Omega}{2} \parallel R_{in2} = 2.25k\Omega \parallel 19.8k\Omega = 2.02k\Omega$$

$$C_p + C_m = \frac{g_m}{w_T} \propto I_C \rightarrow C_{p2} = 2(40pF) - 1pF = 79pF$$

$$r_{p2}C_{T2} = (544) \left[79pF + 1pF \left(1 + 136mS(2.02k\Omega) + \frac{2.02k\Omega}{0.544k\Omega} \right) \right] = 1.95 \times 10^{-7} s$$

$$R_{th3} = \frac{54.2k\Omega}{2} \parallel \frac{4.7k\Omega}{2} \parallel 51.8k\Omega = 2.08k\Omega$$

$$\frac{2.08k\Omega + 250\Omega}{1 + 79.6mS(0.232k)} 50pF + (2.08k\Omega + 250\Omega)1pF = 8.31 \times 10^{-9} s$$

$$f_H = \frac{1}{2p(9.92 \times 10^{-8} s + 1.95 \times 10^{-7} s + 8.31 \times 10^{-9} s)} = 526 \text{ kHz}$$

17.85

For A_{mid} , refer to Section 15.1.1 : $R_{B3} = 2(51.8k\Omega) = 104k\Omega$, $R_{E3} = 6.6k\Omega$, $r_{p3} = \frac{1k\Omega}{2} = 500\Omega$

$$A_{v1} = \text{doesn't change} \quad | \quad R_{L2} = 4.7k\Omega \parallel 104k\Omega \parallel [500\Omega + 81(6.6k\Omega \parallel 250\Omega)] = 3.67k\Omega$$

$$A_{v12} = -62.8mS(3.67k\Omega) = -231 \quad | \quad A_{v13} = \frac{81(241)}{500 + 81(241)} = 0.975$$

$$A_v = \frac{1M\Omega}{1.01M\Omega}(-4.78)(-231)(0.975) = +1070 \quad \text{or} \quad 60.6 \text{ dB}$$

For f_L , refer to Section 17.9.3

$$R_{S5} = (4.7k\Omega \parallel 54.2k\Omega) + 104k\Omega \parallel [500\Omega + 81(6.6k\Omega \parallel 250\Omega)] = 21.1k\Omega$$

$$R_{th3} = 104k\Omega \parallel 4.7k\Omega \parallel 54.2k\Omega = 4.15k\Omega \quad | \quad R_{6S} = 250 + 6.6k\Omega \parallel \frac{4.15k\Omega + 0.5k\Omega}{81} = 307\Omega$$

$$f_L = \frac{1}{2p} \left(99 + 319 + 372 + 2340 + \frac{1}{21.1k\Omega(1mF)} + \frac{1}{307\Omega(22mF)} \right) = 529 \text{ Hz}$$

For f_H , refer to Section 17.9.3

$$R_{L2} = 54.2k\Omega \parallel 4.7k\Omega \parallel 104k\Omega \parallel [500\Omega + 81(6.6k\Omega \parallel 250\Omega)] = 3.44k\Omega$$

$$R_{po2}C_{T2} = (610\Omega) \left[39pF + 1pF \left(1 + 67.8mS(3.44k\Omega) + \frac{3.44k\Omega}{0.610k\Omega} \right) \right] = 1.70 \times 10^{-7} s$$

$$C_p + C_m = \frac{g_m}{w_T} \propto I_C \rightarrow C_{p3} = 2(51pF) - 1pF = 101pF \quad | \quad R_{th3} = 104k\Omega \parallel 4.7k\Omega \parallel 54.2k\Omega = 4.15k\Omega$$

$$\frac{4.15k\Omega + 250\Omega}{1 + 159.4mS(0.241k)} 101pF + (4.15k\Omega + 250\Omega)1pF = 1.57 \times 10^{-8} s$$

$$f_H = \frac{1}{2p(1.07 \times 10^{-7} s + 1.70 \times 10^{-7} s + 1.57 \times 10^{-8} s)} = 544 \text{ kHz}$$

17.86

$$A_v = -100 (40dB) \quad | \quad f_H = 5 \times 10^6 \text{ Hz} \quad | \quad f_T \geq 2(100)(5 \times 10^6) = 1.00 \text{ GHz}$$

$$GBW \leq \frac{1}{r_x C_m} \quad | \quad r_x C_m \leq \frac{1}{2p(10^9 \text{ Hz})} = 159 \text{ ps}$$

17.87

$$A_v = 100 (40dB) \quad | \quad f_H = 20 \times 10^6 \text{ Hz} \quad | \quad f_T \geq 2(100)(2 \times 10^7) = 4.00 \text{ GHz}$$

$$GBW \leq \frac{1}{r_x C_m} \quad | \quad r_x C_m \leq \frac{1}{2p(4 \times 10^9 \text{ Hz})} = 39.8 \text{ ps}$$


17.88

$$w_H \cong \frac{1}{\left(R_I \parallel \frac{1}{g_m}\right) C_{GS} + R_L C_{GD}} \quad | \quad A_{mid} = \frac{R_{in}}{R_I + R_{in}} g_m R_L \cong \frac{g_m R_L}{1 + g_m R_I} \quad | \quad R_L = A_{mid} \left(\frac{1}{g_m} + R_I \right) = 20 \left(\frac{1}{g_m} + 100 \right)$$

$$2p(25 \times 10^6) = \frac{1}{\left[\frac{100 \Omega}{1 + g_m(100 \Omega)} \right] 10^{-11} F + 20 \left(\frac{1}{g_m} + 100 \Omega \right) 3 \times 10^{-12} F} \rightarrow g_m = 190 mS$$

$$R_L = 20 \left(\frac{1}{0.190} + 100 \right) = 2.11 k\Omega \quad | \quad I_D = \frac{g_m^2}{2K_n} = \frac{(190 mS)^2}{2 \left(25 \frac{mS}{V} \right)} = 722 \mu A$$

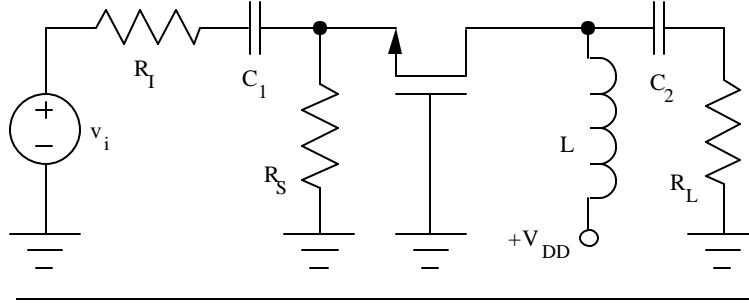Note that we cannot supply I_D through R_L since $I_D R_L = 1520 V > V_{DD}$.



17.89

$$A_{mid} = g_m R_L \quad | \quad g_m = \frac{100}{100 k\Omega} = 1.00 mS \quad | \quad r_p = \frac{b_o}{g_m} \cong \frac{100}{1.00 mS} = 100 k\Omega$$

$$\text{Assume } r_p \gg r_x \quad | \quad r_{po} = r_p \parallel r_x \cong r_x$$

$$w_H = \frac{1}{r_x \left[C_p + C_m \left(1 + g_m R_L + \frac{R_L}{r_x} \right) \right]} \cong \frac{1}{r_x C_m \left(1 + g_m R_L + \frac{R_L}{r_x} \right)} = \frac{1}{r_x C_m (1 + g_m R_L) + R_L C_m}$$

$$r_x C_m (1 + g_m R_L) + R_L C_m = \frac{1}{w_H} \quad | \quad r_x C_m (1 + 100) + 10^5 C_m = \frac{1}{2p(10^6)} = 1.59 \times 10^{-7}$$

$$C_m = \frac{1.59 pF}{1 + 1.01 \times 10^{-3} r_x} \quad | \quad C_m \text{ cannot exceed } 1.59 pF \text{ for an ideal transistor with } r_x = 0.$$

Other more realistic possibilities (C_u, r_x) : (1pF, 584Ω) (0.75pF, 1.11kΩ) (0.5pF, 2.16kΩ)

17.90

$$w_H = \frac{1}{R_{th} \left[C_{GS} + C_{GD} \left[1 + g_m R_L + \frac{R_L}{R_{th}} \right] \right]} = \frac{1}{100 \left[15 pF + 5 pF \left[1 + g_m R_L + \frac{R_L}{100} \right] \right]}$$

$$2p(25 \times 10^6) = \frac{1}{100 \left[20 pF + 5 pF \left[g_m R_L + \frac{R_L}{100} \right] \right]} \quad | \quad g_m R_L + \frac{R_L}{100} = \left[\frac{1}{2p(25 \times 10^6)(100)10^{-12}} - 20 \right] \frac{1}{5}$$

$$g_m = \frac{8.73}{R_L} - 0.01 \rightarrow R_L \leq 873 \Omega \quad | \quad I_D = \frac{g_m^2}{2K_n} = \frac{g_m^2}{0.05} = 20g_m^2$$

For strong inversion (for the square-law model to be valid), we desire

$$(V_{GS} - V_{TN}) \geq 0.25V \rightarrow I_D \geq \frac{0.025}{2} (0.25)^2 = 781 \text{ } \mu\text{A}.$$


We normally would like $g_m R_L$ to be as large as possible, so set $I_D = 781 \text{ } \mu\text{A}$.

$$g_m = \sqrt{2K_n I_D} = \sqrt{2(0.025)(7.81 \times 10^{-4})} = 6.25 \text{ mS} \quad | \quad R_L = \frac{8.73}{g_m - 0.01} = 537 \Omega \quad | \quad g_m R_L = 3.36$$

17.91

$$f_H \leq \frac{1}{2pR_L C_m} = \frac{1}{2p(12k\Omega \| 47k\Omega)(2pF)} \rightarrow f_H \leq 8.33 \text{ MHz}$$

17.92

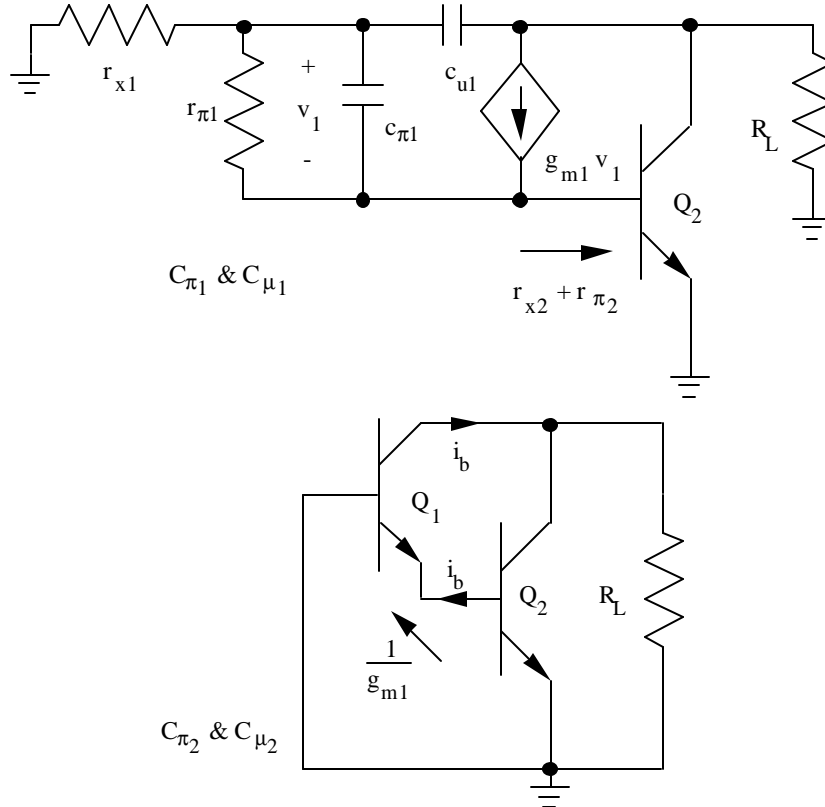

$$(a) R_{m1O} : v_x \cong i_x r_{x1} - i_x r_{x1} \left[\frac{(b_o + 1)(r_{x2} + r_{p2})}{r_{p1} + (b_o + 1)(r_{x2} + r_{p2})} \right] - \frac{b_o}{r_{x2} + r_{p2}} R_L \Big) - (-i_x R_L)$$

$$R_{m1O} \cong i_x \left[R_L + r_{x1} \left(1 + \frac{b_o r_{p2}}{r_{p1} + b_o r_{p2}} g_{m2} R_L \right) \right] \text{ assuming } r_{x2} \ll r_{p2}.$$

$$r_{p1} \cong 10r_{p2} \quad | \quad b_o = 100 \quad | \quad g_{m1} \cong \frac{b_o}{r_{p1}} = \frac{10}{r_{p2}} \quad | \quad R_{m1O} = \frac{v_x}{i_x} = R_L + r_{x1} \left(1 + \frac{10}{11} g_{m2} R_L \right)$$

R_{p1O} : Split i_x and use superposition with $r_{x2} \ll r_{p2}$:

$$v_x \cong i_x r_{x1} \left[1 - \frac{(b_o + 1)(r_{x2} + r_{p2})}{r_{p1} + (b_o + 1)(r_{x2} + r_{p2})} \right] + \frac{i_x}{g_{p2} + g_{m1}} \cong i_x r_{x1} \frac{r_{p1}}{r_{p1} + b_o r_{p2}} + \frac{i_x}{g_{p2} + 10g_{p2}}$$

$$R_{p1O} = \frac{v_x}{i_x} \cong \frac{10r_{x1} + r_{p2}}{11}$$

R_{p2O} : The circuit is the same as that used for the C_T calculation.

$$R_{p2O} = r_{p2} \left\| \left(r_{x2} + \frac{1}{g_{m1}} \right) \right\| = r_{p2} \left\| \left(r_{x2} + \frac{r_{p2}}{10} \right) \right\|$$

R_{m2O} : The circuit is the same as that used for the C_T calculation except the additional $i_b = i_x/2$ is returned back to the output :

$$R_{m2O} = R_{p2O} + R_{p2O} g_{m2} R_L + \frac{R_L}{2} = R_{p2O} \left(1 + g_{m2} R_L + \frac{R_L}{2R_{p2O}} \right)$$

$$W_H = \frac{1}{C_{p1} \left(\frac{10r_{x1} + r_{p2}}{11} \right) + C_{m1} r_{x1} \left(1 + \frac{10}{11} g_{m2} R_L + \frac{R_L}{r_{x1}} \right) + R_{p2O} \left[C_{p2} + C_{m2} \left(1 + g_{m2} R_L + \frac{R_L}{2R_{p2O}} \right) \right]}$$

$$r_{p2} = \frac{100(0.025V)}{1mA} = 2.50k\Omega \quad | \quad \text{Use } R_L = \frac{r_{o2}}{2} = \frac{50V}{2mA} = 25.0k\Omega$$

$$C_{p1} = \frac{40(10^{-4})}{6 \times 10^8 p} - 0.5pF = 1.62pF \quad | \quad C_{p2} = \frac{40(10^{-3})}{6 \times 10^8 p} - 0.5pF = 20.7pF$$

$$R_{p2O} = r_{p2} \left\| \left(r_{x2} + \frac{r_{p2}}{10} \right) \right\| = 2.50k\Omega \left\| \left(300 + \frac{2.50k\Omega}{10} \right) \right\| = 451\Omega$$

$$f_H = \frac{1}{2p} \left\{ \frac{1.62pF \left(\frac{3k\Omega + 2.5k\Omega}{11} \right) + 0.5pF \left(300\Omega \left[1 + 40mS(25k\Omega) + \frac{25k\Omega}{300\Omega} \right] \right)}{+451\Omega \left[20.7pF + 0.5pF \left(1 + 40mS(25k\Omega) + \frac{25k\Omega}{902\Omega} \right) \right]} \right\}^{-1} = 393 \text{ kHz}$$

(b) The circuit is almost the same except for two important changes : C_{m1} sees only r_{x1} , and the $i_b = i_x/2$ is not returned to the output for C_{m2} .

$$w_H = \frac{1}{C_{p1} \frac{10r_{x1} + r_{p2}}{11} + C_{m1} r_{x1} + R_{p2o} \left[C_{p2} + C_{m2} \left(1 + g_{m2} R_L + \frac{R_L}{R_{p2o}} \right) \right]}$$

$$f_H = \frac{1}{2\pi} \left\{ \frac{1.62 pF \left(\frac{3k\Omega + 2.5k\Omega}{11} \right) + 0.5 pF (300\Omega)}{+451\Omega \left[20.7 pF + 0.5 pF \left(1 + 40mS(25k\Omega) + \frac{25k\Omega}{451\Omega} \right) \right]} \right\}^{-1} = 640 kHz$$


(c) The C - C/C - E cascade offers significantly better bandwidth than the Darlington configuration because C_{m1} is not subject to Miller multiplication.

(d) Improved bandwidth is one reason for the use of the C - C/C - E cascade in the 741 op - amp.

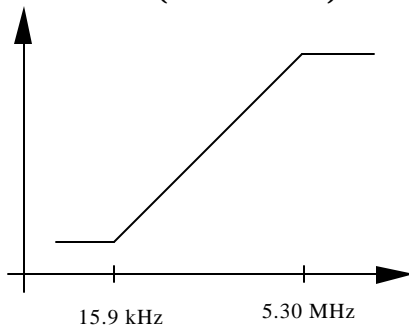17.93 Use $R_C = 100 k\Omega$

$$f_z = \frac{1}{2\pi R_{EE} C_{EE}} = \frac{1}{2\pi (10^7 \Omega)(1 pF)} = 15.9 kHz$$

$$f_p \cong \frac{1}{2\pi (r_x + R_C) C_m} = \frac{1}{2\pi (175\Omega + 10^5 \Omega)(0.3 pF)} = 5.30 MHz$$



17.94

*Problem 17.94 - Bipolar Differential Amplifier CMRR

VIC 1 0 AC 5M

RX 1 2 175

RPI 2 3 25K

CPI 2 3 2.88PF

CU 2 4 0.3PF

GM 4 3 2 3 4MS

RO 4 3 500K

REE 3 0 10MEG

CEE 3 0 1PF

RL 4 0 100K

.AC DEC 100 10 20MEG

.PRINT AC VM(4) VP(4)

.PROBE
.END

The results agree with the drawing in Problem 17.93

17.95

$$(a) f_T = \frac{g_{m1}}{2pC_c} = \frac{\sqrt{2(0.001)(125 \times 10^{-6})}}{2p(7.5 \times 10^{-12})} = 10.6 \text{ MHz} \quad | \quad \text{Since } I_2 > I_1, \text{ the slew rate}$$

is approximately symmetrical. $| \quad SR = \frac{I_1}{C_c} = \frac{250 \times 10^{-6}}{7.5 \times 10^{-12}} = 33.3 \times 10^6 \frac{V}{s} = 33.3 \frac{V}{ms}$

$$(b) f_T = \frac{g_{m1}}{2pC_c} = \frac{\sqrt{2(0.001)(250 \times 10^{-6})}}{2p(10^{-11})} = 11.3 \text{ MHz} \quad | \quad \text{Since } I_2 > I_1, \text{ the slew rate}$$

is asymmetrical. $| \quad SR_+ = \frac{I_1}{C_c} = \frac{500 \mu A}{10 \text{ pF}} = 50 \frac{V}{ms} \quad | \quad SR_- = \frac{250 \mu A}{10 \text{ pF}} = 25 \frac{V}{ms}$

17.96

$$f_T = \frac{g_{m1}}{2pC_c} = \frac{\sqrt{2(0.001)(250 \times 10^{-6})}}{2p(10^{-11})} = 11.3 \text{ MHz} \quad | \quad \text{Since } I_2 > I_1, \text{ the slew rate}$$

is symmetrical. $| \quad SR = \frac{I_1}{C_c} = \frac{500 \times 10^{-6}}{10^{-11}} = 50 \times 10^6 \frac{V}{s} = 50 \frac{V}{ms}$

17.97

```
*Problem 17.97 - CMOS Op-amp
VDD 8 0 DC 10
VSS 9 0 -10
I1 1 9 250U
I2 6 9 500U
I3 7 9 2M
V1 4 0 DC -2.23M AC 0.5
V2 2 0 AC -0.5
M1 3 2 1 1 NFET W=20U L=1U
M2 5 4 1 1 NFET W=20U L=1U
M3 3 3 8 8 PFET W=40U L=1U
M4 5 3 8 8 PFET W=40U L=1U
M5 6 5 8 8 PFET W=160U L=1U
M6 8 6 7 7 NFET W=60U L=1U
CC 5 6 7.5PF
*CC 5 10 7.5PF
*RZ 10 6 1K
.MODEL NFET NMOS KP=2.5E-5 VTO=0.70 GAMMA=0.5
+LAMBDA=0.05 TOX=20N
+CGSO=4E-9 CGDO=4E-9 CJ=2.0E-4 CJSW=5.0E-10
.MODEL PFET PMOS KP=1.0E-5 VTO=-0.70 GAMMA=0.75
+LAMBDA=0.05 TOX=20N
+CGSO=4E-9 CGDO=4E-9 CJ=2.0E-4 CJSW=5.0E-10
.OP
.TF V(7) V1
.AC DEC 100 1 20MEG
.PRINT AC VM(7) VP(7)
```

.PROBE
.END

Results: 8.1 MHz, -110 degrees; 8.0 MHz, -92 degrees

17.98

$$(a) f_T = \frac{g_m}{2pC_C} = \frac{40I_{C1}}{2pC_C} \quad | \quad I_{C1} = \frac{I_1}{2} \quad | \quad f_T = \frac{40(25mA)}{2p(12pF)} = 13.3 \text{ MHz}$$

$$SR = \frac{I_1}{C_C} = \frac{25mA}{12pF} = 2.09 \frac{MV}{s} = 2.09 \frac{V}{ms} \text{ since } I_2 > I_1. \text{ The slew rate is symmetrical.}$$

$$(b) f_T = \frac{40(100mA)}{2p(12pF)} = 53.1 \text{ MHz} \quad | \quad SR = \frac{I_1}{C_C} = \frac{100mA}{12pF} = 8.33 \frac{MV}{s} = 8.33 \frac{V}{ms}$$

17.99

$$f_T = \frac{g_m}{2pC_C} = \frac{40I_{C1}}{2pC_C} \quad | \quad I_{C1} = \frac{I_1}{2} \quad | \quad f_T = \frac{40(250mA)}{2p(10pF)} = 159 \text{ MHz}$$

$$SR = \frac{I_1}{C_C} = \frac{500mA}{10pF} = 50 \frac{MV}{s} = 50 \frac{V}{ms} \text{ since } I_2 > I_1. \text{ The slew rate is symmetrical.}$$

17.100

$$SR = \frac{I_1}{C_C} = \frac{40mA}{5pF} = 8 \times 10^6 \frac{V}{s} = 8 \frac{V}{ms}$$

*Problems 17.100 - Bipolar Op-amp

VCC 8 0 DC 10

VEE 9 0 -10

I1 1 9 40U

I2 6 9 400U

I3 7 9 500U

V1 4 0 DC 0 PWL (0 0 5U 0 5.1U 5 10U 5 10.2U -5 15U -5 15.2U 5 20U 5)

VF 2 7 DC -0.0045

Q1 3 2 1 NBJT

Q2 5 4 1 NBJT

Q3 3 10 8 PBJT

Q4 5 10 8 PBJT

Q11 0 3 10 PBJT

Q5 6 5 8 PBJT

Q6 8 6 7 NBJT

CC 5 6 5PF

.MODEL NBJT NPN BF=100 IS=1FA VAF=80 RB=250 TF=0.65NS CJC=2PF

.MODEL PBJT PNP BF=100 IS=1FA VAF=80 RB=250 TF=0.65NS CJC=2PF

.OP

.TRAN .05U 20U

.PROBE V(4) V(5) V(6) V(7)

.END

Results: -8V/μs, +6V/μs

17.101

$$SR = \frac{I_1}{C_C} = \frac{100mA}{8pF} = 12.5 \times 10^6 \frac{V}{s} = 12.5 \frac{V}{ms}$$

17.102

$$f_T = \frac{g_m}{2pC_C} = \frac{40I_{C1}}{2pC_C} \quad | \quad I_{C1} = \frac{I_1}{2} \quad | \quad f_T = \frac{40(50mA)}{2p(15pF)} = 21.2 \text{ MHz}$$

*Problem 17.101 - Bipolar Op-amp

VCC 8 0 DC 10

VEE 9 0 -10

I1 1 9 100U

I2 6 9 500U

I3 7 9 500U

V1 4 0 DC 2.10M AC 0.5

V2 2 0 DC 0 AC -0.5

Q1 3 2 1 NBJT

Q2 5 4 1 NBJT

Q3 3 10 8 PBJT

Q4 5 10 8 PBJT

Q11 0 3 10 PBJT

Q5 6 5 8 PBJT

Q6 8 6 7 NBJT

CC 5 6 15PF

.MODEL NBJT NPN BF=100 IS=1FA VAF=80 RB=250 TF=0.65NS CJC=2PF

.MODEL PBJT PNP BF=100 IS=1FA VAF=80 RB=250 TF=0.65NS CJC=2PF

.OP

.TF V(7) V1

.AC DEC 100 1 20MEG

.PRINT AC VM(7) VP(7)

.PROBE

.END

Spice Results: (a) 16.2MHz (b) 16.3 MHz - 15 pF does not represent the effective value of C_C .

17.103

Zero output voltage occurs when the current through the base - collector admittance is exactly equal to the current in the controlled source :

$$g_m v = sC_{GD}v + \frac{v}{R_Z + \frac{1}{sC_C}} \quad | \quad sC_{GD} - g_m + \frac{sC_C}{sC_C R_Z + 1} = 0$$

The numerator polynomial becomes : $s^2 C_{GD} C_C R_Z + s(C_{GD} + C_C - C_C R_Z g_m) - g_m = 0$

For widely spaced roots, $z_1 \cong \frac{g_m}{C_{GD} + C_C - C_C R_Z g_m}$

z_1 can be eliminated by setting : $R_Z = \frac{1}{g_m} \left(1 + \frac{C_{GD}}{C_C} \right)$

17.104

$$f_o = \frac{1}{2\pi\sqrt{LC_{GD}}} = \frac{1}{2\pi\sqrt{10^{-5}(5 \times 10^{-12})}} = 22.5 \text{ MHz}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TN}} = \frac{0.02}{2} = 0.01 \text{ S} \quad r_o = \frac{\frac{1}{0.0167} + 10}{0.01} = 59.9 \text{ k}\Omega$$

$$A_v = -g_m(r_o \parallel R_L) = -0.01 \text{ S}(59.9 \text{ k}\Omega \parallel 10 \text{ k}\Omega) = -85.7$$

$$BW = \frac{1}{2\pi R_p C_{GD}} = \frac{1}{2\pi(8.57 \text{ k}\Omega)(5 \text{ pF})} = 3.71 \text{ MHz} \quad Q = \frac{22.5}{3.71} = 6.06$$

17.105

$$(a) f_o = \frac{1}{2\pi\sqrt{(C + C_m)L}} \rightarrow C = \frac{1}{(2\pi f_o)^2 L} - C_m = \frac{1}{[2\pi(10.7 \times 10^6 \text{ Hz})]^2 10^{-5} \text{ H}} - 2 \text{ pF} = 20.1 \text{ pF}$$

$$(b) r_o = \frac{75 \text{ V} + 10 \text{ V}}{10 \text{ mA}} = 8.50 \text{ k}\Omega \quad | \quad BW = \frac{1}{2\pi(8.5 \text{ k}\Omega)(22.1 \text{ pF})} = 847 \text{ kHz} \quad | \quad Q = \frac{10.7}{0.847} = 12.6$$

$$(c) Q = 100 \quad | \quad BW = \frac{f_o}{Q} = 107 \text{ kHz} \quad | \quad r_o = \frac{1}{w_o(C + C_m)} = \frac{1}{2\pi(107 \text{ kHz})(22.1 \text{ pF})} = 67.3 \text{ k}\Omega$$

$$n^2 = \frac{67.3 \text{ k}\Omega}{8.50 \text{ k}\Omega} = 7.918 \quad | \quad n = 2.81$$


$$(d) C_m' = \frac{C_m}{n^2} = \frac{2 \text{ pF}}{7.918} = 0.253 \text{ pF} \quad | \quad C = 22.1 - 0.253 = 21.9 \text{ pF}$$

17.106

```

*Problem 17.106(a) - Double-Tuned Common-Source Amplifier
VDD 4 0 DC 15
VS 1 0 AC 12.65M
C1 1 2 25PF
L1 2 0 20UH
RG 2 0 100K
M1 3 2 0 0 NFET
CGS 2 0 25PF
L2 3 4 20UH
C2 3 4 50PF
RD 3 4 100K
.MODEL NFET NMOS VTO=-1 KP=20M LAMBDA=0.02
.OP
.AC LIN 500 4.5MEG 5.5MEG
.PRINT AC VM(2) VP(2) VM(3) VP(3)
.PROBE
.END

```

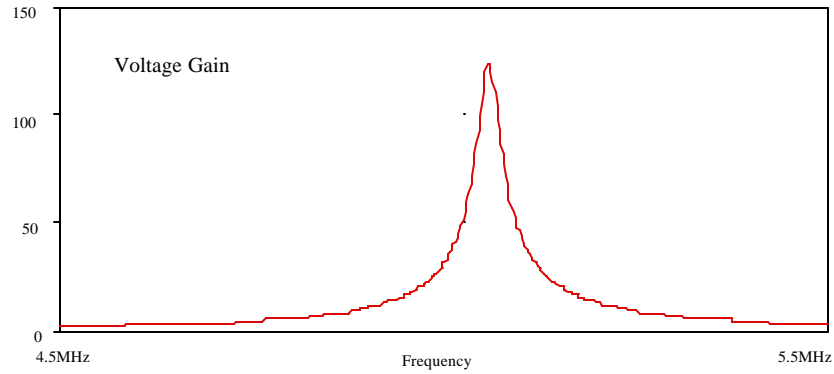

*Problem 17.106(b) - Double-Tuned Common-Source Amplifier

VDD 4 0 DC 15

VS 1 0 AC 12.65M

C1 1 2 25PF

L1 2 0 20UH

RG 2 0 100K

M1 3 2 0 0 NFET

CGS 2 0 25PF

CGD 2 3 1PF

L2 3 4 20UH

C2 3 4 50PF

RD 3 4 100K

.MODEL NFET NMOS VTO=-1 KP=20M LAMBDA=0.02


.OP

.AC LIN 500 1MEG 10MEG

.PRINT AC VM(2) VP(2) VM(3) VP(3)

.PROBE

.END

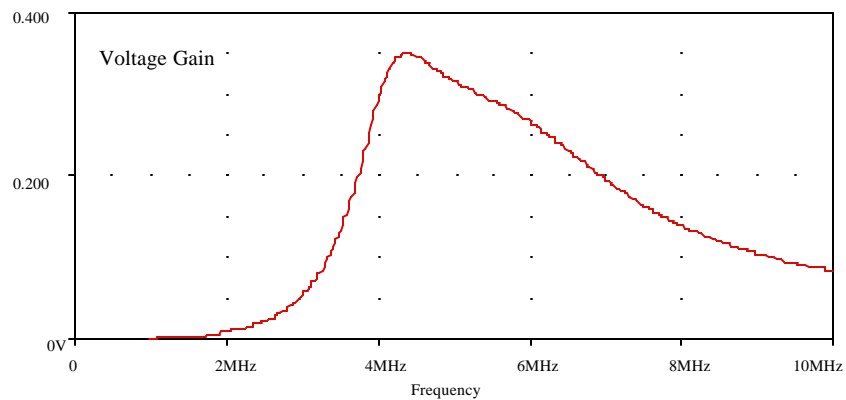

Note that the synchronous tuning and gain are ruined by the Miller multiplication of C_{GD} .

In fact, the circuit is now an oscillator!

Define : $C_3 = C_1 + C_{GS}$

$$\begin{bmatrix} sC_1V_i \\ 0 \end{bmatrix} = \begin{bmatrix} s(C_3 + C_{GD}) + G_G + \frac{1}{sL_1} & -sC_{GD} \\ s(sC_{GD} - g_m) & s(C_2 + C_{GD}) + G_L + \frac{1}{sL_2} \end{bmatrix} \begin{bmatrix} V_{gs} \\ V_o \end{bmatrix}$$

$$\Delta(s) = s^4 [C_2C_3 + (C_2 + C_3)C_{GD}] + s^3 [(C_3 + C_{GD})G_L + (C_2 + C_{GD})G_G + g_m C_{GD}] + s^2 \left[G_G G_L + \frac{(C_3 + C_{GD})}{L_2} + \frac{(C_2 + C_{GD})}{L_1} \right] + s \left[\frac{G_G}{L_2} + \frac{G_L}{L_1} \right] + \frac{1}{L_1 L_2}$$

$$I_D = \frac{0.02}{2} (0+1)^2 [1 + 0.02(15)] = 13.0 \text{ mA} \quad | \quad g_m = \frac{2(.013)}{1} = 26.0 \text{ mS} \quad | \quad r_o = \frac{50+15}{.013} = 5.00 \text{ k}\Omega$$


$$G_L = \frac{1}{5\text{k}\Omega \parallel 100\text{k}\Omega} = 0.210 \text{ mS} \quad | \quad \frac{V_o}{V_i} = \frac{s^2 C_1 (sC_{GD} - g_m)}{\Delta(s)}$$

$$\Delta(s) = 2.60 \times 10^{-21} s^4 + 3.72 \times 10^{-14} s^3 + 5.10 \times 10^{-6} s^2 + 11.00 s + 2.5 \times 10^9$$

Using the roots function in MATLAB : $(-1.06 \pm j3.74) \times 10^7 \text{ rad/s}, (+0.318 \pm j2.55) \times 10^7 \text{ rad/s}$

The positive real parts indicate that the circuit will oscillate!

17.107

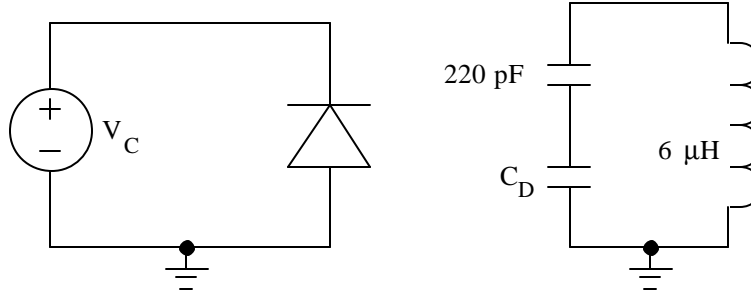


$$C_D = \frac{20 \text{ pF}}{\sqrt{1 + \frac{V_C}{0.9}}} \quad (a) \quad C_D = \frac{20 \text{ pF}}{\sqrt{1 + \frac{0}{0.9}}} = 20 \text{ pF} \quad | \quad C = \frac{20(220)}{20 + 220} \text{ pF} = 18.3 \text{ pF}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(6 \text{ mH})(18.3 \text{ pF})}} = 15.2 \text{ MHz}$$

$$(b) \quad C_D = \frac{20 \text{ pF}}{\sqrt{1 + \frac{10}{0.9}}} = 5.75 \text{ pF} \quad | \quad C = \frac{5.75(220)}{5.75 + 220} \text{ pF} = 5.60 \text{ pF}$$

$$f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{(6 \text{ mH})(5.60 \text{ pF})}} = 27.5 \text{ MHz}$$

17.108 (a)

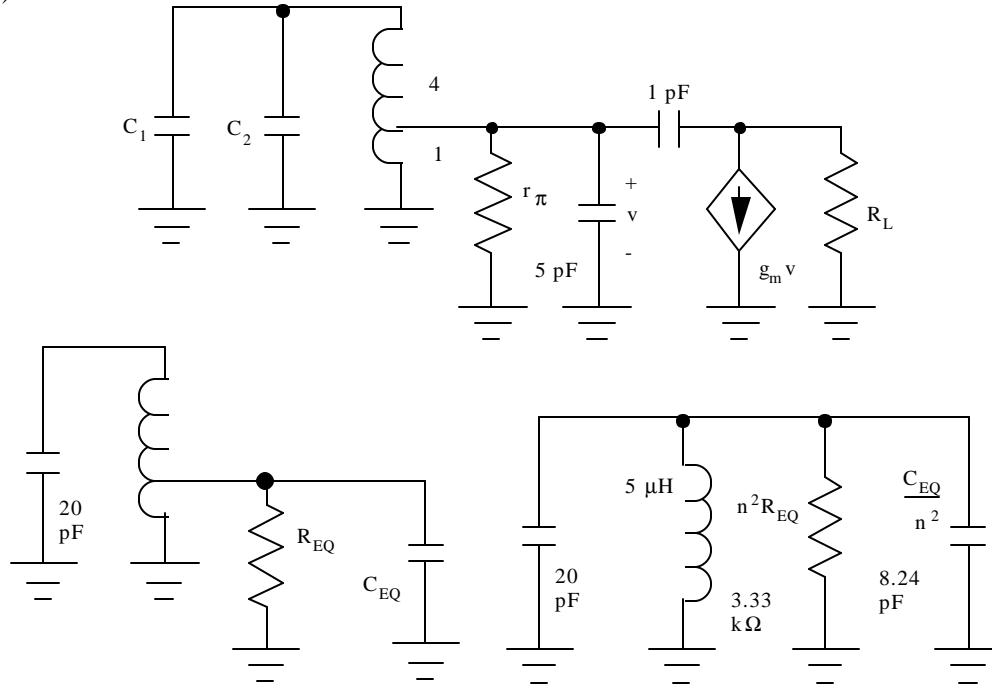


$$C_{EQ} = C_p + C_m[1 + g_m R_L] = 5 \text{ pF} + 1 \text{ pF} [1 + 40(1 \text{ mA})(5 \text{ k}\Omega)] = 206 \text{ pF}$$

$$C_p = 20 \text{ pF} + \frac{C_{EQ}}{n^2} = 20 \text{ pF} + \frac{206 \text{ pF}}{5^2} = 28.2 \text{ pF} \quad | \quad f_o = \frac{1}{2\pi \sqrt{(5 \text{ mH})(28.2 \text{ pF})}} = 13.4 \text{ MHz}$$

$$R_{EQ} = r_p \left\| \frac{R_L}{(1 + g_m R_L)(w R_L C_m)^2} = 2.5 \text{ k}\Omega \right\| \frac{5000}{(1 + 200)[2\pi(13.4 \text{ MHz})(5 \text{ k}\Omega)(1 \text{ pF})]^2} = 2.5 \text{ k}\Omega \parallel 140 \Omega = 133 \Omega$$


$$R_p = n^2 R_{EQ} = 25(133 \Omega) = 3.33 \text{ k}\Omega \quad | \quad BW = \frac{1}{2\pi(3.33 \text{ k}\Omega)(28.2 \text{ pF})} = 1.70 \text{ MHz} \quad | \quad Q = \frac{13.4}{1.70} = 7.88$$

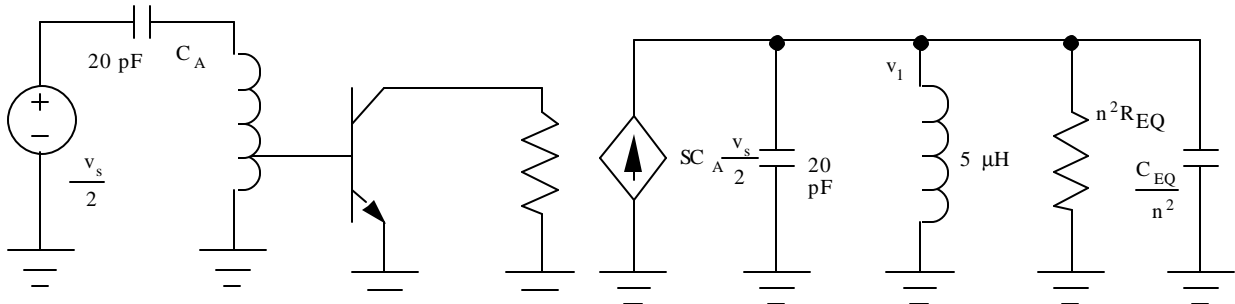Note the huge error that would be caused by using only r_π as the input resistance term.




$$v_i = j2\pi(13.4\text{MHz})(20\text{pF})\left(\frac{1}{2}\right)(3.33\text{k}\Omega)v_i = j2.80v_s$$

$$v_o = (-g_m R_L) \frac{j2.80v_s}{5} = -40(10^{-3})(5\text{k}\Omega)j0.560v_i \quad | \quad A_v = 112 \angle -90^\circ$$

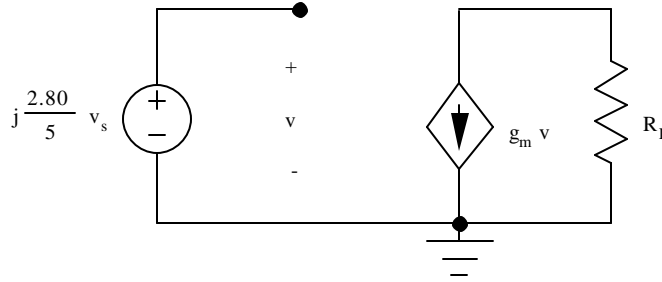

17.108 (b)

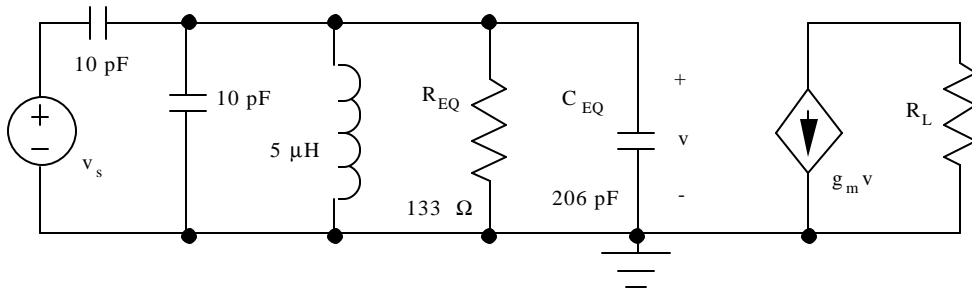

$$C_T = 5\text{pF} + 1\text{pF}[1 + 40(1\text{mA})(5\text{k}\Omega)] = 206\text{pF} \quad | \quad C_p = 20\text{pF} + 206\text{pF} = 226\text{pF}$$

$$f_o = \frac{1}{2\pi\sqrt{(5\text{mH})(226\text{pF})}} = 4.74\text{MHz}$$

$$R_{EQ} = r_p \left\| \frac{R_L}{(1 + g_m R_L)(\omega R_L C_m)^2} \right\| = 2.5\text{k}\Omega \left\| \frac{5000}{(1 + 200)[2\pi(4.74\text{MHz})(5\text{k}\Omega)(1\text{pF})]^2} \right\|$$

$$R_{EQ} = 2.5\text{k}\Omega \parallel 1.12\text{k}\Omega = 774\Omega \quad | \quad BW = \frac{1}{2\pi(774\Omega)(226\text{pF})} = 910\text{kHz} \quad | \quad Q = \frac{4.74}{0.910} = 5.21$$

$$v_o = j2\pi(4.74\text{MHz})(10\text{pF})(774\Omega)(-g_m R_L)v_i$$

$$v_o = j2\pi(4.74\text{MHz})(10\text{pF})(774\Omega)[-0.04\text{mS}(5\text{k}\Omega)]v_i \quad | \quad A_v = 46.1 \angle -90^\circ$$

17.109

$$(a) C_{EQ} = C_{GS1} + C_{GD1}(1 + g_{m1}R_L) = C_{GS1} + C_{GD1}\left(1 + \frac{g_{m1}}{g_{m2}}\right)$$

$$I_{D2} = I_{D1} = \frac{0.01}{2}[0 - (-1)]^2 = 5.00\text{mA} \quad | \quad V_{GS2} = -4 + \sqrt{\frac{2(0.005)}{0.01}} = -3\text{V}$$

$$V_{DS1} = V_{SG2} = +3\text{V} > 1\text{V} \rightarrow \text{Saturation region is ok.} \quad | \quad g_{m2} = g_{m1} = \sqrt{2(0.01)(0.005)} = 10.0\text{mS}$$

$$C_{EQ} = 20\text{pF} + 5\text{pF}[1 + 1] = 30\text{pF} \quad | \quad C_p = C_1 + C_{EQ} = 30\text{pF} + 20\text{pF} + 20\text{pF} = 70\text{pF}$$

$$\text{Require } C_2 + C_{GD} = C_p \rightarrow C_2 = 70\text{pF} - 5\text{pF} = 65\text{pF}$$

$$(b) f_o = \frac{1}{2p\sqrt{LC_p}} = \frac{1}{2p\sqrt{(10\text{mH})(70\text{pF})}} = 6.02 \text{ MHz} \quad | \quad R_{L1} = \frac{1}{g_{m2}}$$

$$R_p = R_G \left\| \frac{R_{L1}}{(1 + g_{m1}R_{L1})(wR_{L1}C_{GD1})^2} = 100\text{k}\Omega \right\| \frac{100}{(1+1)[2p(6.02\text{MHz})(100)(5\text{pF})]^2}$$

$$R_p = 100\text{k}\Omega \parallel 140\text{k}\Omega = 58.3\text{k}\Omega \quad | \quad BW_1 = \frac{1}{2pR_pC_p} = \frac{1}{2p(58.3\text{k}\Omega)(70\text{pF})} = 39.0\text{kHz}$$

$$BW_2 \cong BW_1 \sqrt{2^{\frac{1}{2}} - 1} = 25.1\text{kHz} \quad | \quad \text{Note that this is an approximation since } R_p = 100\text{k}\Omega$$

$$\text{at the output and } 58.3 \text{ k}\Omega \text{ at the input.} \quad | \quad Q = \frac{6.02 \text{ MHz}}{25.1\text{kHz}} = 240 \quad | \quad v_o = (wC_3v_i)(R_p)(-g_mR_D)$$

$$A_{mid} = 2p(6.02\text{MHz})(20\text{pF})(58.3\text{k}\Omega)(-10.0\text{mS})(100\text{k}\Omega) = 4.41 \times 10^4$$

17.110

*Problem 17.110 - Synchronously-Tuned Cascode Amplifier

VDD 5 0 DC 12

VS 1 0 AC 1

C3 1 2 20PF

L1 2 0 10UH

C1 2 0 20PF

RG 2 0 100K

M1 3 2 0 0 NFET1

CGS1 2 0 20PF

CGD1 2 3 5PF

M2 4 0 3 3 NFET2

CGS2 3 0 20PF

CGD2 4 3 5PF

L2 4 5 10UH

C2 4 5 65PF

RD 4 5 100K

.MODEL NFET1 NMOS VTO=-1 KP=10M

.MODEL NFET2 NMOS VTO=-4 KP=10M

.OP

.AC LIN 200 5.5MEG 6.5MEG

.PRINT AC VM(2) VP(2) VM(3) VP(3) VM(4) VP(4)

.PROBE

.END

Results: $A_{mid} = 279$, $f_o = 6.10 \text{ MHz}$, $Q = 24$

The amplifier is actually stagger-tuned. Note that the loop of capacitors around M_1 messes up the hand results based upon the C_{EQ} approximation. The C_{EQ} approximation itself may not be accurate enough for precise synchronous tuning. Plot a graph of V(2) and V(3) to show the problem. Evidence of the problem is also provided by the huge error in the mid-band gain.

17.111

From Prob. 17.109 : $C_{p2} = \frac{1}{(2pf_o)^2 L} = \frac{1}{\left(2p \frac{1.02}{\sqrt{LC_{p1}}}\right)^2 L} = \frac{C_{p1}}{(1.02)^2} = \frac{70pF}{(1.02)^2} = 67.3pF$

$$C_2 = C_{p2} - C_{GD2} = 67.3pF - 5pF = 62.3pF \quad | \quad R_{p2} = 100k\Omega$$

$$BW_1 = \frac{1}{2p(58.3k\Omega)(70pF)} = 39.0kHz \quad | \quad BW_2 = \frac{1}{2p(10^5\Omega)(67.3pF)} = 23.7kHz$$

$$BW \cong \frac{BW_1}{2} + 0.02f_{o1} + \frac{BW_2}{2} = \frac{39.0kHz}{2} + 0.02(6.02MHz) + \frac{23.7kHz}{2} = 152kHz$$

$$\text{The new } f_o \cong \frac{f_{o1} + 1.02f_o}{2} = 6.08MHz \quad | \quad Q = \frac{6.08MHz}{152kHz} = 40$$

17.112

*Problem 17.112 - Stagger-Tuned Cascode Amplifier

VDD 5 0 DC 12

VS 1 0 AC 1

C3 1 2 20PF

L1 2 0 10UH

C1 2 0 20PF

RG 2 0 100K

M1 3 2 0 0 NFET1

CGS1 2 0 20PF

CGD1 2 3 5PF

M2 4 0 3 3 NFET2

CGS2 3 0 20PF

CGD2 4 3 5PF

L2 4 5 10UH

C2 4 5 62.3PF

RD 4 5 100K

.MODEL NFET1 NMOS VTO=-1 KP=10M

.MODEL NFET2 NMOS VTO=-4 KP=10M

.OP


.AC LIN 200 5.5MEG 6.5MEG

.PRINT AC VM(2) VP(2) VM(3) VP(3) VM(4) VP(4)

.PROBE

.END

Results: $A_{mid} = 512$, $f_o = 6.19MHz$, $BW = 0.19MHz$, $Q = 33$

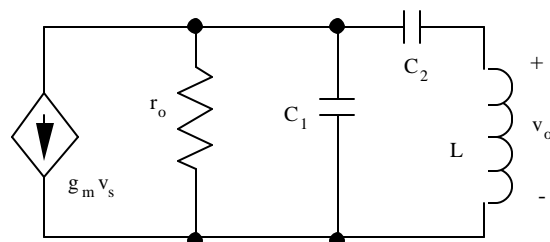17.113

$$(a) \begin{bmatrix} -g_m V_s \\ 0 \end{bmatrix} = \begin{bmatrix} s(C_1 + C_2) + g_o & -sC_2 \\ -sC_2 & sC_2 + \frac{1}{sL} \end{bmatrix} \begin{bmatrix} V_1 \\ V_o \end{bmatrix} \quad | \quad A_v(j\omega) = \frac{V_o}{V_s} = -\frac{j\omega C_2 g_m}{\Delta}$$

$$\Delta(s) = C_1 C_2 \left[s^2 + s \frac{g_o}{C_1} + \frac{g_o}{s C_1 C_2 L} + \frac{C_1 + C_2}{C_1 C_2} \frac{1}{L} \right]$$

$$\Delta(j\omega) = C_1 C_2 \left[\frac{C_1 + C_2}{C_1 C_2} \frac{1}{L} - \omega^2 + j\omega \frac{g_o}{C_1} + \frac{g_o}{j\omega C_1 C_2 L} \right] \quad | \quad \omega_o^2 = \frac{C_1 + C_2}{C_1 C_2} \frac{1}{L}$$

$$A_v(j\omega_o) = -\frac{\omega_o \frac{g_m}{C_1}}{\omega_o \frac{g_o}{C_1} - \frac{g_o}{\omega_o C_1 C_2 L}} = -\frac{g_m r_o}{1 - \frac{1}{\omega_o^2 L C_2}} = -\frac{m_f}{1 - \frac{C_1}{C_1 + C_2}} = -m_f \left(1 + \frac{C_1}{C_2} \right)$$

$$\text{Referring to Eqs. (17.192 - 17.193): } BW = \frac{\omega_o}{Q} = \frac{g_o}{C_1} - \frac{g_o}{\omega_o^2 C_1 C_2 L} = \frac{1}{r_o C_1} \left(1 - \frac{1}{\omega_o^2 L C_2} \right) = \frac{1}{r_o C_1 \left(1 + \frac{C_1}{C_2} \right)}$$

$$C_{EQ} = \frac{45(40)}{45 + 40} pF = 21.2 pF \quad | \quad f_o = \frac{1}{2\pi \sqrt{(10mH)(21.2pF)}} = 10.9 MHz$$

$$r_o = \frac{1}{0.02(20mA)} = 2.50 k\Omega \quad | \quad BW = \frac{1}{2\pi (2.50k\Omega)(45pF) \left(1 + \frac{45}{40} \right)} = 666 kHz$$

$$Q = \frac{10.9}{0.666} = 16.4 \quad | \quad A_{mid} = -m_f \left(1 + \frac{C_1}{C_2} \right) = -\sqrt{2(0.005)(0.02)(2500)} \left(1 + \frac{45pF}{40pF} \right) = -75.1$$

$$(b) f_o = \frac{1}{2\pi \sqrt{(10mH)(25pF)}} = 10.1 MHz \quad | \quad BW = \frac{1}{2\pi (2.5k\Omega)(25pF)} = 2.55 MHz$$

$$Q = \frac{10.1}{2.55} = 3.96 \quad | \quad A_{mid} = -g_m r_o = -m_f = -35.4$$

17.114

$$C_{EQ} = \frac{(C_1 + 5pF)C_2}{C_1 + 5pF + C_2} = 25 pF \quad | \quad C_2 = 50 pF \quad | \quad C_1 = 45 pF$$

$$f_o = \frac{1}{2\pi \sqrt{(10mH)(25pF)}} = 10.1 MHz \quad | \quad r_o = \frac{1}{0.02(20mA)} = 2.50 k\Omega$$

$$\text{Using the results from Prob. 17.113 : } BW = \frac{1}{2\pi (2.50k\Omega)(50pF) \left(1 + \frac{50pF}{50pF} \right)} = 635 kHz$$

$$Q = \frac{10.1}{0.635} = 15.9 \quad | \quad A_{mid} = -m_f \left(1 + \frac{C_1}{C_2} \right) = -\sqrt{2(0.005)(0.02)(2500)} \left(1 + \frac{50pF}{50pF} \right) = -70.7$$

17.115

*Problem 17.115(a) - Fig. P17.121(a)

```
VS 1 0 AC 1
CGD 1 2 5PF
GM 2 0 1 0 14.1MS
RO 2 0 2.5K
C1 2 0 40PF
C2 2 3 40PF
L1 3 0 10UH
.AC LIN 400 8MEG 12MEG
.PRINT AC VM(2) VP(2) VM(3) VP(3)
.PROBE V(2) V(3)
.END
```

Results: $A_{\text{mid}} = 75.1$, $f_o = 10.1$ MHz, BW = 670 kHz

*Problem 17.115(b) - Fig. P17.8121b)


```
VS 1 0 AC 1
CGD 1 2 5PF
GM 2 0 1 0 14.1MS
RO 2 0 2.5K
C1 2 0 20PF
L1 2 0 10UH
.AC LIN 400 8MEG 12MEG
.PRINT AC VM(2) VP(2)
.PROBE V(2)
.END
```

Results: $A_{\text{mid}} = 35.3$, $f_o = 10.1$ MHz, BW = 2.50 MHz

*Problem 17.115(c) - Problem 17.114

```
VS 1 0 AC 1
CGD 1 2 5PF
GM 2 0 1 0 14.1MS
RO 2 0 2.5K
C1 2 0 45PF
C2 2 3 50PF
L1 3 0 10UH
.AC LIN 400 8MEG 12MEG
.PRINT AC VM(2) VP(2) VM(3) VP(3)
.PROBE V(2) V(3)
.END
```

Results: $A_{\text{mid}} = 70.7$, $f_o = 10.1$ MHz, BW = 640 kHz

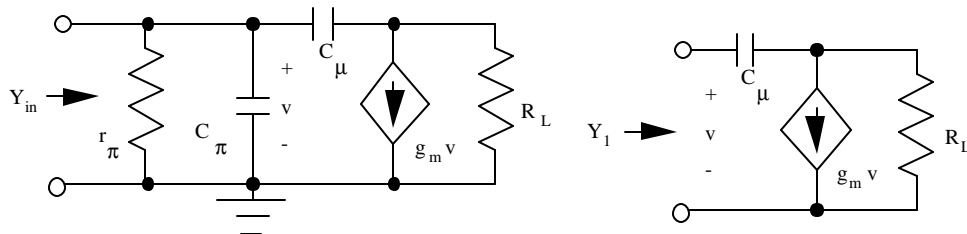17.116

$$Y_{in} = g_p + sC_p + Y_1 \quad | \quad (sC_m - g_m)V = (sC_m + G_L)V_o \quad | \quad V_o = \frac{(sC_m - g_m)}{(sC_m + G_L)}V$$

$$I = sC_m(V - V_o) = sC_m \frac{g_m + G_L}{(sC_m + G_L)}V \quad | \quad Y_1 = \frac{I}{V} = sC_m \frac{g_m + G_L}{(sC_m + G_L)} = sC_m \frac{1 + g_m R_L}{(sC_m R_L + 1)}$$

$$Y_1(j\omega) = j\omega C_m \frac{1 + g_m R_L}{(j\omega C_m R_L + 1)} = j\omega C_m (1 + g_m R_L) \frac{1 - j\omega C_m R_L}{(\omega C_m R_L)^2 + 1} \quad | \quad \text{For } (\omega C_m R_L)^2 \ll 1,$$

$$Y_1(j\omega) \cong j\omega C_m (1 + g_m R_L) + \frac{(1 + g_m R_L)}{R_L} (\omega C_m R_L)^2$$

From the results we see that the input capacitance is correctly modeled by the total Miller input capacitance, but the input resistance is not correctly modeled by just r_π :


$$C_{in} = C_p + C_m(1 + g_m R_L) \quad | \quad R_{in} = r_p \left\| \frac{R_L}{(1 + g_m R_L)(\omega C_m R_L)^2} \right.$$

$$(b) C_{in} = C_{GS} + C_{GD}(1 + g_m R_L) = 6pF + 2pF[1 + 5mS(10k\Omega)] = 108pF$$

$$R_{in} = \frac{R_L}{(1 + g_m R_L)(\omega C_{GD} R_L)^2} = \frac{10k\Omega}{[1 + 5mS(10k\Omega)][2p(5 \times 10^6)(2pF)(10k\Omega)]^2} = 497\Omega !$$

$$\text{Note also that } X_{C_{in}} = \frac{1}{2p(5 \times 10^6)(108pF)} = 295\Omega \quad | \quad \text{Both values are far less than infinity.}$$

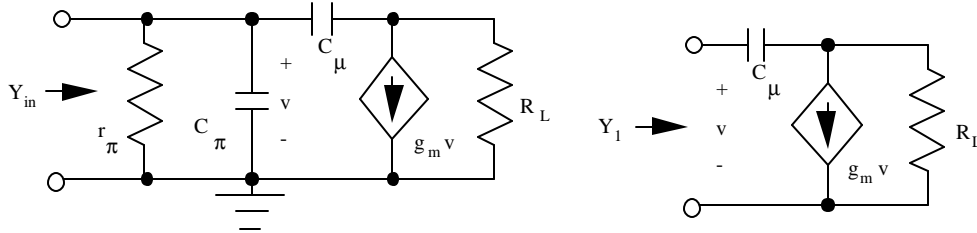Although the C_T approximation gives an excellent estimate for the dominant pole of the common-emitter amplifier, it does not do a good job of representing the input admittance at high frequencies. An improved estimate is needed for several of the problems to come.



$$Y_{in} = g_p + sC_p + Y_1 \quad | \quad (sC_m - g_m)V = (sC_m + G_L)V_o \quad | \quad V_o = \frac{(sC_m - g_m)}{(sC_m + G_L)}V$$

$$I = sC_m(V - V_o) = sC_m \frac{g_m + G_L}{(sC_m + G_L)}V \quad | \quad Y_1 = \frac{I}{V} = sC_m \frac{g_m + G_L}{(sC_m + G_L)} = sC_m \frac{1 + g_m R_L}{(sC_m R_L + 1)}$$

$$Y_1(j\omega) = j\omega C_m \frac{1 + g_m R_L}{(j\omega C_m R_L + 1)} = j\omega C_m (1 + g_m R_L) \frac{1 - j\omega C_m R_L}{(\omega C_m R_L)^2 + 1} \quad | \quad \text{For } (\omega C_m R_L)^2 \ll 1,$$

$$Y_1(j\omega) \cong j\omega C_m (1 + g_m R_L) + \frac{(1 + g_m R_L)}{R_L} (\omega C_m R_L)^2$$

From the results we see that the input capacitance is correctly modeled by the total Miller input capacitance, but the input resistance is not correctly modeled by just r_{π} :

$$C_{in} = C_p + C_m(1 + g_m R_L) \quad | \quad R_{in} = r_p \parallel \frac{R_L}{(1 + g_m R_L)(w C_m R_L)^2}$$

17.117

$$(a) f_s = 900 \text{ MHz} \quad | \quad f_{LO} = 1000 \text{ MHz} \quad | \quad f_{VHF} = f_{LO} - f_s = 100 \text{ MHz} \quad | \quad f_{IM} = f_{LO} + f_s = 1900 \text{ MHz}$$

$$(b) f_s = 900 \text{ MHz} \quad | \quad f_{LO} = 800 \text{ MHz} \quad | \quad f_{VHF} = f_s - f_{LO} = 100 \text{ MHz} \quad | \quad f_{IM} = f_s + f_{LO} = 1700 \text{ MHz}$$

17.118

$$\text{Using Eq. (17.192): } T(s) = A_{mid} \frac{s \frac{w_o}{Q}}{s^2 + s \frac{w_o}{Q} + w_o^2} \quad | \quad f_o = 100 \text{ MHz} \quad | \quad f = 1900 \text{ MHz} \quad | \quad Q = 75$$

$$T(jw) = A_{mid} \frac{jw \frac{w_o}{Q}}{w_o^2 - w^2 + jw \frac{w_o}{Q}} = A_{mid} \frac{j \frac{w_o}{wQ}}{\frac{w_o^2}{w^2} - 1 + j \frac{w_o}{wQ}} = A_{mid} \frac{j \frac{f_o}{fQ}}{\frac{f_o^2}{f^2} - 1 + j \frac{f_o}{fQ}}$$

$$|T(jw)| = |A_{mid}| \frac{\frac{f_o}{fQ}}{\sqrt{\left(\frac{f_o^2}{f^2} - 1\right)^2 + \left(\frac{f_o}{fQ}\right)^2}} = |A_{mid}| \frac{\frac{100}{1900(75)}}{\sqrt{\left[\left(\frac{100}{1900}\right)^2 - 1\right]^2 + \left(\frac{100}{1900(75)}\right)^2}} = 7.04 \times 10^{-3} |A_{mid}|$$

$$\text{Relative gain at 1900 MHz} = 20 \log(7.04 \times 10^{-3}) = -63.1 \text{ dB} \quad | \quad \text{Attenuation} = 63.1 \text{ dB}$$

17.119

$$\text{Using Eq. (17.192): } T(s) = A_{mid} \frac{s \frac{w_o}{Q}}{s^2 + s \frac{w_o}{Q} + w_o^2} \quad | \quad f_o = 10.7 \text{ MHz} \quad | \quad f = 189.3 \text{ MHz} \quad | \quad Q = 50$$

$$T(jw) = A_{mid} \frac{jw \frac{w_o}{Q}}{w_o^2 - w^2 + jw \frac{w_o}{Q}} = A_{mid} \frac{j \frac{w_o}{wQ}}{\frac{w_o^2}{w^2} - 1 + j \frac{w_o}{wQ}} = A_{mid} \frac{j \frac{f_o}{fQ}}{\frac{f_o^2}{f^2} - 1 + j \frac{f_o}{fQ}}$$

$$|T(jw)| = |A_{mid}| \frac{\frac{f_o}{fQ}}{\sqrt{\left(\frac{f_o^2}{f^2} - 1\right)^2 + \left(\frac{f_o}{fQ}\right)^2}} = |A_{mid}| \frac{\frac{10.7}{189.3(50)}}{\sqrt{\left[\left(\frac{10.7}{189.3}\right)^2 - 1\right]^2 + \left(\frac{10.7}{189.3(50)}\right)^2}} = 1.13 \times 10^{-3} |A_{mid}|$$

$$\text{Relative gain at 189.3 MHz} = 20 \log(1.13 \times 10^{-3}) = -58.9 \text{ dB} \quad | \quad \text{Attenuation} = 58.9 \text{ dB}$$

17.120

$$(a) f_s = 1800 \leftrightarrow 2000 \text{ MHz} \quad | \quad f_{IF} = 70 \text{ MHz}$$

$$f_{LO}^{\min} = f_s^{\min} - f_{IF} = 1800 - 70 = 1730 \text{ MHz} \quad | \quad f_{LO}^{\max} = f_s^{\max} - f_{IF} = 2000 - 70 = 1930 \text{ MHz}$$

$$f_{IM}^{\min} = f_s^{\min} + f_{LO}^{\min} = 1800 + 1730 = 3530 \text{ MHz} \quad | \quad f_{IM}^{\max} = f_s^{\max} + f_{LO}^{\max} = 2000 + 1930 = 3930 \text{ MHz}$$

$$(b) f_s = 1800 \leftrightarrow 2000 \text{ MHz} \quad | \quad f_{IF} = 70 \text{ MHz}$$

$$f_{LO}^{\min} = f_s^{\min} + f_{IF} = 1800 + 70 = 1870 \text{ MHz} \quad | \quad f_{LO}^{\max} = f_s^{\max} + f_{IF} = 2000 + 70 = 2070 \text{ MHz}$$

$$f_{IM}^{\min} = f_s^{\min} + f_{LO}^{\min} = 1800 + 1870 = 3670 \text{ MHz} \quad | \quad f_{IM}^{\max} = f_s^{\max} + f_{LO}^{\max} = 2000 + 2070 = 4070 \text{ MHz}$$

(c) In both cases, the LO range overlaps the received frequency range which is not the most desirable choice for LO. Because of the low IF frequency, there is not much difference in the image frequencies.

17.121

$$(a) V_{EQ} = -12 \frac{30k\Omega}{10k\Omega + 30k\Omega} = -9V \quad | \quad R_{EQ} = 10k\Omega \parallel 30k\Omega = 7.5k\Omega$$

$$I_{EE} = 100 \frac{-9 - 0.7 - (-12)}{7500 + (101)2200} = 1.00 \text{ mA} \quad | \quad I_1 = g_m v_{r_p} = g_m \frac{r_p}{r_p + (b_o + 1)R_E} V_1 = \frac{b_o}{r_p + (b_o + 1)R_E} V_1$$

$$r_p = \frac{100(0.025V)}{1.00mA} = 2.5k\Omega \quad | \quad I_1 = \frac{100(0.25V)}{2.5k\Omega + (101)2.2k\Omega} = 111 \text{ }\mu\text{A} \quad | \quad f_2 = 2kHz \quad | \quad f_1 = 1MHz$$

$$(b) v_o(t) = \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} [6.2 \sin n\mathbf{w}_2 t + 0.344 \sin(n\mathbf{w}_2 - \mathbf{w}_1)t - 0.344 \sin(n\mathbf{w}_2 + \mathbf{w}_1)t]$$

$$n = 1: \quad \frac{4}{\mathbf{p}} [6.2 \sin 2\mathbf{p}(1.00MHz)t + 0.344 \sin 2\mathbf{p}(0.998MHz)t - 0.344 \sin 2\mathbf{p}(1.002MHz)t]$$

$$n = 3: \quad \frac{4}{3\mathbf{p}} [6.2 \sin 2\mathbf{p}(3.00MHz)t + 0.344 \sin 2\mathbf{p}(2.998MHz)t - 0.344 \sin 2\mathbf{p}(3.002MHz)t]$$

$$0.998 \text{ MHz}: \quad \frac{1.38}{\mathbf{p}} = 0.438 \text{ V} \quad | \quad 1.000 \text{ MHz}: \quad \frac{24.8}{\mathbf{p}} = 7.89 \text{ V} \quad | \quad 1.002 \text{ MHz}: \quad -\frac{1.38}{\mathbf{p}} = -0.438 \text{ V}$$

$$2.998 \text{ MHz}: \quad \frac{1.38}{3\mathbf{p}} = 0.146 \text{ V} \quad | \quad 3.000 \text{ MHz}: \quad \frac{24.8}{3\mathbf{p}} = 2.63 \text{ V}$$

$$(c) V_1^{\max} = 5mV(1 + g_m R_E) = 0.005[1 + 40(1.00mA)(2.2k\Omega)] = 0.445 \text{ V}$$

17.122

$$v_o(t) = \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} [5 \sin n\mathbf{w}_1 t + 0.5 \sin(n-1)\mathbf{w}_1 t - 0.5 \sin(n+1)\mathbf{w}_1 t]$$

$$n=1: \frac{4}{\mathbf{p}} [5 \sin \mathbf{w}_1 t - 0.5 \sin 2\mathbf{w}_1 t]$$

$$n=3: \frac{4}{3\mathbf{p}} [5 \sin 3\mathbf{w}_1 t + 0.5 \sin 2\mathbf{w}_1 t - 0.5 \sin 4\mathbf{w}_1 t]$$

$$n=5: \frac{4}{5\mathbf{p}} [5 \sin 5\mathbf{w}_1 t + 0.5 \sin 4\mathbf{w}_1 t - 0.5 \sin 6\mathbf{w}_1 t]$$

$$n=7: \frac{4}{7\mathbf{p}} [5 \sin 7\mathbf{w}_1 t + 0.5 \sin 6\mathbf{w}_1 t - 0.5 \sin 8\mathbf{w}_1 t]$$

$$\mathbf{w}_1: \frac{20}{\mathbf{p}} = 6.37 \text{ V} \quad | \quad 2\mathbf{w}_1: -\frac{2}{\mathbf{p}} + \frac{2}{3\mathbf{p}} = -\frac{4}{3\mathbf{p}} = 0.424 \text{ V} \quad | \quad 3\mathbf{w}_1: \frac{20}{3\mathbf{p}} = 2.12 \text{ V}$$

$$4\mathbf{w}_1: -\frac{2}{3\mathbf{p}} + \frac{2}{5\mathbf{p}} = -\frac{4}{15\mathbf{p}} = 0.9849 \text{ V} \quad | \quad 5\mathbf{w}_1: \frac{4}{\mathbf{p}} = 1.27 \text{ V}$$

17.123 The amplitude of each of the first two sidebands is 1/2 the amplitude of the carrier.

17.124

(a) For $n=2$, the output is zero.

$$v_o(t) = 0.01 \left(\frac{5k\Omega}{0.5k\Omega} \right) \left(\frac{2}{\mathbf{p}} \right) [\cos(1.6 \times 10^8 \mathbf{p}t) - \cos(2.0 \times 10^8 \mathbf{p}t)]$$

$$v_o(t) = 0.0637 [\cos(1.6 \times 10^8 \mathbf{p}t) - \cos(2.0 \times 10^8 \mathbf{p}t)] \text{ V}$$

(b) Using the result for the differential pair in Section 15.3.3,

$$V_1 \leq 0.027 \text{ V} [1 + 40(2 \text{ mA})(0.5 k\Omega)] = 1.11 \text{ V}$$

17.125

$$(a) v_o(t) = V_m \left(\frac{1k\Omega}{0.1k\Omega} \right) \left(\frac{2}{\mathbf{p}} \right) [\cos(\mathbf{w}_c - \mathbf{w}_m)t - \cos(\mathbf{w}_c + \mathbf{w}_m)t]$$

$$v_o(t) = \frac{20}{\mathbf{p}} V_m [\cos(1.6 \times 10^8 \mathbf{p}t) - \cos(2.0 \times 10^8 \mathbf{p}t)] \text{ V}$$

$$A_v = \frac{20V_m}{\mathbf{p}V_m} = \frac{20}{\mathbf{p}} = 6.37$$

(b) Using the result for the differential pair in Section 15.3.3,

$$V_1 \leq 0.027 \text{ V} [1 + 40(5 \text{ mA})(0.1 k\Omega)] = 0.567 \text{ V}$$

17.126

$$v_o(t) = V_m \frac{R_c}{R_1} \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} \cos n\mathbf{w}_c t \cos \mathbf{w}_m t = V_m \frac{R_c}{R_1} \left[\sum_{n \text{ odd}} \frac{2}{n\mathbf{p}} \cos(n\mathbf{w}_c - \mathbf{w}_m)t \cos(n\mathbf{w}_c + \mathbf{w}_m)t \right]$$

17.127

$$v_o(t) = \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} [5 \sin n\mathbf{w}_1 t + 0.5 \sin (n-1)\mathbf{w}_1 t - 0.5 \sin (n+1)\mathbf{w}_1 t]$$

$$n=1: \frac{4}{\mathbf{p}} [5 \sin \mathbf{w}_1 t - 0.5 \sin 2\mathbf{w}_1 t]$$

$$n=3: \frac{4}{3\mathbf{p}} [5 \sin 3\mathbf{w}_1 t + 0.5 \sin 2\mathbf{w}_1 t - 0.5 \sin 4\mathbf{w}_1 t]$$

$$n=5: \frac{4}{5\mathbf{p}} [5 \sin 5\mathbf{w}_1 t + 0.5 \sin 4\mathbf{w}_1 t - 0.5 \sin 6\mathbf{w}_1 t]$$

$$n=7: \frac{4}{7\mathbf{p}} [5 \sin 7\mathbf{w}_1 t + 0.5 \sin 6\mathbf{w}_1 t - 0.5 \sin 8\mathbf{w}_1 t]$$

$$\mathbf{w}_1: \frac{20}{\mathbf{p}} = 6.37 \text{ V} \quad | \quad 2\mathbf{w}_1: -\frac{2}{\mathbf{p}} + \frac{2}{3\mathbf{p}} = -\frac{4}{3\mathbf{p}} = 0.424 \text{ V} \quad | \quad 3\mathbf{w}_1: \frac{20}{3\mathbf{p}} = 2.12 \text{ V}$$

$$4\mathbf{w}_1: -\frac{2}{3\mathbf{p}} + \frac{2}{5\mathbf{p}} = -\frac{4}{15\mathbf{p}} = 0.9849 \text{ V} \quad | \quad 5\mathbf{w}_1: \frac{4}{\mathbf{p}} = 1.27 \text{ V}$$


17.128

For this case, the output switches between 0 and v_1 , and v_1 is multiplied by the function

$$v_2 = 1 + \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} \sin n\mathbf{w}_2 t \text{ and}$$

$$v_o(t) = I_{EE} R_C + I_1 R_C \sin n\mathbf{w}_1 t + \sum_{n \text{ odd}} \frac{4}{n\mathbf{p}} \left[I_{EE} R_C \sin n\mathbf{w}_2 t + \frac{I_1 R_C}{2} \cos (n\mathbf{w}_2 - \mathbf{w}_1) t - \frac{I_1 R_C}{2} \cos (n\mathbf{w}_2 + \mathbf{w}_1) t \right]$$

17.129

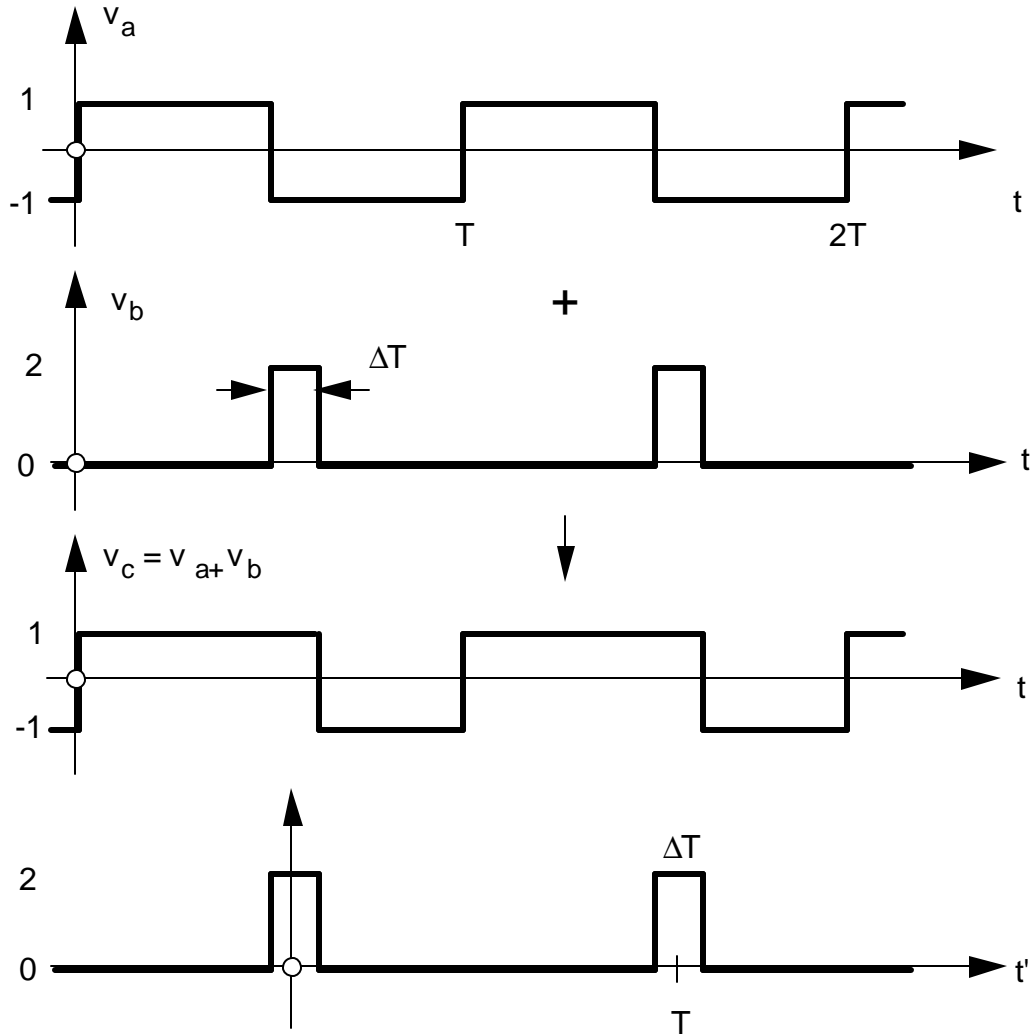

$$v_p(t) = 2\frac{\Delta T}{T} + \frac{4}{p} \sum_1^{\infty} \frac{(-1)^n}{n} \sin(n\omega_2 \Delta T) \cos(n\omega_2 t)$$

The new undesired term at ω_1 in the output is caused by the dc offset term in $v_p(t)$.

$$v_{ol}(t) = 2\frac{\Delta T}{T} I_1 R_C \sin \omega_1 t. \text{ For a 60/40 duty cycle, } v_{ol}(t) = \frac{I_1 R_C}{5} \sin \omega_1 t$$

$$\text{whereas the desired output component is } v_{ol}(t) = \frac{2}{p} I_1 R_C \cos(\omega_2 - \omega_1)t$$

17.130

Referring to the previous problem,
$$v_p(t) = \frac{\Delta T}{T} + \frac{2}{p} \sum_1^{\infty} \frac{(-1)^n}{n} \sin(n\omega_c \Delta T) \cos(n\omega_c t)$$

$$v_o(t) = V_m \left(\frac{R_C}{R_1} \right) \left[\frac{\Delta T}{T} + \frac{2}{p} \sum_1^{\infty} \frac{(-1)^n}{n} \sin(n\omega_c \Delta T) \cos(n\omega_c t) \right] \sin(\omega_m t)$$

There still is not output at the carrier frequency ω_c . The imbalance occurs at ω_m .