

CHAPTER 18

18.1

$$(a) T = A\mathbf{b} = \infty \quad | \quad A_v = \frac{1}{\mathbf{b}} = 5 \quad | \quad FGE = 0$$

$$(b) A = 10^{\frac{86}{20}} = 20000 \quad | \quad T = 20000(0.2) = 4000$$

$$A_v = \frac{A}{1 + A\mathbf{b}} = \frac{20000}{1 + 4000} = 5.00 \quad | \quad FGE = \frac{100\%}{1 + A\mathbf{b}} = \frac{100\%}{4001} = 0.025\%$$

$$(c) T = 10(0.2) = 2 \quad | \quad A_v = \frac{A}{1 + A\mathbf{b}} = \frac{10}{1 + 2} = 3.33 \quad | \quad FGE = \frac{100\%}{1 + 2} = 33.3\%$$

18.2

$$(a) \mathbf{b} = \frac{R_1}{R_1 + R_2} = \frac{1k\Omega}{101k\Omega} = \frac{1}{101}$$

$$(b) T = A\mathbf{b} = 10^{\frac{80}{20}} \left(\frac{1}{101} \right) = 99.0 \quad | \quad A_v = \frac{A}{1 + A\mathbf{b}} = \frac{10^4}{100} = 100$$

18.3

$$(a) \mathbf{b}(s) = \frac{R_1}{R_1 + R_2} = \frac{1k\Omega}{101k\Omega} = \frac{1}{101} \quad | \quad T(s) = A\mathbf{b} = 10^{\frac{80}{20}} \left(\frac{1}{101} \right) = 99.0$$

$$A_v = -\frac{R_2}{R_1} \frac{A\mathbf{b}}{1 + A\mathbf{b}} = -\left(\frac{100k\Omega}{1k\Omega} \right) \left(\frac{99}{100} \right) = -99$$

18.4

$$\mathbf{b}(s) = \frac{Z_1(s)}{Z_1(s) + Z_2(s)} = \frac{R}{R + \frac{1}{sC}} = \frac{s}{s + \frac{1}{RC}} = \frac{s}{s + 10^4} \quad | \quad A = 10^{\frac{80}{20}} = 10^4$$

$$T(s) = A\mathbf{b} = \frac{10^4 s}{s + 10^4} \quad | \quad A_v = -\frac{Z_2}{Z_1} \frac{A\mathbf{b}}{1 + A\mathbf{b}} = -\left(\frac{1}{sRC} \right) \frac{\frac{10^4 s}{s + 10^4}}{1 + \frac{10^4 s}{s + 10^4}} = -\left(\frac{1}{RC} \right) \left(\frac{1}{s + 1} \right)$$

Instead of a pole at the origin, the integrator has a low-pass response with a pole at $\omega = 1$ rad/s.

18.5

$$S_{A_v}^{A_v} = \frac{A}{A_v} \frac{\mathcal{I}A_v}{\mathcal{I}A} \quad A_v = \frac{A}{1 + Ab}$$

$$\frac{\mathcal{I}A_v}{\mathcal{I}A} = \frac{(1 + Ab)1 - Ab}{(1 + Ab)^2} = \frac{1}{(1 + Ab)^2} \quad S_{A_v}^{A_v} = \frac{A}{\frac{A}{1 + Ab}} \frac{1}{(1 + Ab)^2} = \frac{1}{1 + Ab} \approx \frac{1}{Ab}$$


$$S_{A_v}^{A_v} = \frac{1}{1 + 10^5(0.01)} = \frac{1}{1001}$$

$$\frac{\mathcal{I}A_v}{A_v} = S_{A_v}^{A_v} \frac{\mathcal{I}A}{A} = \frac{1}{1001} 10\% = 9.99 \times 10^{-3}\%$$

18.6

$$A_v = \frac{A}{1 + Ab} = \frac{A}{1 + A} \quad | \quad \text{From Chapter 12, } GE = \frac{1}{1 + Ab} = \frac{1}{1 + A}$$

$$\frac{1}{1 + A} \leq 10^{-4} \rightarrow A \geq 9999 \quad | \quad A \geq 80 \text{ dB}$$

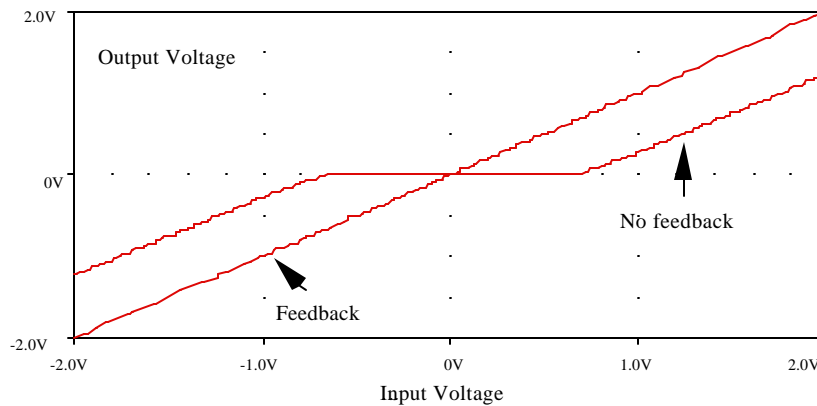18.7

*Problem 18.7 – Figure 18.74 - Class-B Amplifiers

```

VCC 3 0 DC 10
VEE 4 0 DC -10
VI 1 0 DC 0
Q1 3 1 2 NBJT
Q2 4 1 2 PBJT
RL1 2 0 2K
RID 1 7 100K
E1 5 0 1 7 5000
RO 5 6 100
Q3 3 6 7 NBJT
Q4 4 6 7 PBJT
RL2 7 0 2K
.MODEL NBJT NPN
.MODEL PBJT PNP
.OP
.DC VS -10 10 .01
.PROBE V(1) V(2) V(7)
.END

```

18.8

$$A_v = \frac{A}{1 + Ab} \quad | \quad \text{From Chapter 12, } GE = \frac{1}{1 + Ab} \cong \frac{1}{Ab}$$

$$\frac{1}{b} = 200 \quad | \quad GE \cong \frac{200}{A} \leq 0.002 \rightarrow A \geq \frac{200}{0.002} = 10^5 \quad | \quad A \geq 100 \text{ dB}$$

18.9 (a) Series-series feedback (b) Shunt-series feedback (c) Shunt-shunt feedback (d) Series-shunt feedback

18.10 (a) Series-shunt feedback (b) Shunt-series feedback (c) Series-series feedback (d) Shunt-shunt feedback

18.11 (a) Series-shunt and series-series feedback (b) Shunt-series and shunt-shunt and feedback

18.12 (a) Shunt-series and series-series feedback (b) Shunt-shunt and series-shunt feedback

18.13

$$A = 10^{\frac{86}{20}} = 20000$$

$$(a) R_{in} = R_{id}(1 + Ab) \quad | \quad \text{For } b = 1, R_{in} = 40k\Omega(1 + 20000) = 800 \text{ M}\Omega$$

$$(b) R_{in} = \frac{R_{id}}{(1 + Ab)} \quad | \quad \text{For } b = 1, R_{in} = \frac{40k\Omega}{(1 + 20000)} = 2.00 \text{ }\Omega$$

$$(c) R_{out} = R_o(1 + Ab) \quad | \quad \text{For } b = 1, R_{out} = 1k\Omega(1 + 20000) = 20 \text{ M}\Omega$$

$$(d) R_{out} = \frac{R_o}{(1 + Ab)} \quad | \quad \text{For } b = 1, R_{out} = \frac{1k\Omega}{(1 + 20000)} = 50.0 \text{ m}\Omega$$

18.14


$$(a) A_v = 10^{\frac{86}{20}} = 20000 \quad | \quad A_i = \frac{i_o}{i_i} \quad | \quad i_o = i_i(40k\Omega) \frac{20000}{1k\Omega} \rightarrow A_i = 8.00 \times 10^5$$

With resistive feedback, the closed-loop gain cannot exceed the open-loop gain.

Therefore, $A_i \leq 8.00 \times 10^5$.

$$(b) A_{tr} = \frac{i_o}{v_i} = \frac{i_o}{i_i(40k\Omega)} = \frac{A_i}{(40k\Omega)} \quad | \quad A_{tr} \leq \frac{8 \times 10^5}{4 \times 10^4 \Omega} = 20 \text{ S}$$

18.15 (a)

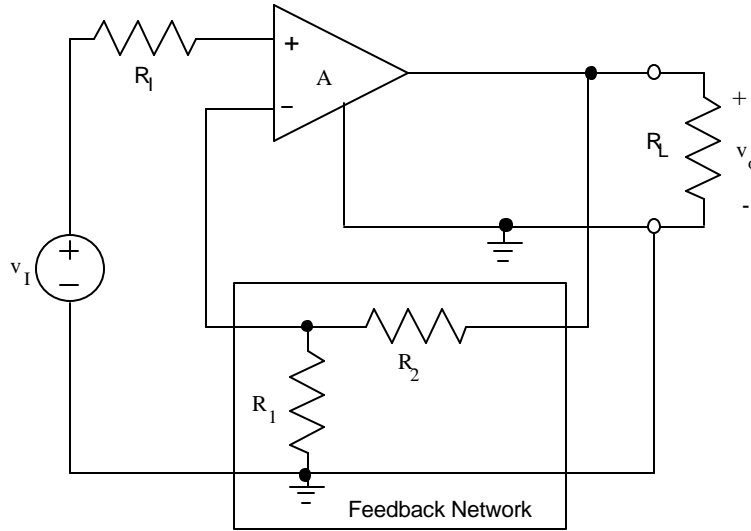

$$(b) h_{11}^A = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 15k\Omega \quad | \quad h_{11}^F = 4.3k\Omega \parallel 39k\Omega = 3.87k\Omega \quad | \quad h_{11}^T = 18.9k\Omega$$

$$h_{22}^A = \left. \frac{i_2}{v_2} \right|_{i_1=0} = (1k\Omega)^{-1} = (1k\Omega)^{-1} \quad | \quad h_{22}^F = (39k\Omega + 4.3k\Omega)^{-1} = (43.3k\Omega)^{-1} \quad | \quad h_{22}^T = +1.02mS$$

$$h_{21}^A = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{15k\Omega(5000)}{1k\Omega} = -75,000 \quad | \quad h_{21}^F = \left. \frac{i_2}{i_1} \right|_{v_2=0} = -\frac{4.3k\Omega}{39k\Omega + 4.3k\Omega} = -0.0993$$

$$h_{12}^A = \left. \frac{v_1}{v_2} \right|_{i_1=0} = 0 \quad | \quad h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = \frac{4.3k\Omega}{39k\Omega + 4.3k\Omega} = 0.0993$$

$$(c) A = \frac{-h_{21}^A}{(R_I + h_{11}^T)(h_{22}^T + G_L)} = \frac{-(-75000)}{(1k\Omega + 15k\Omega + 3.87k\Omega) \left(\frac{1}{5.6k\Omega} + \frac{1}{1k\Omega} + \frac{1}{43.3k\Omega} \right)} = 3140$$

$$b = 0.0993$$

$$(d) A_v = \frac{3140}{1 + 3140(0.0993)} = 10.0$$

$$(e) h_{21}^A \gg h_{21}^F \quad | \quad h_{12}^F \gg h_{12}^A \quad | \quad \text{Note : } (R_{in} = 6.22 M\Omega, R_{out} = 2.66 \Omega)$$

18.16 The circuit topology is identical to Fig. 18.8.

$$h_{11}^F = 5k\Omega \parallel 45k\Omega = 4.50k\Omega \quad | \quad h_{22}^F = (45k\Omega + 5k\Omega)^{-1} = (50.0k\Omega)^{-1}$$

$$b = h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = \frac{5k\Omega}{5k\Omega + 45k\Omega} = \frac{1}{10} \quad | \quad R_L \parallel \frac{1}{h_{22}^F} = 5k\Omega \parallel 50k\Omega = 4.55k\Omega$$


$$A = \frac{15k\Omega}{1k\Omega + 15k\Omega + 4.5k\Omega} (5000) \frac{4.55k\Omega}{1k\Omega + 4.55k\Omega} = 3000$$

$$A_v = \frac{A}{1 + Ab} = \frac{3000}{1 + 3000\left(\frac{1}{10}\right)} = \frac{3000}{301} = 9.97$$

$$R_{in} = R_{in}^A (1 + Ab) = (1k\Omega + 15k\Omega + 4.5k\Omega)(301) = 6.17 \text{ M}\Omega$$

$$R_{out} = \frac{R_{out}^A}{1 + Ab} = \frac{5k\Omega \parallel 50k\Omega \parallel 1k\Omega}{301} = 2.72 \text{ }\Omega$$

18.17

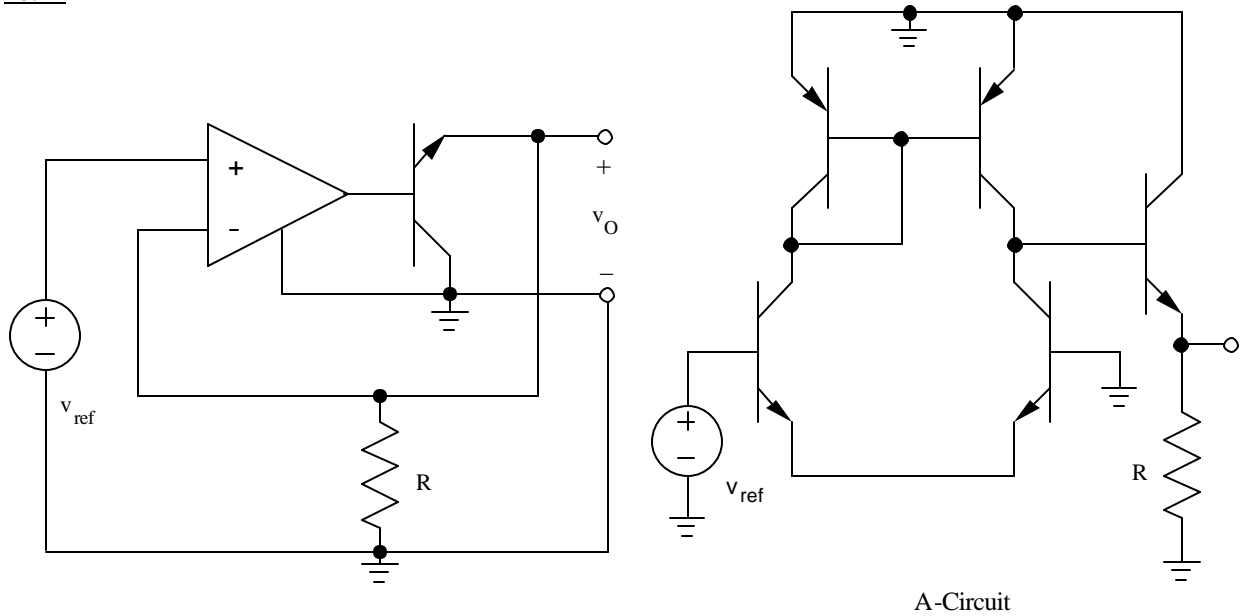

$$h_{11}^F = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 0 \quad | \quad h_{22}^F = \left. \frac{i_2}{v_2} \right|_{i_1=0} = \frac{1}{R} \quad | \quad h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = 1$$

$$A = g_{m1} (r_{o2} \parallel r_{o4} \parallel [r_{p5} + (b_o + 1)R]) \frac{(b_o + 1)R}{r_{p5} + (b_o + 1)R} = g_{m1} \frac{r_{o2} \parallel r_{o4}}{(r_{o2} \parallel r_{o4}) + r_{p5} + (b_o + 1)R} (b_o + 1)R$$

$$r_{o2} = \frac{50 + 1.4}{10^{-4}} = 514k\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613k\Omega \quad | \quad r_{o2} \parallel r_{o4} = 280k\Omega$$

$$I_{C5} \cong I_{E5} \cong \frac{12}{10^4} = 1.2mA \quad | \quad r_{p5} = \frac{100(.025)}{1.2mA} = 2.08k\Omega$$

$$A = 40(10^{-4})(280k\Omega) \frac{(101)10k\Omega}{280k\Omega + 2.08k\Omega + (101)10k\Omega} = 876$$


$$A_v = \frac{A}{1 + T} = \frac{876}{1 + 876(1)} = \frac{109}{110} = 0.999$$

$$R_{in} = R_{id}(1+T) = 2r_{p1}(1+T) = 2 \frac{100(0.025)}{10^{-4}}(877) = 43.9 \text{ M}\Omega$$

$$R_{out} = \frac{R \left\| \frac{r_{p5} + r_{o2} \parallel r_{o4}}{b_o + 1} \right\| 10 \text{ k}\Omega}{1+T} = \frac{10 \text{ k}\Omega \left\| \frac{2.08 \text{ k}\Omega + 280 \text{ k}\Omega}{101} \right\|}{877} = 2.49 \text{ }\Omega$$

$$i_o = a_o i_e = a_o \frac{v_o}{R} \quad \left| \quad \frac{i_o}{v_{ref}} = \frac{a_o}{R} \frac{v_o}{v_{ref}} = \frac{100}{101} \left(\frac{1}{10^4} \right) (0.999) = 98.9 \text{ }\mu\text{S} \right.$$

18.18

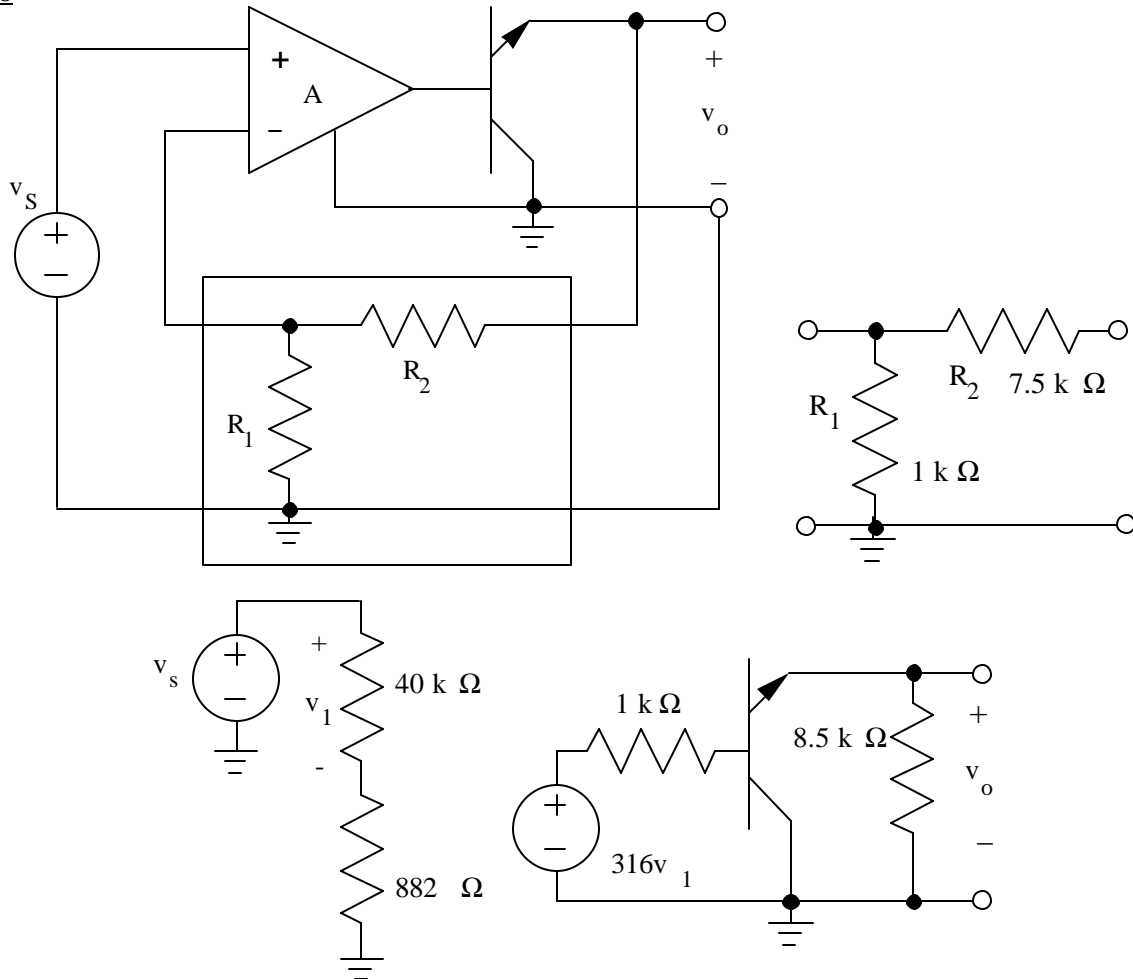

$$h_{11}^F = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 1 \text{ k}\Omega \parallel 7.5 \text{ k}\Omega = 882 \text{ }\Omega \quad \left| \quad h_{22}^F = \left. \frac{i_2}{v_2} \right|_{i_1=0} = \frac{1}{1 \text{ k}\Omega + 7.5 \text{ k}\Omega} = \frac{1}{8.5 \text{ k}\Omega}$$

$$b = h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 7.5 \text{ k}\Omega} = \frac{1}{8.5}$$


$$I_C = a_F I_E = \frac{100}{101} (200 \text{ mA}) = 198 \text{ mA} \quad \left| \quad r_p = \frac{100(0.025 \text{ V})}{198 \text{ mA}} = 12.6 \text{ k}\Omega$$

$$A = \frac{v_o}{v_s} = \frac{40k\Omega}{40k\Omega + 0.882k\Omega} (316) \frac{(b_o + 1)8.5k\Omega}{R_o + r_p + (b_o + 1)8.5k\Omega} = 309 \frac{(101)8.5k\Omega}{1k\Omega + 12.6k\Omega + (101)8.5k\Omega} = 304$$

$$A_v = \frac{A}{1 + T} = \frac{304}{1 + 304 \left(\frac{1}{8.5} \right)} = \frac{304}{36.8} = 8.27$$

$$R_{in} = R_{in}^A (1 + T) = 40.9k\Omega (36.8) = 1.51 M\Omega \quad | \quad R_{out} = \frac{R_{out}^A}{1 + T} = \frac{8.5k\Omega \parallel \frac{12.6k\Omega + 1k\Omega}{101}}{36.8} = 3.60 \Omega$$

18.19

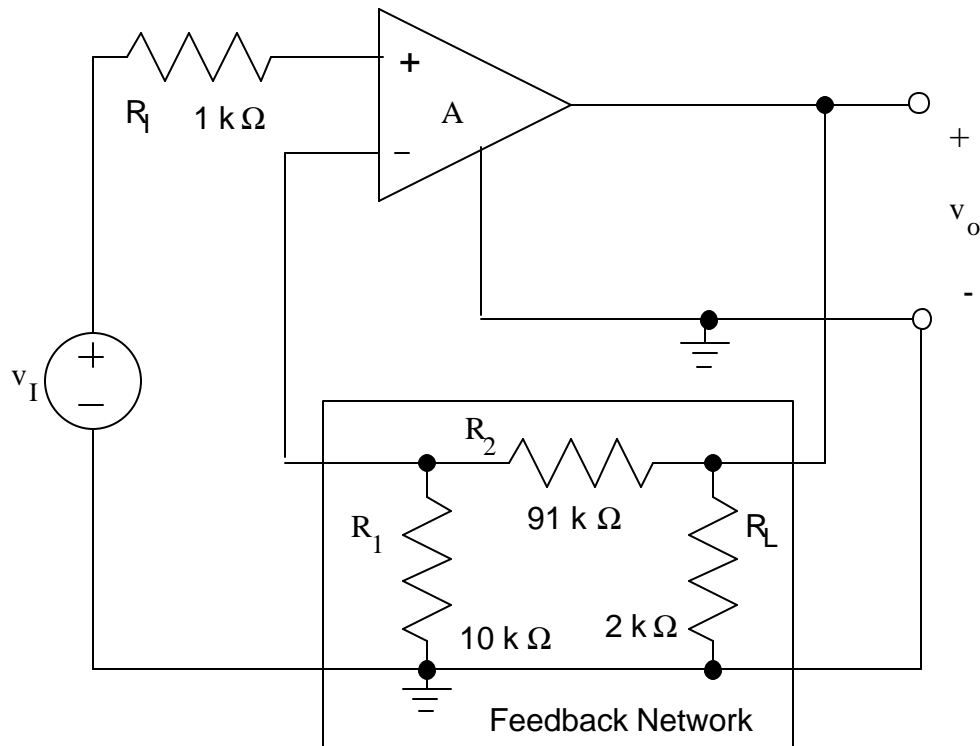

$$h_{11}^F = \left. \frac{v_1}{i_1} \right|_{v_2=0} = 10k\Omega \parallel 91k\Omega = 9.01k\Omega \quad | \quad h_{22}^F = \left. \frac{i_2}{v_2} \right|_{i_1=0} = \frac{1}{2k\Omega \parallel (1k\Omega + 7.5k\Omega)} = \frac{1}{1.96k\Omega}$$

$$\mathbf{b} = h_{12}^F = \left. \frac{v_1}{v_2} \right|_{i_2=0} = \frac{10k\Omega}{10k\Omega + 91k\Omega} = \frac{1}{0.0990}$$

$$A = \frac{v_o}{v_i} = \frac{25k\Omega}{1k\Omega + 25k\Omega + 9.01k\Omega} (10^4) \frac{1.96k\Omega}{1k\Omega + 1.96k\Omega} = 4730$$

$$A_v = \frac{A}{1 + A\mathbf{b}} = \frac{4730}{1 + 4730(0.990)} = 10.1 \quad | \quad R_{in} = R_{in}^A (1 + T) = 34.0k\Omega (469) = 16.0 M\Omega$$

$$R_{out} = \frac{R_{out}^A}{1 + T} = \frac{1.96k\Omega \parallel 1k\Omega}{469} = 1.41 \Omega$$

18.20


$$(a) S_A^{R_{in}} = \frac{A}{R_{in}} \frac{\mathcal{R}R_{in}}{\mathcal{I}A} \quad | \quad R_{in} = R_{in}^A (1 + Ab) \quad | \quad S_A^{R_{in}} = \frac{A}{R_{in}^A (1 + Ab)} R_{in}^A b = \frac{Ab}{(1 + Ab)} \approx 1$$

$$\frac{\mathcal{R}R_{in}}{R_{in}} = S_A^{R_{in}} \frac{\mathcal{I}A}{A} = \frac{10^5 (0.01)}{1 + 10^5 (0.01)} 10\% = 9.99\%$$

$$(b) S_A^{R_{out}} = \frac{A}{R_{out}} \frac{\mathcal{R}R_{out}}{\mathcal{I}A} \quad | \quad R_{out} = \frac{R_{out}^A}{(1 + Ab)} \quad | \quad \frac{\mathcal{R}R_{out}}{\mathcal{I}A} = -\frac{bR_{out}^A}{(1 + Ab)^2}$$

$$S_A^{R_{out}} = -\frac{A(1 + Ab)}{R_{out}^A} \frac{bR_{out}^A}{(1 + Ab)^2} = -\frac{Ab}{(1 + Ab)} \approx -1 \quad | \quad \frac{\mathcal{R}R_{out}}{R_{out}} = S_A^{R_{out}} \frac{\mathcal{I}A}{A} = -\frac{10^5 (0.01)}{1 + 10^5 (0.01)} 10\% = -9.99\%$$

18.21

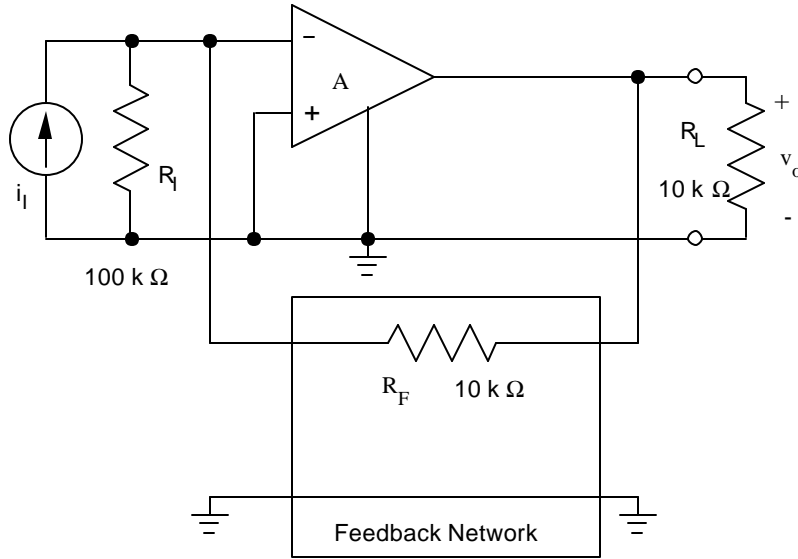

$$y_{11}^A = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{15k\Omega} \quad | \quad y_{22}^A = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{1k\Omega} \quad | \quad y_{21}^A = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -\frac{(-5000)}{1k\Omega} = 5S \quad | \quad y_{12}^A = \left. \frac{i_1}{v_2} \right|_{v_1=0} = 0$$

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{10k\Omega} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{10k\Omega} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -\frac{1}{10k\Omega} \quad | \quad y_{21}^F = \left. \frac{i_2}{v_1} \right|_{v_2=0} = -\frac{1}{10k\Omega}$$


$$y_{11}^T = \frac{1}{15k\Omega} + \frac{1}{10k\Omega} = 0.167mS \quad | \quad y_{22}^T = \frac{1}{1k\Omega} + \frac{1}{10k\Omega} = 1.10mS$$

$$A = \frac{-y_{21}^A}{(G_I + y_{11}^T)(y_{22}^T + G_L)} = \frac{-5}{(10^{-5} + 0.167 \times 10^{-3})(1.1 \times 10^{-3} + 10^{-4})} = -2.35 \times 10^7 \Omega \quad | \quad b = y_{12}^F = -10^{-4}$$

$$A_r = \frac{A}{1 + Ab} = \frac{-2.35 \times 10^7 \Omega}{1 + (-2.35 \times 10^7 \Omega)(-10^{-4} S)} = -10.0 k\Omega \quad | \quad Ab = 2350$$

$$\text{Note : } R_{in} = \frac{100k\Omega \parallel 10k\Omega \parallel 15k\Omega}{1 + 2350} = 2.41 \Omega \quad | \quad R_{out} = \frac{10k\Omega \parallel 1k\Omega \parallel 10k\Omega}{1 + 2350} = 0.355 \Omega$$

18.22

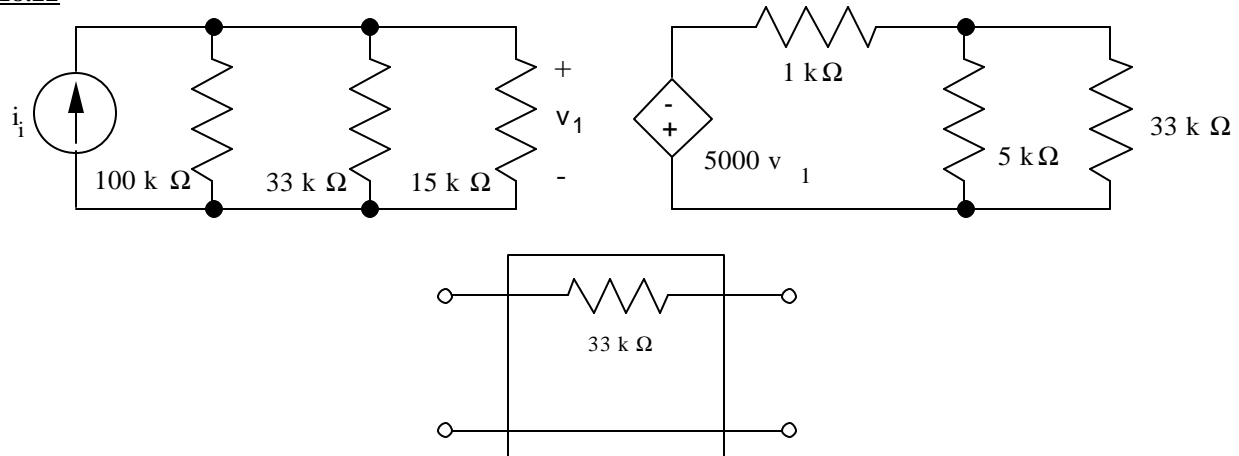

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{33k\Omega} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{33k\Omega} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -\frac{1}{33k\Omega}$$


$$(15k\Omega \parallel 33k\Omega \parallel 100k\Omega) = 9.35k\Omega \quad | \quad (5k\Omega \parallel 33k\Omega) = 4.34k\Omega$$

$$A = \frac{v_o}{i_i} = -5000 \frac{4.34k\Omega}{1k\Omega + 4.34k\Omega} (9.35k\Omega) = -3.80 \times 10^7$$

$$A_{tr} = \frac{A}{1 + Ab} = \frac{-3.80 \times 10^7}{1 + (-3.80 \times 10^7) \left(-\frac{1}{33 \times 10^3} \right)} = -33.0 k\Omega$$

$$R_{in} = \frac{(15k\Omega \parallel 33k\Omega \parallel 100k\Omega)}{1 + (-3.80 \times 10^7) \left(-\frac{1}{33 \times 10^3} \right)} = 8.11 \Omega \quad | \quad R_{out} = \frac{(33k\Omega \parallel 5k\Omega \parallel 1k\Omega)}{1 + (-3.80 \times 10^7) \left(-\frac{1}{33 \times 10^3} \right)} = 0.705 \Omega$$


18.23 REQ in Figure

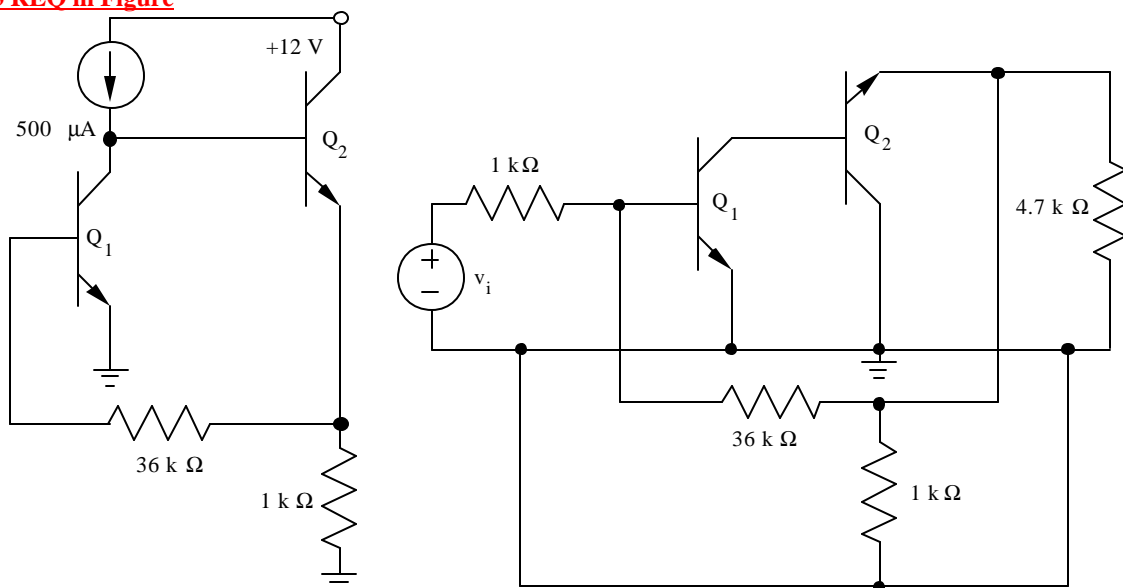

$$I_{C1} = 500\text{mA} - I_{B2} \quad | \quad I_{E2} = I_{B1} + \frac{36000I_{B1} + 0.7}{1000} = 37I_{B1} + 700\text{mA} \quad | \quad I_{B2} = \frac{I_{E2}}{101}$$

$$I_{C1} = 500\text{mA} - \frac{37I_{B1} + 700\text{mA}}{101} = 493\text{mA} - 0.366I_{B1} \rightarrow I_{C1} = 491.2\text{mA}$$

$$I_{E2} = 37 \frac{I_{C1}}{100} + 700\text{mA} = 881.7\text{mA} \quad | \quad I_{C2} = \frac{100}{101} I_{E2} = 873\text{mA}$$

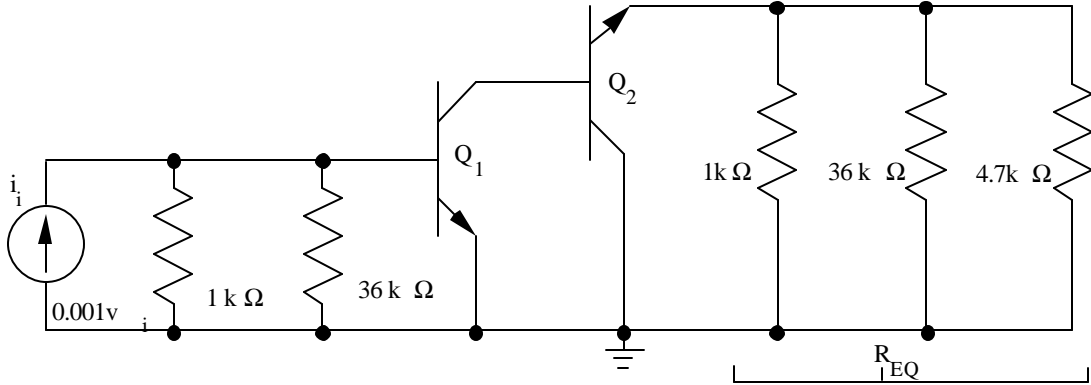

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{36k\Omega} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{36k\Omega \parallel 1k\Omega} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -\frac{1}{36k\Omega}$$

$$r_{p1} = \frac{100(0.025)}{491\text{mA}} = 5.09k\Omega \quad | \quad r_{p2} = \frac{100(0.025)}{873\text{mA}} = 2.86k\Omega \quad | \quad r_{o1} = \frac{50 + 1.6}{493 \times 10^{-6}} = 105k\Omega$$

$$R_E = (1k\Omega \parallel 36k\Omega \parallel 4.7k\Omega) = 807\Omega$$

$$A = \frac{v_o}{i_i} = (1k\Omega \parallel 36k\Omega \parallel r_{p1}) g_{m1} [r_{o1} \parallel (r_{p2} + (b_o + 1)R_E)] \frac{r_{p2} + (b_o + 1)R_E}{r_{o1} + r_{p2} + (b_o + 1)R_E}$$

$$A = \frac{v_o}{i_i} = -(1k\Omega \parallel 36k\Omega \parallel 5.09k\Omega) g_{m1} [r_{o1} \parallel (r_{p2} + (b_o + 1)R_{EQ})] \frac{(b_o + 1)R_{EQ}}{r_{p2} + (b_o + 1)R_{EQ}}$$

$$(1k\Omega \parallel 36k\Omega \parallel r_{p1}) = (1k\Omega \parallel 36k\Omega \parallel 5.09k\Omega) = 817\Omega \quad | \quad g_m = 40(491\text{mA}) = 19.6\text{mS}$$

$$[r_{o1} \parallel (r_{p2} + (b_o + 1)R_{EQ})] = [105k\Omega \parallel (2.86k\Omega + (101)806\Omega)] = 46.8k\Omega$$

$$R_{EQ} = 1k\Omega \parallel 36k\Omega \parallel 4.7k\Omega = 806\Omega \quad | \quad \frac{(b_o + 1)R_{EQ}}{r_{p2} + (b_o + 1)R_{EQ}} = \frac{(101)806\Omega}{2.86k\Omega + (101)806\Omega} = 0.966$$

$$A = -(817\Omega)(19.6\text{mS})(46.8k\Omega)(0.966) = -724k\Omega \quad | \quad Ab = -724k\Omega \left(-\frac{1}{36k\Omega} \right) = 20.1$$

$$A_{tr} = \frac{A}{1 + Ab} = \frac{-724k\Omega}{1 + 20.1} = -36.0k\Omega$$

$$\text{Note : } R_{in} = \frac{(1k\Omega \parallel 36k\Omega \parallel 5.09k\Omega)}{1 + 20.1} = 38.7\Omega \quad | \quad R_{in} = \left(R_{EQ} \parallel \frac{r_{p2} + r_{o1}}{b_o + 1} \right) \frac{1}{1 + Ab} = 21.8\Omega$$

$$R_{in} = \frac{(1k\Omega \parallel 36k\Omega \parallel 5.09k\Omega)}{1 + Ab} = \frac{817\Omega}{9.94} = 82.2 \Omega$$

$$R_{out} = \frac{\left(1k\Omega \parallel 36k\Omega \parallel 4.7k\Omega \parallel \frac{r_{p2} + r_{ol}}{101}\right)}{1 + Ab} = \frac{\left(806\Omega \parallel \frac{2.86k\Omega + 105k\Omega}{101}\right)}{9.94} = 46.2 \Omega$$

$$i_i = 10^{-3} v_i \rightarrow A_v = \frac{v_o}{v_i} = \frac{v_o}{1000 i_i} = -32.4$$


Note that this amplifier can be analyzed as a shunt-series feedback amplifier. This is good for student practice - see Problem 18.32.

18.24

```
*Problem 18.24 – Figure 18.77
VCC 5 0 DC 12
IDC 5 4 DC 500UA
II 0 2 AC 1
*IX 0 7 AC 1
RS 2 0 1K
C1 2 3 82UF
Q1 4 3 0 NBJT
Q2 5 4 6 NBJT
RF 3 6 36K
RE 6 0 1K
C2 6 7 47UF
RL 7 0 4.7K
.MODEL NBJT NPN BF=100 VA=50 IS=1E-15
.OP
.AC DEC 100 1E2 1E7
.PRINT AC VM(7) VP(7) VM(2) VP(2)
.END
```

Results: $A_{tr} = -34.4 \text{ k}\Omega$, $R_{in} = 36.8 \Omega$, $R_{out} = 18.6 \Omega$ -- Note that these values are highly sensitive to the precise value of r_{π} .

18.25

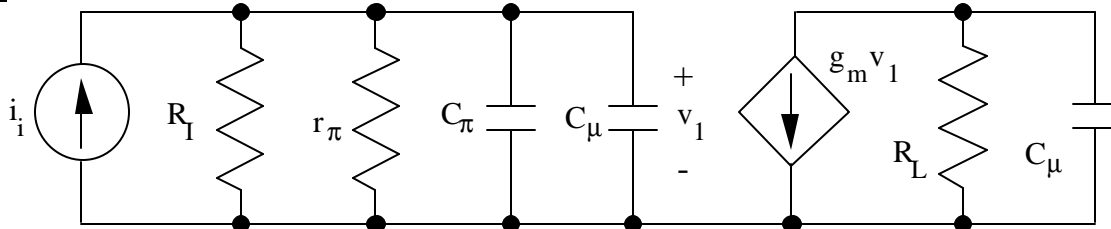

$$y_{12}^F = -sC_m \quad | \quad A = \frac{v_o}{i_i} = -\frac{r_{po}}{s(C_p + C_m)r_{po} + 1} (g_m) \frac{R_L}{sC_m R_L + 1} = -\frac{g_m r_{po} R_L}{[s(C_p + C_m)r_{po} + 1][sC_m R_L + 1]}$$


$$Z_{in}^A = \frac{r_{po}}{s(C_p + C_m)r_{po} + 1} \quad | \quad Z_{in} = \frac{Z_{in}^A}{1 + Ab} = \frac{\frac{r_{po}}{s(C_p + C_m)r_{po} + 1}}{1 - \frac{g_m r_{po} R_L}{[s(C_p + C_m)r_{po} + 1][sC_m R_L + 1]} (-sC_m)}$$

where $r_{po} = r_p \parallel R_L$ | $Z_{in} = \frac{r_{po}(sC_m R_L + 1)}{[s(C_p + C_m)r_{po} + 1][sC_m R_L + 1] + sC_m g_m r_{po} R_L}$

$$Z_{in} = \frac{r_{po}(sC_m R_L + 1)}{s^2(C_p + C_m)C_m r_{po} R_L + sr_{po}\left[C_p + C_m(1 + g_m R_L) + \frac{R_L}{r_{po}}\right] + 1} = \frac{r_{po}(sC_m R_L + 1)}{s^2(C_p + C_m)C_m r_{po} R_L + sr_{po}C_T + 1}$$

$$Z_{in} \cong \frac{r_{po}(sC_m R_L + 1)}{sr_{po}\left[C_p + C_m(1 + g_m R_L) + \frac{R_L}{r_{po}}\right] + 1} = \frac{r_{po}(sC_m R_L + 1)}{sr_{po}C_T + 1} \text{ for } \omega \ll \omega_T$$

18.26

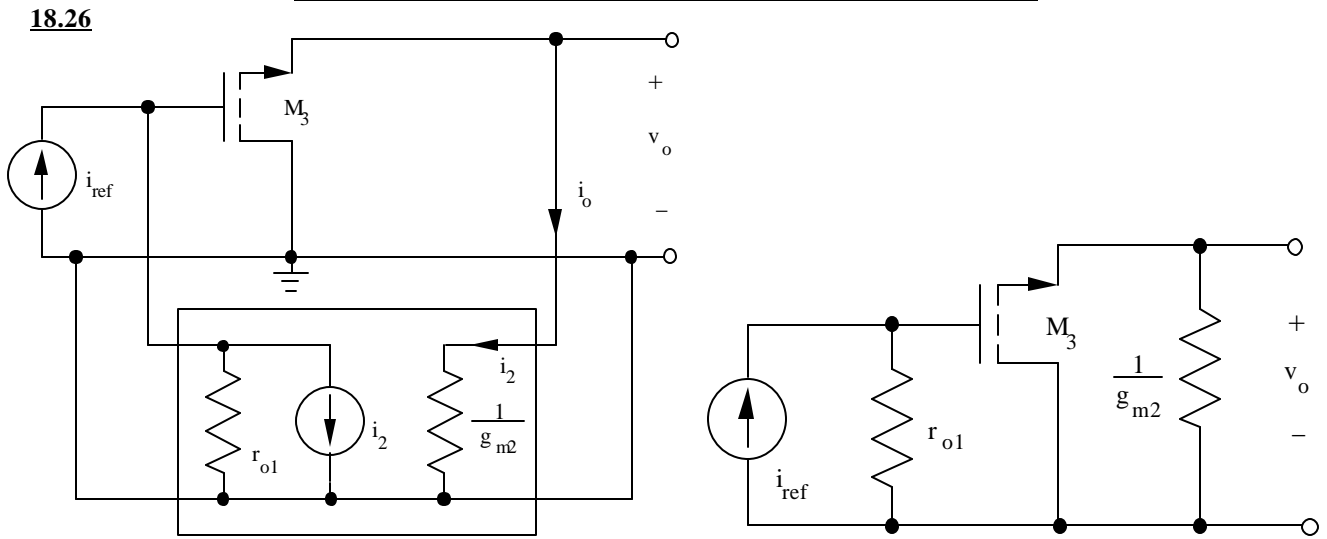

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = g_{o1} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = g_{m2} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = g_{m2}$$

$$A = \frac{v_o}{i_{ref}} = r_{o1} \frac{g_{m3} \frac{1}{g_{m2}}}{1 + g_{m3} \frac{1}{g_{m2}}} = \frac{r_{o1}}{2} \quad | \quad A_{tr} = \frac{A}{1 + Ab} = \frac{\frac{r_{o1}}{2}}{1 + \frac{r_{o1}}{2}(g_{m2})} = \frac{r_{o1}}{2 + m_{f1}}$$


$$R_{in} = \frac{r_{o1}}{1 + Ab} = \frac{r_{o1}}{1 + \frac{m_{f2}}{2}} = \frac{36k\Omega}{1 + \frac{72}{2}} = 973\Omega \quad | \quad \text{Note: } R_{in} \cong \frac{2}{g_m}$$

$$i_o = i_2 = g_{m2}v_o = g_{m2} \frac{r_{o1}}{m_{f1} + 2} i_{ref} \quad | \quad \frac{i_o}{i_{ref}} = \frac{m_{f1}}{m_{f1} + 2} = 0.973$$

18.27

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = g_{o1} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = g_{m2} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = \frac{b}{b+2} g_{m2} \cong g_{m2}$$

$$i_o = a_o i_2 = a_o g_{m2} v_o \quad | \quad A = \frac{v_o}{i_{ref}} = r_{o1} \frac{(b_o+1) \frac{1}{g_{m2}}}{r_{o1} + r_{p3} + (b_o+1) \frac{1}{g_{m2}}} \cong r_{o1} \frac{(b_o+1)}{m_f + 2b_o + 1} \cong \frac{b_o}{m_f} r_{o1} = r_{p1}$$

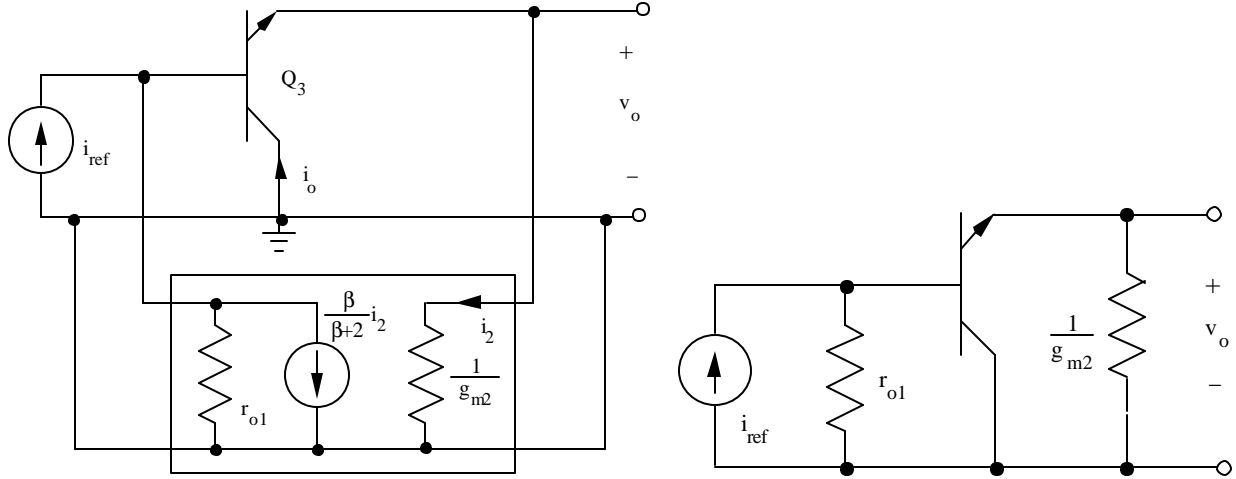

$$A_{tr} = \frac{A}{1 + Ab} = \frac{r_{o1} \frac{(b_o+1)}{m_f + 2b_o + 1}}{1 + r_{o1} \frac{(b_o+1)}{m_f + 2b_o + 1} (g_{m2})} \cong r_{o1} \frac{b_o + 1}{m_f b_o + 2m_f + 2b_o + 2} \cong \frac{r_{o1}}{m_f} = \frac{1}{g_{m1}}$$

$$A_{tr} = \frac{1}{50mS} = 20.0 \, \Omega \quad | \quad A_I = \frac{i_o}{i_{ref}} = a_o g_{m2} \frac{v_o}{i_{ref}} = a_o \frac{g_{m2}}{g_{m1}} \cong 1$$

$$R_{in}^A = r_{o1} \left[r_{p3} + (b_o+1) \frac{1}{g_{m2}} \right] \cong r_{o1} \| 2r_{p3} \cong 2r_{p3}$$

$$R_{in} = \frac{R_{in}^A}{1 + Ab} = \frac{r_{o1} \| 2r_{p3}}{1 + r_{o1} \frac{(b_o+1)}{m_f + 2b_o + 1} (g_{m2})} \cong \frac{r_{o1} \| 2r_{p3}}{1 + \frac{m_f (b_o+1)}{m_f + 2b_o + 1}} \cong \frac{r_{o1} \| 2r_{p3}}{b_o + 1} \cong \frac{2r_{p3}}{b_o + 1} \cong \frac{2}{g_{m3}}$$

$$R_{in} = \frac{r_{o1} \| 2r_{p3}}{b_o + 1} = \frac{40k\Omega \| 4k\Omega}{101} = 36.0 \, \Omega$$

18.28

*Problem 18.28 - BJT Wilson Source

*Current gain = 100

VCC 0 3 DC -6

IREF 0 1 DC 100UA

Q1 1 2 0 NBJT

Q2 2 2 0 NBJT

Q3 3 1 2 NBJT

.MODEL NBJT NPN BF=100 VA=50 IS=1E-15

.OP

.TF I(VCC) IREF

$$\frac{b_o r_{o3}}{2} = \frac{100(55.3V)}{2(100mA)} = 27.7 M\Omega \quad | \quad \text{SPICE : } 29.9 M\Omega$$

*Problem 18.28 - BJT Wilson Source

*Current gain = 10K

VCC 0 3 DC -6

IREF 0 1 DC 100UA

Q1 1 2 0 NBJT

Q2 2 2 0 NBJT

Q3 3 1 2 NBJT

.MODEL NBJT NPN BF=10K VA=50 IS=1E-15

.OP

.TF I(VCC) IREF

$$\text{END} \quad \text{SPICE : } 799 M\Omega$$

*Problem 18.28 - BJT Wilson Source

*Current gain = 1MEG

VCC 0 3 DC -6

IREF 0 1 DC 100UA

Q1 1 2 0 NBJT

Q2 2 2 0 NBJT

Q3 3 1 2 NBJT


.MODEL NBJT NPN BF=1MEG VA=50 IS=1E-15

.OP

.TF I(VCC) IREF

$$\text{END} \quad m_{f1} r_{o3} = 40(51.4) \frac{55.3V}{100mA} = 1.14 G\Omega \quad | \quad \text{SPICE : } 1.08 G\Omega$$

18.29

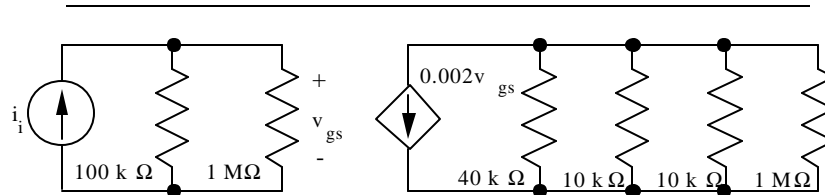

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = 10^{-6} S \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = 10^{-6} S \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -10^{-6} S$$

$$v_{gs} = i_i (100k\Omega \parallel 1M\Omega) = (90.9k\Omega) i_i \quad | \quad v_o = -(2 \times 10^{-3}) v_{gs} (40k\Omega \parallel 10k\Omega \parallel 10k\Omega \parallel 1M\Omega)$$


$$A = \frac{v_o}{i_i} = -(2mS)(4.44k\Omega)(90.9k\Omega) = -8.08 \times 10^5$$

$$A_{rr} = \frac{A}{1 + Ab} = \frac{-8.08 \times 10^5}{1 + (-8.08 \times 10^5)(-10^{-6})} = \frac{-8.08 \times 10^5}{1.81} = -446 k\Omega$$

$$R_{in} = \frac{(100k\Omega \parallel 1M\Omega)}{(1 + Ab)} = \frac{90.9k\Omega}{1.81} = 50.2 k\Omega$$

$$R_{out} = \frac{(40k\Omega \parallel 10k\Omega \parallel 10k\Omega \parallel 1M\Omega)}{(1 + Ab)} = \frac{4.44k\Omega}{1.81} = 2.45k\Omega$$

18.30

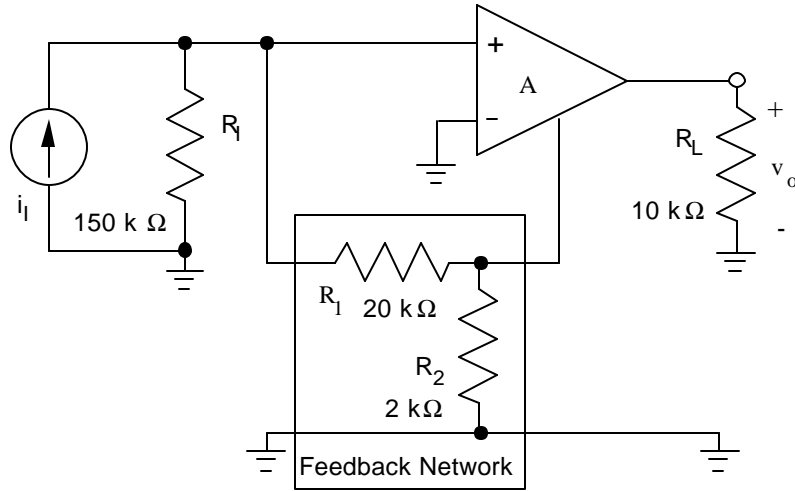

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{22k\Omega} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = 2k\Omega \parallel 20k\Omega = 1.82k\Omega \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = -\frac{2k\Omega}{20k\Omega + 2k\Omega} = -\frac{1}{11}$$

$$g_{11}^T = \frac{1}{15k\Omega} + \frac{1}{22k\Omega} = \frac{1}{8.92k\Omega} \quad | \quad g_{22}^T = 1.82k\Omega + 1k\Omega = 2.82k\Omega \quad | \quad g_{21}^A = \left. \frac{v_2}{v_1} \right|_{i_2=0} = 5000$$


$$A = -\frac{g_{21}^A}{(G_I + g_{11}^T)(g_{22}^T + R_L)} = -\frac{5000}{\left(\frac{1}{150k\Omega} + \frac{1}{22k\Omega}\right)(2.82k\Omega + 10k\Omega)} = -3280 \quad | \quad b = g_{12}^F = -\frac{1}{11}$$

$$A_i = \frac{A}{1 + Ab} = \frac{-3280}{1 + (-3280)\left(-\frac{1}{11}\right)} = -11.0 \quad | \quad Ab = 298$$

$$R_{in} = \frac{(150k\Omega \parallel 8.92k\Omega)}{(1 + Ab)} = \frac{8.42k\Omega}{1 + 298} = 28.1 \Omega$$

$$R_{out} = (10k\Omega + 2.82k\Omega)(1 + Ab) = (12.8k\Omega)(299) = 3.83 M\Omega$$

18.31

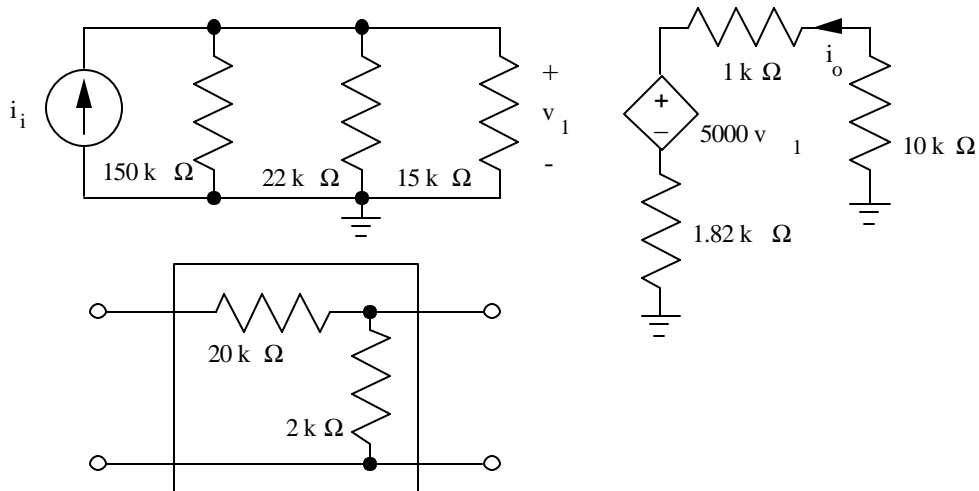

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{11k\Omega} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = 1k\Omega \parallel 10k\Omega = 909\Omega \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = -\frac{1k\Omega}{10k\Omega + 1k\Omega} = -\frac{1}{11}$$


$$A = \frac{i_2}{i_i} = -\left(100k\Omega \parallel 11k\Omega \parallel 15k\Omega\right) \frac{5k\Omega}{(5+1+0.909)k\Omega} = -4.32 \times 10^3$$

$$A_i = \frac{A}{1+Ab} = \frac{-4.32 \times 10^3}{1 + (-4.32 \times 10^3) \left(-\frac{1}{11}\right)} = -11.0$$

$$R_{in} = \frac{(100k\Omega \parallel 11k\Omega \parallel 15k\Omega)}{(1+Ab)} = \frac{5.97k\Omega}{394} = 15.2 \Omega$$

$$R_{out} = (5k\Omega + 1k\Omega + 0.909k\Omega)(1+Ab) = (6.91k\Omega)(394) = 2.72M\Omega$$


18.32

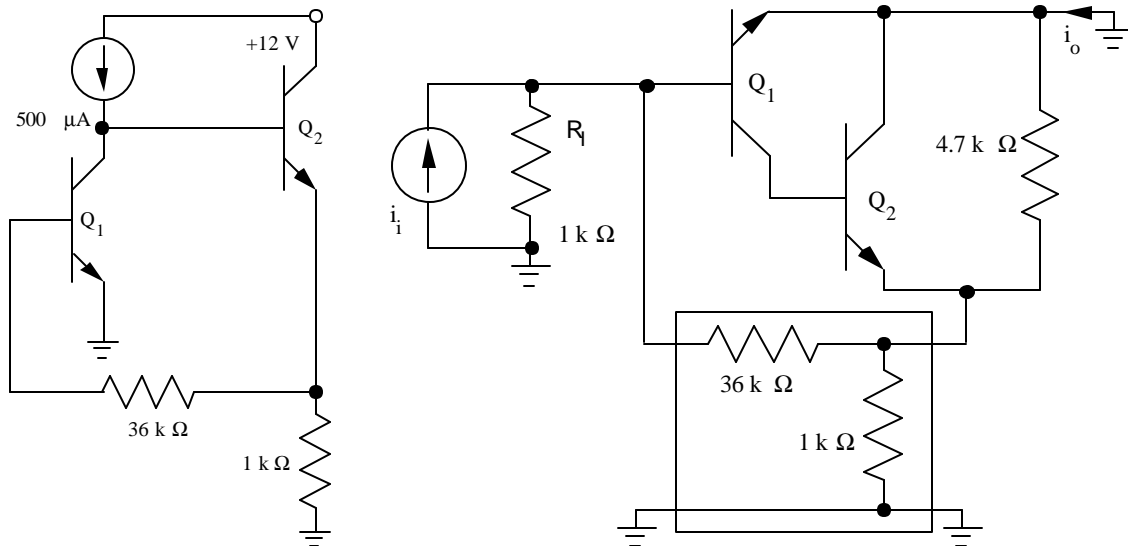

$$I_{C1} = 500mA - I_{B2} \quad | \quad I_{E2} = I_{B1} + \frac{36000I_{B1} + 0.7}{1000} = 37I_{B1} + 700mA \quad | \quad I_{B2} = \frac{I_{E2}}{101}$$

$$I_{C1} = 500mA - \frac{37I_{B1} + 700mA}{101} = 493mA - 0.366I_{B1} \rightarrow I_{C1} = 491.2mA$$

$$I_{E2} = 37 \frac{I_{C1}}{100} + 700mA = 881.7mA \quad | \quad I_{C2} = \frac{100}{101} I_{E2} = 873mA$$

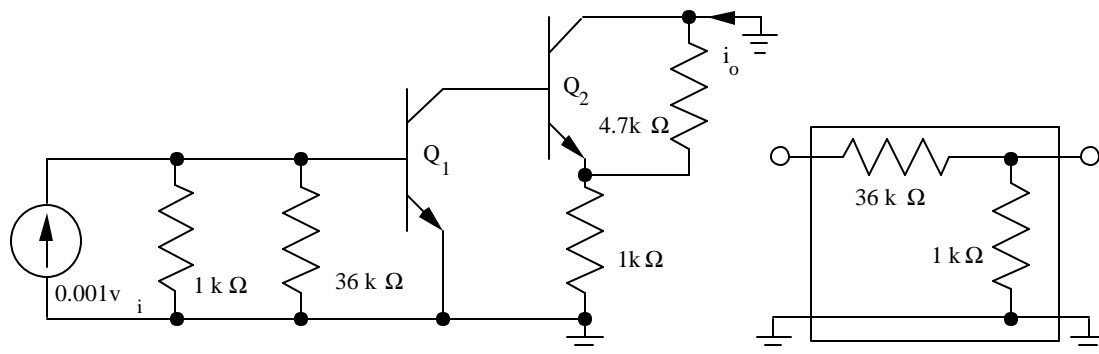

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{37 \text{ k}\Omega} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = 36 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 973 \text{ }\Omega \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = -\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 36 \text{ k}\Omega} = -\frac{1}{37}$$

$$1 \text{ k}\Omega \parallel 37 \text{ k}\Omega = 974 \text{ }\Omega \quad | \quad r_{p1} = \frac{100(0.025)}{491 \text{ mA}} = 5.09 \text{ k}\Omega \quad | \quad r_{p2} = \frac{100(0.025)}{873 \text{ mA}} = 2.86 \text{ k}\Omega$$

$$A = \frac{i_o}{i_i} = -\frac{974 \text{ }\Omega}{974 \text{ }\Omega + 5090 \text{ }\Omega} (-100)(101) \left(\frac{4700 \text{ }\Omega}{973 \text{ }\Omega + 4700 \text{ }\Omega} \right) = -1340$$


$$A_i = \frac{A}{1 + A\mathbf{b}} = \frac{-1340}{1 + (-1340) \left(-\frac{1}{37} \right)} = \frac{-1340}{37.2} = -36.0 \quad | \quad 1 + A\mathbf{b} = 37.2$$

$$A_v = \frac{v_o}{v_i} = \frac{973 i_o}{1000 i_i} = 0.973 \frac{i_o}{i_i} = -35.0$$

$$R_{in} = \frac{(1 \text{ k}\Omega \parallel 37 \text{ k}\Omega \parallel r_{p1})}{1 + A\mathbf{b}} = \frac{(1 \text{ k}\Omega \parallel 37 \text{ k}\Omega \parallel 5.09 \text{ k}\Omega)}{37.2} = 22.0 \text{ }\Omega \quad | \quad r_{ol} = \frac{50 + 1.6}{493 \times 10^{-6}} = 105 \text{ k}\Omega$$

$$R_{out} = \frac{\left(1 \text{ k}\Omega \parallel 36 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega \parallel \frac{r_{p2} + r_{ol}}{101} \right)}{1 + A\mathbf{b}} = \frac{\left(1 \text{ k}\Omega \parallel 36 \text{ k}\Omega \parallel 4.7 \text{ k}\Omega \parallel \frac{5.09 \text{ k}\Omega + 105 \text{ k}\Omega}{101} \right)}{37.2} = 12.5 \text{ }\Omega$$

18.33

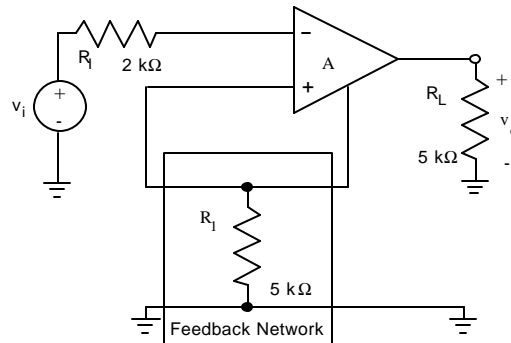

$$z_{11}^F = \left. \frac{v_1}{i_1} \right|_{i_2=0} = 5 \text{ k}\Omega \quad | \quad z_{22}^F = \left. \frac{v_2}{i_2} \right|_{i_1=0} = 5 \text{ k}\Omega \quad | \quad \mathbf{b} = z_{12}^F = \left. \frac{v_1}{i_2} \right|_{i_1=0} = 5 \text{ k}\Omega$$

$$z_{11}^T = 5 \text{ k}\Omega + 15 \text{ k}\Omega = 20 \text{ k}\Omega \quad | \quad z_{22}^T = 5 \text{ k}\Omega + 1 \text{ k}\Omega = 6 \text{ k}\Omega \quad | \quad z_{21}^A = \left. \frac{v_2}{i_1} \right|_{i_2=0} = 15 \text{ k}\Omega (5000) = 75 \text{ M}\Omega$$


$$A = \frac{z_{21}^A}{(R_i + z_{11}^T)(z_{22}^T + R_L)} = \frac{75 \text{ M}\Omega}{(2 \text{ k}\Omega + 20 \text{ k}\Omega)(6 \text{ k}\Omega + 5 \text{ k}\Omega)} = 0.310 \text{ S}$$

$$A_{ic} = \frac{A}{1 + A\mathbf{b}} = \frac{0.310}{1 + 0.310(5 \text{ k}\Omega)} = 2.00 \times 10^{-4} \text{ S} \quad | \quad A\mathbf{b} = 1550$$

$$\text{Note : } R_{in} = (R_i + z_{11}^T)(1 + A\mathbf{b}) = (22 \text{ k}\Omega)(1551) = 34.1 \text{ M}\Omega$$

$$R_{out} = (z_{22}^T + R_L)(1 + A\mathbf{b}) = (11 \text{ k}\Omega)(1551) = 17.1 \text{ M}\Omega$$

18.34

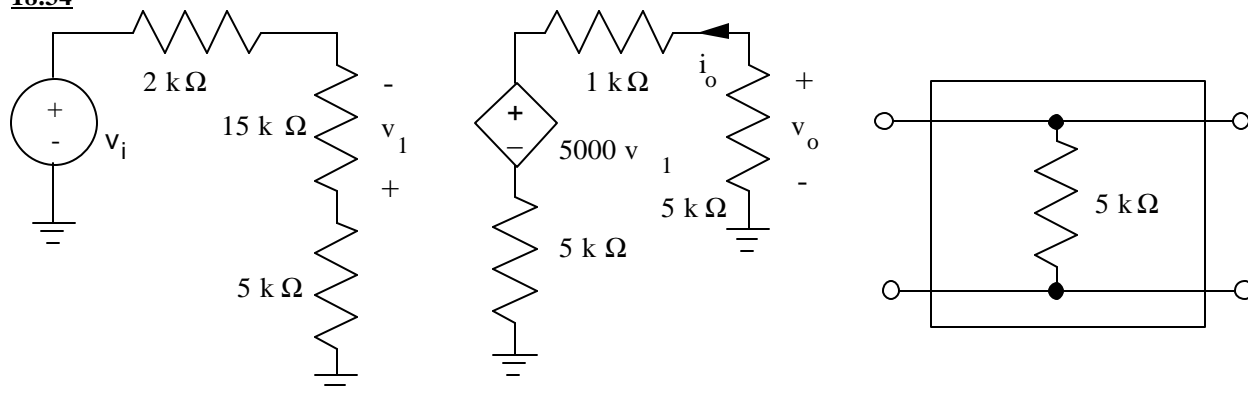

$$z_{11}^F = \frac{v_1}{i_1} \bigg|_{i_2=0} = 5 \text{ k}\Omega \quad | \quad z_{22}^F = \frac{v_2}{i_2} \bigg|_{i_1=0} = 5 \text{ k}\Omega \quad | \quad \mathbf{b} = z_{12}^F = \frac{v_1}{i_2} \bigg|_{i_1=0} = 5 \text{ k}\Omega$$


$$\mathbf{A} = \frac{i_o}{v_s} = \frac{15 \text{ k}\Omega}{2 \text{ k}\Omega + 15 \text{ k}\Omega + 5 \text{ k}\Omega} \left(\frac{5000}{5 \text{ k}\Omega + 1 \text{ k}\Omega + 5 \text{ k}\Omega} \right) = 0.310$$

$$\mathbf{A}_{tr} = \frac{i_o}{v_s} = \frac{\mathbf{A}}{1 + \mathbf{A}\mathbf{b}} = \frac{0.310}{1 + 0.310(5000)} = 0.200 \text{ mS} \quad | \quad \frac{v_o}{v_s} = -5000 \frac{i_o}{v_s} = -1.00 \quad | \quad 1 + \mathbf{A}\mathbf{b} = 1550$$

$$R_{in} = (2 \text{ k}\Omega + 15 \text{ k}\Omega + 5 \text{ k}\Omega)(1 + \mathbf{A}\mathbf{b}) = (22 \text{ k}\Omega)(1550) = 34.1 \text{ M}\Omega$$

$$R_{out} = (5 \text{ k}\Omega + 1 \text{ k}\Omega + 5 \text{ k}\Omega)(1 + \mathbf{A}\mathbf{b}) = (11 \text{ k}\Omega)(1550) = 17.1 \text{ M}\Omega$$

18.35

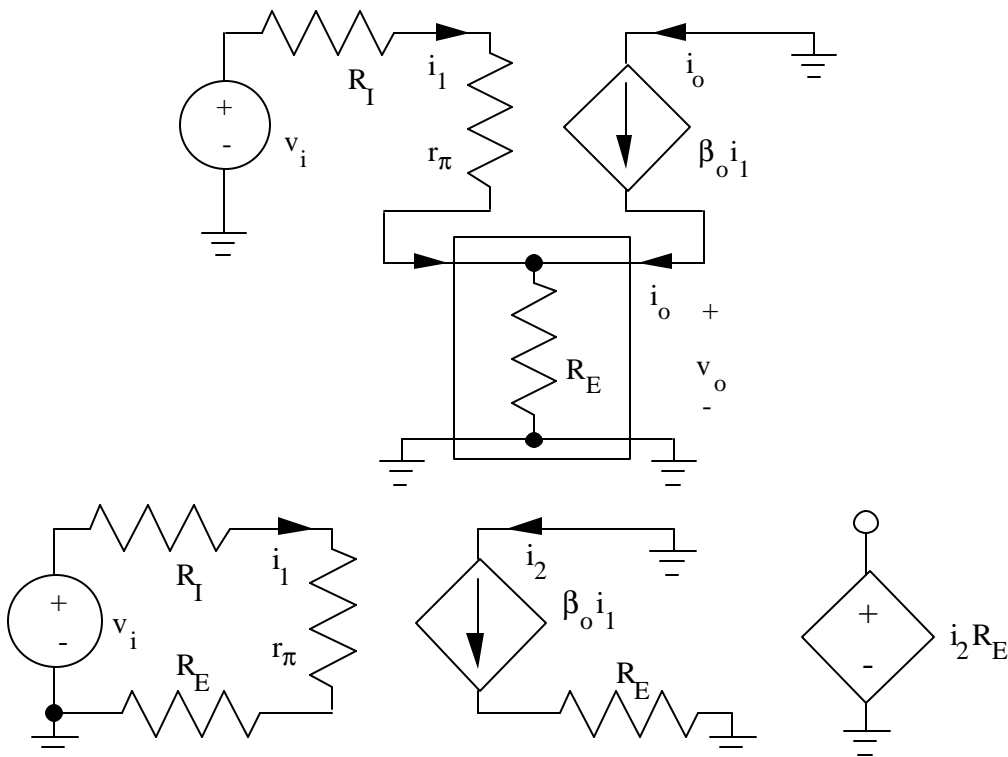

By carefully drawing the circuit, it can be represented as a series-series feedback amplifier. In particular, r_π and the current generator are connected within the feedback network.

$$A = \frac{i_2}{v_s} = \frac{b_o}{R_S + r_p + R_E} \quad | \quad b = z_{12}^F = R_E$$

$$A_{tc} = \frac{i_o}{v_s} = \frac{A}{1 + Ab} = \frac{\frac{b_o}{R_S + r_p + R_E}}{1 + \frac{b_o}{R_S + r_p + R_E} R_E} = \frac{b_o}{R_S + r_p + (b_o + 1)R_E}$$

$$A_v = \frac{v_o}{v_s} = \frac{i_o}{v_s} \frac{R_E}{a_o} = \frac{b_o}{R_S + r_p + (b_o + 1)R_E} \frac{(b_o + 1)R_E}{b_o} = \frac{(b_o + 1)R_E}{R_S + r_p + (b_o + 1)R_E}$$

$$R_{in} = R_{in}^A (1 + Ab) = (R_S + r_p + R_E) \left(1 + \frac{b_o}{R_S + r_p + R_E} R_E \right) = R_S + r_p + (b_o + 1)R_E$$


Both answers agree with our previous direct derivations.

18.36

$$A_v = \frac{b_o R_L}{R_S + r_p + (b_o + 1)R_E} = \frac{b_o R_L}{R_S + r_p + R_E + b_o R_E}$$


$$A_v = \frac{\frac{b_o}{R_S + r_p + R_E} R_L}{1 + \frac{b_o}{R_S + r_p + R_E} R_E} = \frac{A_{tc} R_L}{1 + A_{tc} b}$$

$$A_{tc} = \frac{b_o}{R_S + r_p + R_E} \quad | \quad b = R_E$$

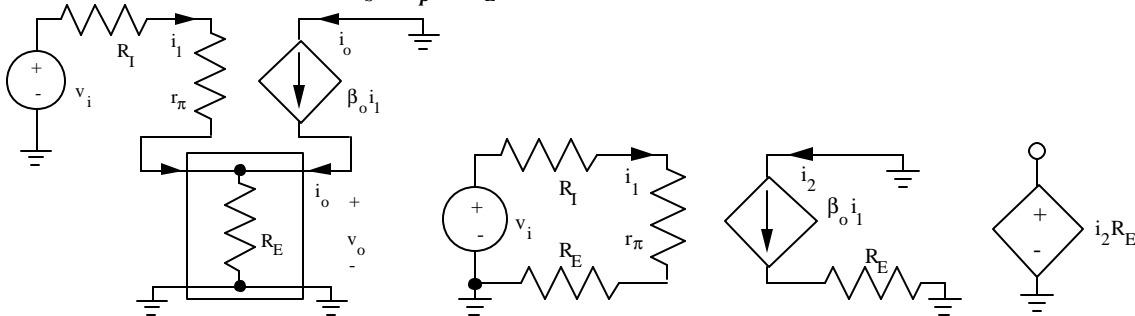

By carefully drawing the circuit, it can be represented as a series-series feedback amplifier. In particular, r_π and the current generator are connected within the feedback network.

18.37

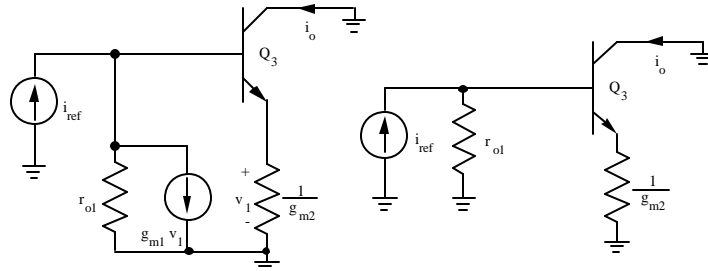

$$g_{11}^F = \left. \frac{i_1}{v_1} \right|_{i_2=0} = \frac{1}{r_{o1}} \quad | \quad g_{22}^F = \left. \frac{v_2}{i_2} \right|_{v_1=0} = \frac{1}{g_{m2}} \quad | \quad g_{12}^F = \left. \frac{i_1}{i_2} \right|_{v_1=0} = \frac{g_{m1}}{g_{m2}} \cong 1$$


$$i_o = i_{ref} r_{o1} \frac{b_o}{r_{o1} + r_{p3} + (b_{o3} + 1) \frac{1}{g_{m2}}} \approx i_{ref} \frac{b_o r_{o1}}{r_{o1} + 2r_{p3} + \frac{1}{g_{m2}}} \quad | \quad A = \frac{i_o}{i_{ref}} = \frac{b_o m_f}{m_f + 2b_o + 1} \approx b_o$$

$$A_i = \frac{A}{1 + Ab} = \frac{b_o}{1 + b_o(1)} = a_o \approx 1 \text{ which is correct.}$$

$$R_{in} = \frac{r_{o1} \left\| \left(r_{p3} + (b_{o3} + 1) \frac{1}{g_{m2}} \right) \right.}{1 + b_o} \approx \frac{2r_p}{b_o} = \frac{2}{g_m} \text{ which is correct.}$$

$$R_{out} = (1 + b_o) r_{o3} \left(1 + \frac{b_{o3} \frac{1}{g_{m2}}}{r_{o1} + r_{p3} + \frac{1}{g_{m2}}} \right) = (1 + b_o) r_o \left(1 + \frac{b_o}{m_f + b_o + 1} \right) \approx b_o r_o - \text{not correct!}$$

18.38

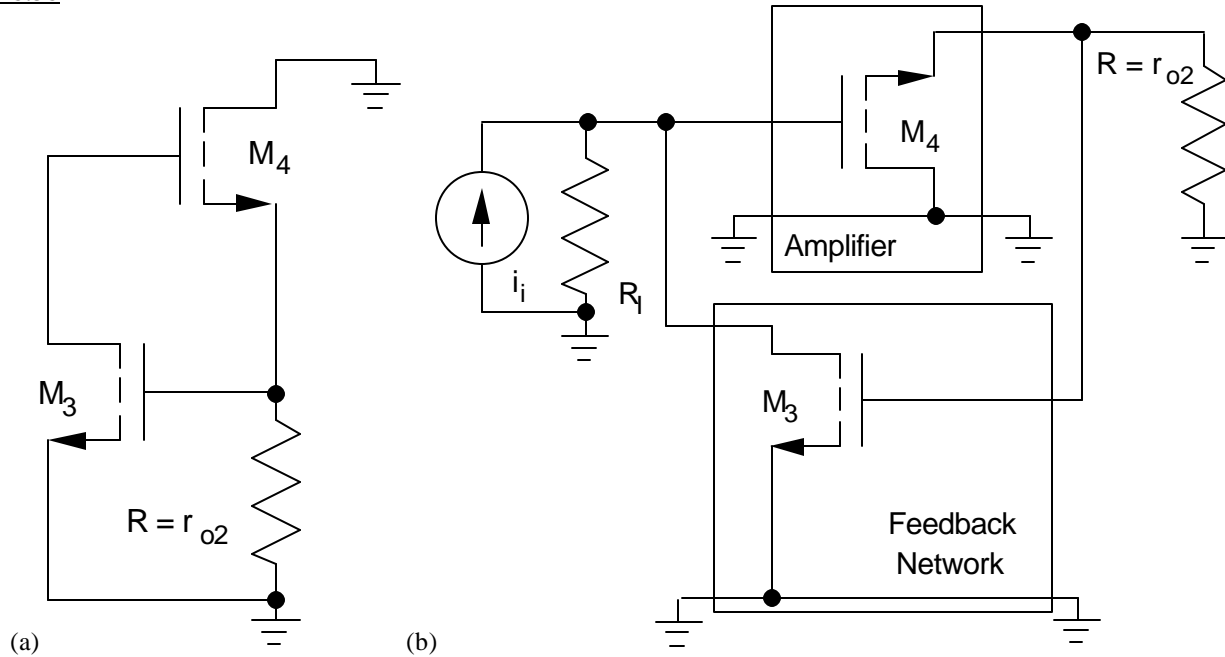


(c) Yes, see figure.

$$A_{(i)} = r_{o3} \frac{g_{m4} r_{o2}}{1 + g_{m4} r_{o2}} \frac{1}{r_{o2}} \cong \frac{r_{o3}}{r_{o2}} \quad | \quad b = g_{m3} r_{o2} \quad | \quad Ab = g_{m3} r_{o3} = m_{f3}$$

$$R_{out}^A = m_{f4} r_{o2} \quad | \quad R_{out} = R_{out}^A (1 + Ab) = m_{f4} (1 + m_{f3}) r_{o2}$$

$$\text{Also, } R_{in}^A = r_{o3} \quad | \quad R_{in} = \frac{R_{in}^A}{(1 + Ab)} = \frac{r_{o3}}{1 + m_{f3}} \cong \frac{1}{g_{m3}}$$

(d)

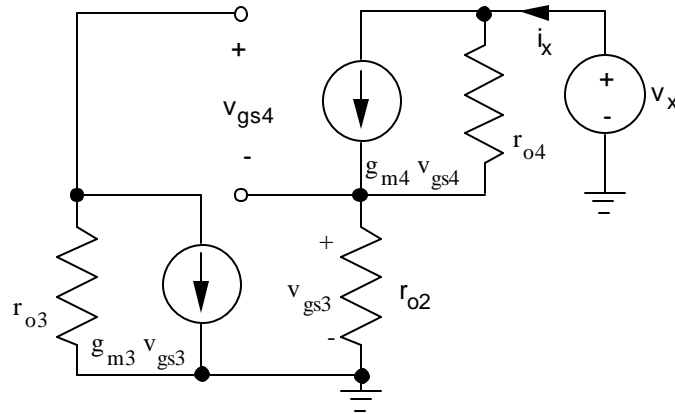


$$v_x = (i_x - g_{m4}v_{gs4})r_{o4} + i_x r_{o2} \quad | \quad v_{gs4} = (-m_{f3}v_{gs3} - v_{gs3}) = -i_x r_{o2} (m_{f3} + 1)$$

$$v_x = i_x r_{o4} + i_x r_{o2} + g_{m4} r_{o4} (1 + m_{f3}) i_x r_{o2} \quad | \quad R_{out} = m_{f4} (1 + m_{f3}) r_{o2}$$

(e)

$$m_f = g_m r_o \cong \sqrt{2(0.75 \times 10^{-3})(10^{-4})} \left[\frac{50 + 8}{(10^{-4})} \right] = (0.387 \text{ mS})(580 \text{ k}\Omega) = 194$$

$$R_{out} = m_{f4} (1 + m_{f3}) r_{o2} = 194(195)(580 \text{ k}\Omega) = 21.9 \text{ G}\Omega$$

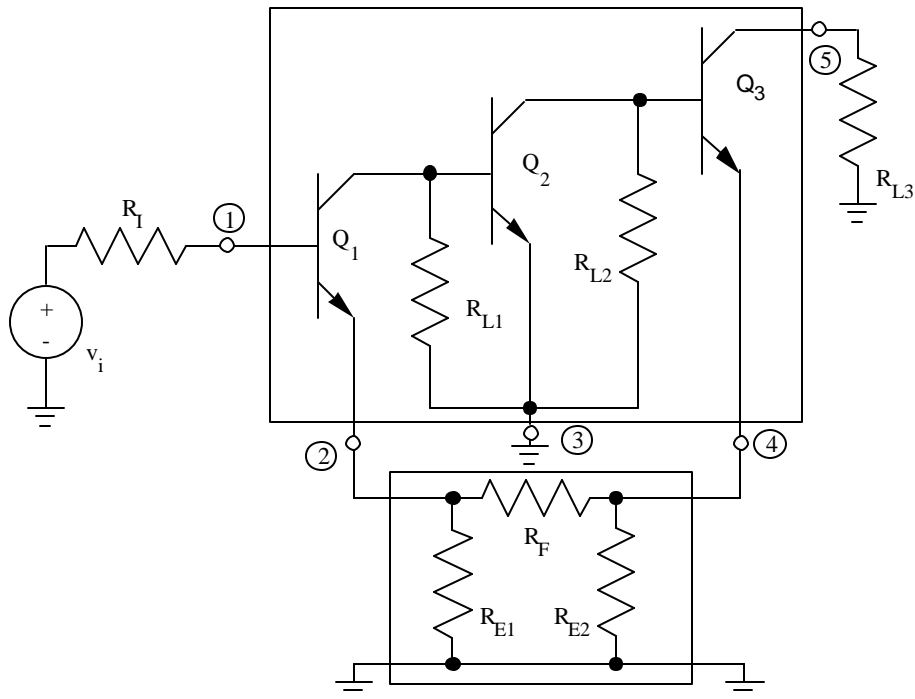(f) SPICE yields 28.0 G Ω with the formula above using the parameter values from SPICE.**18.39**

The amplifier is not a two-port. It has five separate terminals. It can be analyzed correctly as a series-shunt configuration with the output defined at terminal 4. In the series-shunt configuration, R_L is absorbed into the amplifier thereby making it a two-port.


18.40

$$T = \frac{v_o}{v_x} = g_{m2}(r_{o2} \parallel r_{o4}) \frac{(b_o + 1)R}{(r_{o2} \parallel r_{o4}) + r_{p3} + (b_o + 1)R} \quad | \quad g_{m1} = 40(10^{-4}) = 4.00 \text{ mS}$$

$$r_{o2} = \frac{50 + 1.4}{10^{-4}} = 514 \text{ k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613 \text{ k}\Omega \quad | \quad r_{p3} = \frac{100(0.025)}{(12 \text{ V} / 10 \text{ k}\Omega)} = 2.08 \text{ k}\Omega$$

$$T = (4 \times 10^{-3})(280 \text{ k}\Omega) \frac{(101)10 \text{ k}\Omega}{280 \text{ k}\Omega + 2.08 \text{ k}\Omega + 101(10 \text{ k}\Omega)} = 876 \quad (58.9 \text{ dB})$$

18.41

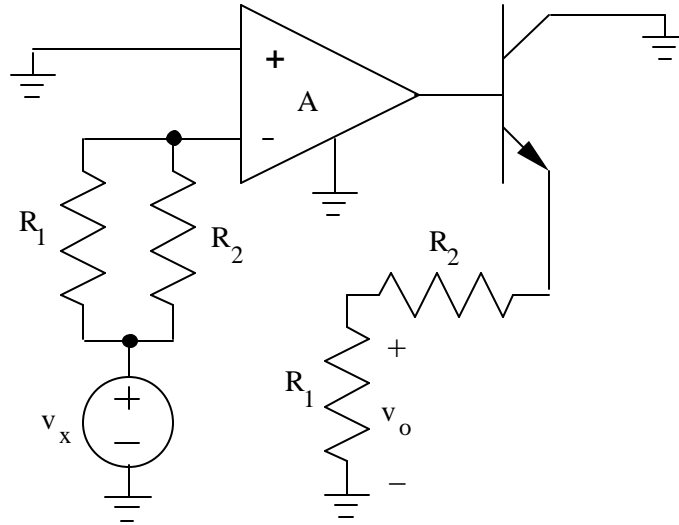

Note: The loading effects of the feedback network must be carefully included.


$$R_1 \parallel R_2 = 1 \text{ k}\Omega \parallel 7.5 \text{ k}\Omega = 882 \Omega \quad | \quad r_p = \frac{100(0.025 \text{ V})}{198 \text{ mA}} = 12.6 \text{ k}\Omega$$

$$T = \frac{v_o}{v_x} = \frac{R_{ID}}{R_{ID} + 882 \Omega} (A) \frac{(b_o + 1)(R_1 + R_2)}{R_o + r_p + (b_o + 1)(R_1 + R_2)} \left(\frac{R_1}{R_1 + R_2} \right)$$

$$T = \frac{v_o}{v_x} = \frac{40 \text{ k}\Omega}{40 \text{ k}\Omega + 882 \Omega} (316) \frac{(101)(8.5 \text{ k}\Omega)}{1 \text{ k}\Omega + 12.6 \text{ k}\Omega + (101)(8.5 \text{ k}\Omega)} \left(\frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 7.5 \text{ k}\Omega} \right) = 35.8$$

which agrees with the result in Prob. 18.18.

18.42

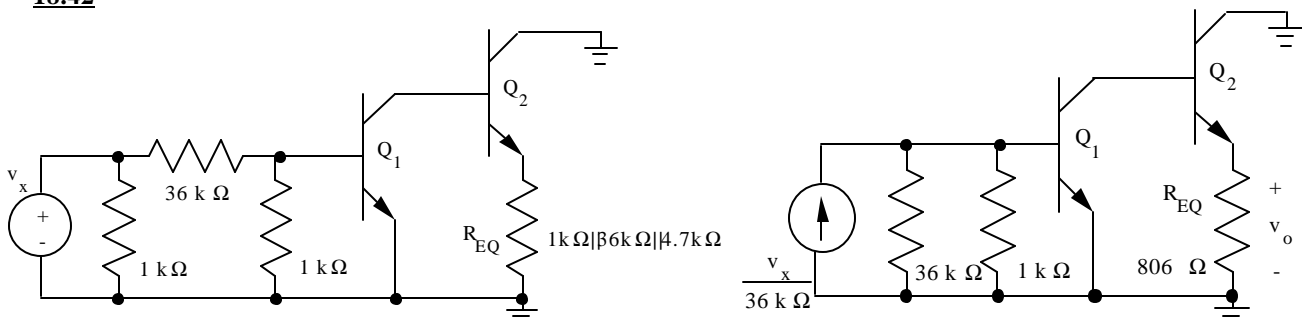

$$y_{11}^F = \left. \frac{i_1}{v_1} \right|_{v_2=0} = \frac{1}{36k\Omega} \quad | \quad y_{22}^F = \left. \frac{i_2}{v_2} \right|_{v_1=0} = \frac{1}{36k\Omega \parallel 1k\Omega} \quad | \quad y_{12}^F = \left. \frac{i_1}{v_2} \right|_{v_1=0} = -\frac{1}{36k\Omega}$$

$$r_{p1} = \frac{100(0.025)}{491mA} = 5.09k\Omega \quad | \quad r_{p2} = \frac{100(0.025)}{873mA} = 2.86k\Omega \quad | \quad r_{o1} = \frac{50+1.6}{493 \times 10^{-6}} = 105k\Omega$$

$$T = \frac{v_o}{v_s} = \frac{1}{36k\Omega} (1k\Omega \parallel 36k\Omega \parallel r_{p1}) g_{m1} \left[r_{o1} \parallel (r_{p2} + (b_o + 1)R_{EQ}) \right] \frac{r_{p2} + (b_o + 1)R_{EQ}}{r_{o1} + r_{p2} + (b_o + 1)R_{EQ}}$$

$$\frac{(1k\Omega \parallel 36k\Omega \parallel r_{p1})}{36k\Omega} = \frac{(1k\Omega \parallel 36k\Omega \parallel 5.09k\Omega)}{36k\Omega} = 0.0227 \quad | \quad g_m = 40(491mA) = 19.6mS$$


$$\left[r_{o1} \parallel (r_{p2} + (b_o + 1)R_{EQ}) \right] = \left[105k\Omega \parallel (2.86k\Omega + (101)806\Omega) \right] = 46.8k\Omega$$

$$\frac{r_{p2} + (b_o + 1)R_{EQ}}{r_{o1} + r_{p2} + (b_o + 1)R_{EQ}} = \frac{2.86k\Omega + (101)806\Omega}{105k\Omega + 2.86k\Omega + (101)806\Omega} = 0.430$$

$$T = (0.0227)(19.6mS)(46.8k\Omega)(0.430) = 8.95$$

These results agree with those of Prob. 18.23.


18.43

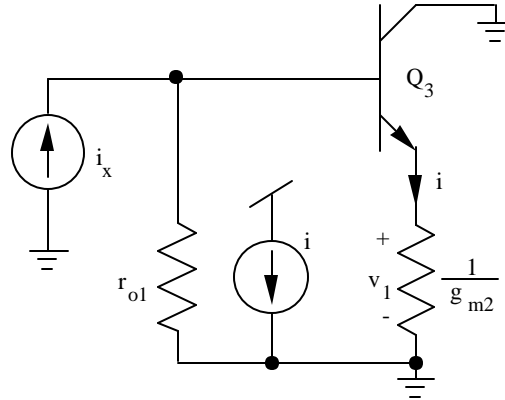

$$T = \frac{i_o}{i_x} = (b_o + 1) \frac{r_o}{r_o + r_p + (b_o + 1) \frac{1}{g_m}} = \frac{(b_o + 1)m_f}{m_f + 2b_o + 1} = \frac{(101)(2000)}{2000 + 200 + 1} = 91.8$$

These results agree with those of Prob. 18.27.

18.44

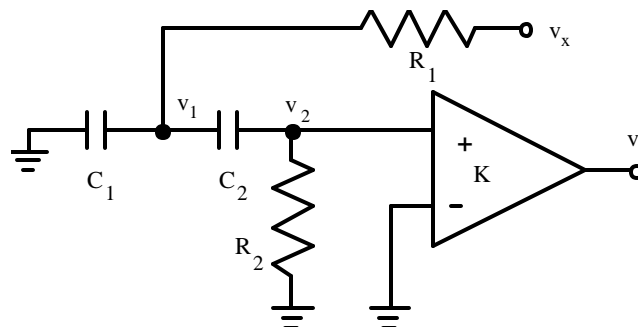


$$\begin{bmatrix} G_1 V_x \\ 0 \end{bmatrix} = \begin{bmatrix} s(C_1 + C_2) + G_1 & -sC_2 \\ -sC_2 & sC_2 + G_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad V_o = KV_2$$

$$\Delta = s^2 C_1 C_2 + s[C_1 G_2 + C_2(G_1 + G_2)] + G_1 G_2$$

$$T = \frac{V_o}{V_x} = K \frac{s \frac{1}{R_1 C_1}}{s^2 + s \left[\frac{1}{R_2 C_2} + \frac{1}{(R_1 \parallel R_2) C_1} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

18.45

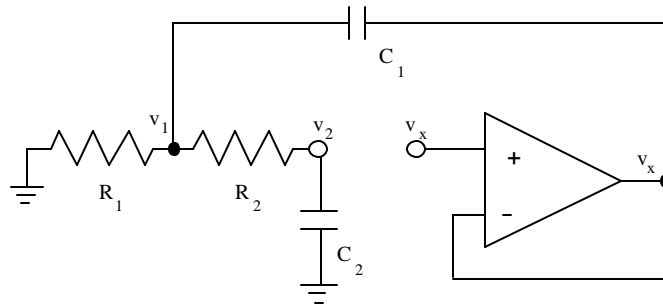

$$\begin{bmatrix} sC_1 V_x \\ 0 \end{bmatrix} = \begin{bmatrix} sC_1 + G_1 + G_2 & -G_2 \\ -G_2 & sC_2 + G_2 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad V_2 = \frac{sC_1 G_2}{\Delta} V_x$$

$$\Delta = s^2 C_1 C_2 + s[C_1 G_2 + C_2(G_1 + G_2)] + G_1 G_2$$

$$T = \frac{V_2}{V_x} = \frac{\frac{s}{R_2 C_2}}{s^2 + s \left[\frac{1}{R_2 C_2} + \frac{1}{(R_1 \parallel R_2) C_1} \right] + \frac{1}{R_1 R_2 C_1 C_2}}$$

18.46

*Problem 18.46 - Fig. 18.75 BJT Op-amp
VCC 8 0 DC 12
VEE 9 0 DC -12
IS 2 9 DC 200U
VS 1 0 DC 0
Q1 4 1 2 NBJT
Q2 5 3 2 NBJT
Q3 4 4 8 PBJT
Q4 5 4 8 PBJT
Q5 8 5 6 NBJT
R 6 9 10K
VB 7 3 DC 0
VX 7 6 AC 0
IX 0 7 AC 1
*VX 7 6 AC 1
*IX 0 7 AC 0
.MODEL NBJT NPN BF=100 VA=50 IS=1E-15
.MODEL PBJT PNP BF=100 VA=50 IS=1E-15
.OP

.AC LIN 1 10 10

.PRINT AC IM(VX) IP(VX) IM(VB) IP(VB) VM(7) VP(7) VM(6) VP(6)

Results: I(VX) = 1.000 A, I(VB) = 3.703 x 10⁻⁵ A, V(7) = 1.188 mV, V(6) = -1.000 V

$$T_v = -\frac{-.9988V}{1.188mV} = 841 \quad | \quad T_i = \frac{1.000A}{37.03mA} = 2.70 \times 10^4$$

$$T = \frac{T_v T_i - 1}{2 + T_v + T_i} = \frac{841(2.70 \times 10^4) - 1}{2 + 841 + 2.70 \times 10^4} = 816 \quad | \quad \frac{R_2}{R_1} = \frac{1 + T_v}{1 + T_i} = \frac{1 + 841}{2.70 \times 10^4} = 0.0312$$

18.47

*Problem 18.47 - Fig. 18.76

VCC 4 0 DC 10

IS 5 0 DC 200U

VS 1 0 DC 0

Q1 4 3 5 NBJT

RID 1 8 40K

RO 2 3 1K

E1 2 0 1 8 316.2

R2 6 5 7.5K

R1 8 0 1K

VB 7 8 DC 0

VX 7 6 AC 0

IX 0 7 AC 1

*VX 7 6 AC 1

*IX 0 7 AC 0

.MODEL NBJT NPN BF=100 VA=50 IS=1E-15

.OP

.AC LIN 1 10 10

.PRINT AC IM(VX) IP(VX) IM(VB) IP(VB) VM(7) VP(7) VM(6) VP(6)

.END

Results: I(VX) = 0.9759 A, I(VB) = 0.0241 A, V(7) = 3.078 mV, V(6) = -0.9969 V

$$T_v = -\frac{-.9969V}{3.078mV} = 324 \quad | \quad T_i = \frac{0.9759A}{0.0241A} = 40.5 \times 10^4$$

$$T = \frac{T_v T_i - 1}{2 + T_v + T_i} = \frac{324(40.5) - 1}{2 + 324 + 40.5} = 35.8 \quad | \quad \frac{R_2}{R_1} = \frac{1 + T_v}{1 + T_i} = \frac{1 + 324}{1 + 40.5} = 7.83$$

18.48 The circuit description is the same as Problem 18.47 except for the change in the values of R₁ and R₂.

R2 6 5 300K

R1 8 0 40K

Results: I(VX) = 0.9548 A, I(VB) = 45.19 mA, V(7) = 3.011 mV, V(6) = -0.9970 V

$$T_v = -\frac{-.9970V}{3.011mV} = 331 \quad | \quad T_i = \frac{0.9548A}{45.19mA} = 21.1$$

$$T = \frac{T_v T_i - 1}{2 + T_v + T_i} = \frac{331(21.1) - 1}{2 + 331 + 21.1} = 19.7 \quad | \quad \frac{R_2}{R_1} = \frac{1 + T_v}{1 + T_i} = \frac{1 + 331}{1 + 21.1} = 15.0$$

18.49

*Problem 18.49 - Fig. 18.73(b)

```

IS 0 1 DC 0
RS 1 0 1K
RID 1 0 15K
RO 2 3 1K
E1 3 4 1 0 5000
RL 2 0 4.7K
R2 4 0 1K
R1 4 6 36K
VB 7 1 DC 0
VX 7 6 AC 0
IX 0 7 AC 1
*VX 7 6 AC 1
*IX 0 7 AC 0
.OP
.AC LIN 1 10 10
.PRINT AC IM(VX) IP(VX) IM(VB) IP(VB) VM(7) VP(7) VM(6) VP(6)
.END

```

Results: $I(VX) = 0.9500 \text{ A}$, $I(VB) = 49.97 \text{ mA}$, $V(7) = 1.271 \text{ mV}$, $V(6) = -0.9987 \text{ V}$

$$T_v = -\frac{-0.9987V}{1.271mV} = 786 \quad | \quad T_i = \frac{0.9500A}{49.97mA} = 19.0$$

$$T = \frac{T_v T_i - 1}{2 + T_v + T_i} = \frac{786(19.0) - 1}{2 + 786 + 19.0} = 18.5 \quad | \quad \frac{R_2}{R_1} = \frac{1 + T_v}{1 + T_i} = \frac{1 + 786}{1 + 19.0} = 39.4$$

18.50

*Problem 18.50

```

VCC 5 0 DC 6
IREF 0 1 DC 100UA
Q1 1 4 0 NBJT
Q2 4 4 0 NBJT
Q3 5 3 4 NBJT
IX 0 2 DC 0
VX1 2 1 DC 0
VX2 2 3 DC 0
.MODEL NBJT NPN BF=100 VA=50 IS=1E-15
.OP
.TF I(VX1) IX
*TF I(VX2) IX
.END

```

---> 0.9910

---> 9.043×10^{-3}

*Problem 18.50

```

VCC 5 0 DC 6
IREF 0 1 DC 100UA
Q1 1 4 0 NBJT
Q2 4 4 0 NBJT
Q3 5 3 4 NBJT
IX 0 2 DC 0
VX1 2 1 DC 0
VX2 2 3 DC 0
.MODEL NBJT NPN BF=100 VA=50 IS=1E-15
.OP
.TF V(1) VX1
*TF V(2) VX1
.END

```

---> -0.9990

---> 1.012×10^{-3}

$$T_v = -\frac{-0.9990}{1.012 \times 10^{-3}} = 987 \quad | \quad T_i = \frac{0.9910}{9.043 \times 10^{-3}} = 110$$

$$T = \frac{987(110) - 1}{2 + 987 + 110} = 98.8 \quad | \quad \frac{R_2}{R_1} = \frac{1 + 987}{1 + 110} = 8.90$$

18.51 Since the output resistance of the amplifier is zero ($R_2 = 0$), the simplified method can be used: $T = T_v$.

*Problem 18.51

VS 1 0 DC 0

C1 1 2 0.005UF

C2 2 3 0.005UF

R1 2 7 2K

R2 3 0 2K

E1 4 0 3 0 1

R 4 5 31.83

C 5 0 1NF

E2 6 0 5 0 2


VX 7 6 AC 1

.OP

.AC DEC 100 1 1E6

.PROBE V(6) V(7)

.END

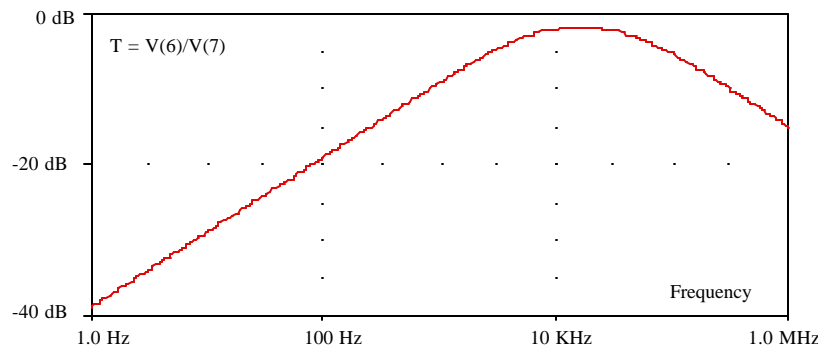

18.52 (a) For Fig. 18.73(a), use values from Problem 18.15.

(b) For Fig. 18.73(b), use values from Problem 18.30.

(c) For Fig. 18.73(c), use values from Problem 18.33.

(d) For Fig. 18.73(a), use values from Problem 18.21.

(a) With gain $A = 0$, $R_{inD} = R_I + R_{id} + R_1 \parallel [R_2 + R_o \parallel R_L]$

$$R_{inD} = 1k\Omega + 15k\Omega + 4.3k\Omega \parallel [39k\Omega + 1k\Omega \parallel 5.6k\Omega] = 19.9k\Omega$$

With the input open - circuited, the current in R_{id} is zero, and so $T_{OC} = 0$.

With the input set to zero, The Thevenin equivalent looking back into R_1 is

$$V_{th} = \left[5000 \left(\frac{5.6k\Omega}{5.6k\Omega + 1k\Omega} \right) \right] \left[\frac{4.3k\Omega}{4.3k\Omega + 39k\Omega + (5.6k\Omega \parallel 1k\Omega)} \right] = 413 \text{ and}$$

$$R_{th} = R_1 \parallel [R_2 + R_o \parallel R_L] = 4.3k\Omega \parallel [39k\Omega + 1k\Omega \parallel 5.6k\Omega] = 3.88k\Omega$$

$$T_{SC} = 413 \frac{15k\Omega}{3.88k\Omega + 15k\Omega + 1k\Omega} = 312 \quad | \quad R_{in} = 19.9k\Omega \left(\frac{1 + 312}{1 + 0} \right) = 6.22 \text{ M}\Omega$$

With gain $A = 0$,

$$R_{outD} = R_L \| R_o \| [R_2 + (R_1 \| (R_{id} + R_i))] = 5.6k\Omega \| 1k\Omega \| [39k\Omega + (4.3k\Omega \| (15k\Omega + 1k\Omega))] = 832\Omega$$

With the output shorted, $T_{SC} = 0$. With the output open - circuited, $T_{OC} = 312$

$$R_{out} = 832\Omega \left(\frac{1+0}{1+312} \right) = 2.66 \Omega \quad | \quad R_{in} \text{ and } R_{out} \text{ agree with both Prob. 18.18 and SPICE.}$$

(b) With gain $A = 0$,

$$R_{inD} = R_i \| R_{id} \| [R_1 + R_2 \| (R_o + R_L)] = 150k\Omega \| 15k\Omega \| [20k\Omega + 2k\Omega \| (1k\Omega + 10k\Omega)] = 8.37k\Omega$$

With the input short - circuited, $T_{SC} = 0$.

$$\text{With the input open - circuited, } T_{OC} = \frac{5000}{R_L + R_o + R_2 \| [R_1 + (R_i \| R_{id})]} \frac{R_2}{R_2 + R_1 + (R_i \| R_{id})} R_i \| R_{id}$$

$$T_{OC} = -\frac{5000}{10k\Omega + 1k\Omega + 2k\Omega \| [20k\Omega + (150k\Omega \| 15k\Omega)]} \left[\frac{2k\Omega}{2k\Omega + 20k\Omega + (150k\Omega \| 15k\Omega)} \right] (150k\Omega \| 15k\Omega) = -297$$

$$R_{in} = 8.37k\Omega \left(\frac{1+0}{1+297} \right) = 28.1 \Omega \quad | \quad \text{Since the circuit is series feed back at the output,}$$

we look into the circuit between ground and the bottom of R_L . With gain $A = 0$,

$$R_{outD} = R_L + R_o + R_2 \| [R_1 + (R_i \| R_{id})] = 10k\Omega + 1k\Omega + 2k\Omega \| [20k\Omega + (150k\Omega \| 15k\Omega)] = 12.9k\Omega$$

With the output open, $i_o = 0$, and $T_{OC} = 0$. With the output short - circuited, T_{SC} is

$$T_{SC} = -\frac{5000}{R_L + R_o + R_2 \| [R_1 + (R_i \| R_{id})]} \frac{R_2}{R_2 + R_1 + (R_i \| R_{id})} (R_i \| R_{id}) = 297$$

$$R_{out} = 12.9k\Omega \left(\frac{1+297}{1+0} \right) = 3.84 \text{ M}\Omega \quad | \quad R_{in} \text{ and } R_{out} \text{ agree with both Prob. 18.30 and SPICE.}$$

We can instead choose to look at the shunt output. With gain $A = 0$,

$$R_{outD} = R_L \| \{ R_o + R_2 \| [R_1 + (R_i \| R_{id})] \} = 10k\Omega \| \{ k\Omega + 2k\Omega \| [20k\Omega + (150k\Omega \| 15k\Omega)] \} = 2.24k\Omega$$

$$\text{With the output shorted, } T_{SC} = -\frac{5000}{R_o + R_2 \| [R_1 + (R_i \| R_{id})]} \frac{R_2}{R_2 + R_1 + (R_i \| R_{id})} R_i \| R_{id} = -1325$$

With the output open - circuited,

$$T_{OC} = -\frac{5000}{R_L + R_o + R_2 \| [R_1 + (R_i \| R_{id})]} \frac{R_2}{R_2 + R_1 + (R_i \| R_{id})} (R_i \| R_{id}) = -297$$

$$R_{out} = 2.24k\Omega \left(\frac{1+1325}{1+297} \right) = 9.967 \text{ k}\Omega \text{ and removing the } 10k\Omega \text{ resistor yields } R_{out} = 3.04 \text{ M}\Omega.$$

The error is due to loss of significance in the calculations.

If we remove R_L from across the output, $R_{outD} = 2.89k\Omega$, $T_{SC} = -1325$, and $T_{OC} = 0$.

$$R_{out} = 2.89k\Omega \left(\frac{1+1325}{1+0} \right) = 3.83 \text{ M}\Omega \quad | \quad R_{out} \text{ again agrees with both Prob. 18.30 and SPICE.}$$

(c) With gain $A = 0$,

$$R_{inD} = R_I + R_{id} + R_I \parallel (R_o + R_L) = 2k\Omega + 15k\Omega + 5k\Omega \parallel (1k\Omega + 5k\Omega) = 19.7k\Omega$$

When the input is open - circuited, zero current exists in R_{id} and $T_{OC} = 0$.

With the input short - circuited,

$$|T_{SC}| = \frac{5000}{R_L + R_o + [R_I \parallel (R_{id} + R_I)]} \left(\frac{R_I}{R_I + R_{id} + R_I} \right) R_{id}$$

$$|T_{SC}| = \frac{5000}{5k\Omega + 1k\Omega + [5k\Omega \parallel (15k\Omega + 2k\Omega)]} \left(\frac{5k\Omega}{5k\Omega + 15k\Omega + 2k\Omega} \right) 5k\Omega = 1730$$

$$R_{in} = 19.7k\Omega \left(\frac{1 + 1730}{1 + 0} \right) = 34.1 M\Omega$$

With gain $A = 0$, (remember, this is series feedback and we look into the bottom of R_L)

$$R_{outD} = R_L + R_o + [R_I \parallel (R_{id} + R_I)] = 5k\Omega + 1k\Omega + [5k\Omega \parallel (15k\Omega + 2k\Omega)] = 9.86k\Omega$$

With the output open - circuited, $T_{OC} = 0$. With the output shorted,

$$|T_{SC}| = 1730, \text{ the same as above, and } R_{out} = 9.86k\Omega \left(\frac{1 + 1730}{1 + 0} \right) = 17.1 M\Omega$$

R_{in} and R_{out} agree with both Prob. 18.33 and SPICE.

$$\text{If we take the output as the voltage at } v_o, \text{ then } |T_{SC}| = \frac{5000}{R_o + [R_I \parallel (R_{id} + R_I)]} \left(\frac{R_I}{R_I + R_{id} + R_I} \right) R_{id}$$

$$|T_{SC}| = \frac{5000}{1k\Omega + [5k\Omega \parallel (15k\Omega + 2k\Omega)]} \left(\frac{5k\Omega}{5k\Omega + 15k\Omega + 2k\Omega} \right) 15k\Omega = 3500$$

$$R_{outD} = R_L \parallel \{R_o + [R_I \parallel (R_{id} + R_I)]\} = 5k\Omega \parallel \{1k\Omega + [5k\Omega \parallel (15k\Omega + 2k\Omega)]\} = 2.47k\Omega$$

$$R_{out} = 2.47k\Omega \left(\frac{1 + 3500}{1 + 1730} \right) = 4.99 k\Omega \quad (= 5k\Omega \parallel (1731)4.86k\Omega)$$

(d) With gain $A = 0$,

$$R_{inD} = R_I \parallel R_{id} \parallel [R_F + (R_L \parallel R_o)] = 100k\Omega \parallel 15k\Omega \parallel [10k\Omega + (10k\Omega \parallel 1k\Omega)] = 5.94k\Omega$$

With the input short - circuited, $T_{SC} = 0$.

When the input is open - circuited,

$$|T_{OC}| = \left(\frac{5000}{R_o} \right) \frac{(R_L \parallel R_o)}{(R_L \parallel R_o) + R_F + (R_I \parallel R_{id})} (R_I \parallel R_{id})$$

$$|T_{OC}| = \left(\frac{5000}{1k\Omega} \right) \frac{(10k\Omega \parallel 1k\Omega)}{(10k\Omega \parallel 1k\Omega) + 10k\Omega + (100k\Omega \parallel 15k\Omega)} (100k\Omega \parallel 15k\Omega) = 2480$$

$$R_{in} = 5.94k\Omega \left(\frac{1 + 0}{1 + 2480} \right) = 2.39 \Omega$$

With gain $A = 0$,

$$R_{outD} = R_L \parallel R_o \parallel [R_F + (R_I \parallel R_{id})] = 10k\Omega \parallel 1k\Omega \parallel [10k\Omega + (100k\Omega \parallel 15k\Omega)] = 875\Omega$$

With the output short - circuited, $T_{SC} = 0$. With the output open,

$$|T_{OC}| = 2480, \text{ the same as above, and } R_{out} = 875\Omega \left(\frac{1+0}{1+2480} \right) = 0.353\Omega$$

R_{in} and R_{out} agree with both Prob. 18.21 and SPICE.

18.53

With gain $A = 0$, $R_{inD} = R_{id} + R_1 \parallel \left[R_2 + \frac{r_p + R_o}{b_o + 1} \right] \mid r_p = \frac{100(0.025V)}{200mA} = 12.5k\Omega$

$$R_{inD} = 40k\Omega + 1k\Omega \parallel \left[7.5k\Omega + \frac{12.5k\Omega + 1k\Omega}{101} \right] = 40.9k\Omega$$

With the input open - circuited, the current in R_{id} is zero, and so $T_{OC} = 0$.

With the input set to zero, the load on the emitter follower is

$$R_{LEQ} = R_2 + (R_1 \parallel R_{id}) = 7.5k\Omega + (1k\Omega \parallel 40k\Omega) = 8.48k\Omega$$

$$T_{SC} = A \frac{(b_o + 1)R_{LEQ}}{R_o + r_p + (b_o + 1)R_{LEQ}} \frac{(R_1 \parallel R_{id})}{R_2 + (R_1 \parallel R_{id})} = 316 \frac{101(8.48k\Omega)}{1k\Omega + 12.5k\Omega + 101(8.48k\Omega)} \left(\frac{0.976k\Omega}{8.48k\Omega} \right) = 35.8$$


$$R_{in} = 40.9k\Omega \left(\frac{1+35.8}{1+0} \right) = 1.51M\Omega$$

With gain $A = 0$, $R_{outD} = [R_2 + (R_1 \parallel R_{id})] \parallel \left(\frac{r_p + R_o}{b_o + 1} \right) = 8.48k\Omega \parallel 134\Omega = 132\Omega$

With the output shorted, $T_{SC} = 0$. With the output open - circuited, $T_{OC} = 32.0$.

$$R_{out} = 132\Omega \left(\frac{1+0}{1+35.8} \right) = 3.59\Omega \mid R_{in} \text{ and } R_{out} \text{ agree with both Prob. 18.18 and SPICE.}$$

18.54

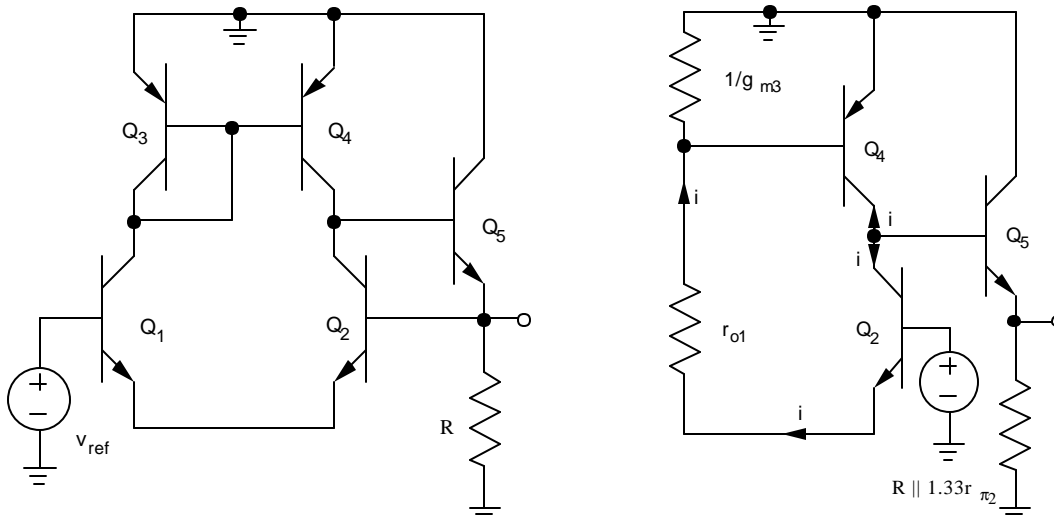

$R_{inD} = 4r_{p1} = 100k\Omega$ (See analysis below **.)

With the input shorted, $T_{SC} = g_{m2} [r_{o2} \parallel r_{o4} \parallel (b_{o5} + 1)(R \parallel 1.33r_{p2})] \Omega \left[\frac{(b_{o5} + 1)(R \parallel 1.33r_{p2})}{r_{p5} + (b_{o5} + 1)(R \parallel 1.33r_{p2})} \right]$

$$A_{vef} = \frac{(b_{o5} + 1)(R \parallel 1.33r_{p2})}{r_{p5} + (b_{o5} + 1)(R \parallel 1.33r_{p2})} = \frac{(101)(10k\Omega \parallel 33.3k\Omega)}{2.08k\Omega + (101)(10k\Omega \parallel 33.3k\Omega)} = 0.997$$

$$T_{SC} = 40(100mA) [500k\Omega \parallel 500k\Omega \parallel (101)(10k\Omega \parallel 33.3k\Omega)] (0.997) = 757$$

With the input open, $T_{OC} \cong -\frac{2i}{v_i} (r_{o2} \parallel r_{o4}) A_{vef} \cong -\frac{2}{r_{o1} + \frac{1}{g_{m3}}} (r_{o2} \parallel r_{o4}) A_{vef} \cong -\frac{2}{r_{o1}} (r_{o2} \parallel r_{o4}) (0.997) \cong -0.997$


$$R_{in} = 100k\Omega \left(\frac{1 + 757}{1 + 0.997} \right) = 38.0M\Omega$$

$$R_{outD} = R \parallel 1.33r_{p1} \parallel \frac{r_{p5} + (r_{o2} \parallel r_{o4})}{b_{o5} + 1} = 10k\Omega \parallel 33.3k\Omega \parallel \frac{2.08k + (500k\Omega \parallel 500k\Omega)}{101} = 1.88k\Omega$$

With the output open, $T_{OC} = 757$. With the output shorted, $T_{SC} = 0$

$$R_{in} = 1.88k\Omega \left(\frac{1 + 0}{1 + 757} \right) = 2.48\Omega.$$

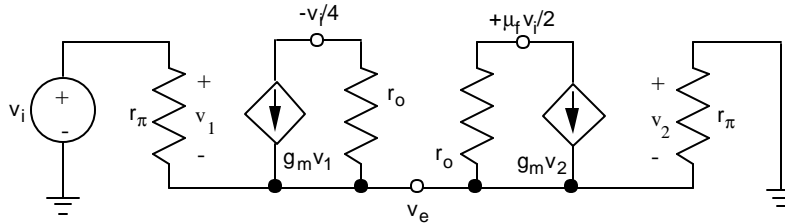The values of R_{in} and R_{out} agree well with simulation when the effect of imbalance due to offset voltage is considered. (Try a buffered current mirror in SPICE.)



** The input resistance to the differential pair with active load is $4r_p$ rather than the $2r_p$ that one might expect. Because of the high gain ($\mu_f/2$) to the output node, a significant current is fed back through r_{o2} . At the emitter node :

$$g_p(v_i - v_e) + g_m(v_i - v_e) + g_m(0 - v_e) + g_p(0 - v_e) + g_o \left(\frac{\mu_f}{2} v_i - v_e \right) + g_o \left(-\frac{v_i}{4} - v_e \right) = 0$$

$$\left(\frac{3}{2} g_m + g_p - \frac{g_o}{4} \right) v_i = (2g_m + 2g_p + 2g_o) v_e \quad \left| \quad \frac{v_e}{v_i} = \frac{\left(\frac{3}{2} g_m + g_p + \frac{g_o}{2} \right)}{(2g_m + 2g_p + 2g_o)} \cong \frac{3}{4} \right.$$

The voltage across r_p of the input transistor is $\frac{v_i}{4}$, so $R_{in} \cong 4r_p$. If an input is applied to the

right side instead of the left, the sign changes on the $g_o \frac{\mu_f}{2} v_i$ term, and $R_{in} \cong \frac{4}{3} r_p$.

18.55

$$I_{C1} = 500\text{mA} - I_{B2} \quad | \quad I_{E2} = I_{B1} + \frac{36000I_{B1} + 0.7}{1000} = 37I_{B1} + 700\text{mA} \quad | \quad I_{B2} = \frac{I_{E2}}{101}$$

$$I_{C1} = 500\text{mA} - \frac{37I_{B1} + 700\text{mA}}{101} = 493\text{mA} - 0.366I_{B1} \rightarrow I_{C1} = 491.2\text{mA}$$

$$I_{E2} = 37 \frac{I_{C1}}{100} + 700\text{mA} = 881.7\text{mA} \quad | \quad I_{C2} = \frac{100}{101} I_{E2} = 873\text{mA} \quad | \quad g_{m1} = 40(491.2\text{mA}) = 19.6\text{mS}$$

$$r_{p1} = \frac{100(0.025)}{491\text{mA}} = 5.09\text{k}\Omega \quad | \quad r_{p2} = \frac{100(0.025)}{873\text{mA}} = 2.86\text{k}\Omega \quad | \quad r_{o1} = \frac{50 + 1.6}{493 \times 10^{-6}} = 105\text{k}\Omega$$

After replacing v_i and R_i with their Norton equivalent, and with $g_{m1} = 0$,

$$R_{inD} = R_i \parallel r_{p1} \parallel \left[R_F + R_E \parallel R_L \parallel \left(\frac{r_{p2} + r_{o1}}{b_{o2} + 1} \right) \right]$$

$$R_{inD} = 1\text{k}\Omega \parallel 5.09\text{k}\Omega \parallel \left[36\text{k}\Omega + 1\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel \left(\frac{2.86\text{k}\Omega + 105\text{k}\Omega}{101} \right) \right] = 817\Omega$$

With the input shorted, $T_{SC} = 0$. With the input open and starting at the output of Q_1 ,

$$T_{OC} = (-g_{m1}r_{o1}) \left\{ \frac{(b_{o2} + 1)[R_E \parallel R_L \parallel (R_F + R_i \parallel r_{p1})]}{r_{o1} + r_{p2} + (b_{o2} + 1)[R_E \parallel R_L \parallel (R_F + R_i \parallel r_{p1})]} \right\} \left[\frac{(R_i \parallel r_{p1})}{R_F + (R_i \parallel r_{p1})} \right]$$

$$T_{OC} = (-2062) \left\{ \frac{(101)[1\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel (36\text{k}\Omega + 1\text{k}\Omega \parallel 5.09\text{k}\Omega)]}{105\text{k}\Omega + 2.86\text{k}\Omega + (101)[1\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel (36\text{k}\Omega + 1\text{k}\Omega \parallel 5.09\text{k}\Omega)]} \right\} \left[\frac{1\text{k}\Omega \parallel 5.09\text{k}\Omega}{36\text{k}\Omega + (1\text{k}\Omega \parallel 5.09\text{k}\Omega)} \right]$$

$$T_{OC} = (-2062)(0.403)(0.0227) = -18.9$$

$$R_{in} = 817\Omega \left(\frac{1 + 0}{1 + 18.9} \right) = 41.2\Omega$$

$$R_{outD} = R_E \parallel R_L \parallel (R_F + R_i \parallel r_{p1}) \parallel \left(\frac{r_{p2} + r_{o1}}{b_{o2} + 1} \right) = 1\text{k}\Omega \parallel 4.7\text{k}\Omega \parallel (36\text{k}\Omega + 1\text{k}\Omega \parallel 5.09\text{k}\Omega) \parallel \frac{2.86\text{k}\Omega + 105\text{k}\Omega}{101} = 460\Omega$$

$$T_{SC} = 0, T_{OC} = 18.9, R_{out} = 460\Omega \left(\frac{1 + 0}{1 + 18.9} \right) = 23.1\Omega \quad | \quad \text{The results agree with SPICE.}$$

18.56

$$R_{inD} = 100\text{k}\Omega \parallel [1\text{M}\Omega + (10\text{k}\Omega \parallel 10\text{k}\Omega \parallel 40\text{k}\Omega)] = 91.0\text{k}\Omega \quad | \quad T_{SC} = 0$$

$$T_{OC} \cong g_m (10\text{k}\Omega \parallel 10\text{k}\Omega \parallel 40\text{k}\Omega) \frac{100\text{k}\Omega}{100\text{k}\Omega + 1\text{M}\Omega} = 0.808 \quad | \quad R_{in} = 91.0\text{k}\Omega \frac{1 + 0}{1 + 0.808} = 50.3\text{k}\Omega$$

$$R_{outD} = 10\text{k}\Omega \parallel 10\text{k}\Omega \parallel 40\text{k}\Omega \parallel 1.1\text{M}\Omega = 4.43\text{k}\Omega \quad | \quad T_{SC} = 0$$

$$T_{OC} \cong g_m (10\text{k}\Omega \parallel 10\text{k}\Omega \parallel 40\text{k}\Omega) \frac{100\text{k}\Omega}{100\text{k}\Omega + 1\text{M}\Omega} = 0.808 \quad | \quad R_{out} = 4.43\text{k}\Omega \frac{1 + 0}{1 + 0.808} = 2.45\text{k}\Omega$$

18.57

$$R_{outD} = \mathbf{m}_{f4} r_{o2} \mid T_{OC} = 0 \mid T_{SC} = (g_{m3} r_{o3}) \frac{g_{m4} (r_{o2} \parallel r_{o4})}{1 + g_{m4} (r_{o2} \parallel r_{o4})} \cong \mathbf{m}_{f3} \frac{\mathbf{m}_{f4}}{2 + \mathbf{m}_{f4}} \cong \mathbf{m}_{f3}$$

$$R_{out} = \mathbf{m}_{f4} r_{o2} \frac{1 + \mathbf{m}_{f3}}{1 + 0} = \mathbf{m}_{f4} r_{o2} (\mathbf{m}_{f3} + 1)$$

$$R_{inD} = r_{o3} \mid T_{SC} = 0 \mid T_{OC} = \mathbf{m}_{f3} \frac{g_{m4} (r_{o2} \parallel r_{o4})}{1 + g_{m4} (r_{o2} \parallel r_{o4})} \cong \mathbf{m}_{f3} \mid R_{in} = r_{o3} \frac{1 + 0}{1 + \mathbf{m}_{f3}} = \frac{1}{g_{m3}}$$

18.58

Using Wq. (14.28), $R_{outD} = r_o \left[1 + \frac{\mathbf{b}_o R_E}{R_{th} + r_p + R_E} \right] = r_{o4} \left[1 + \frac{\mathbf{b}_o (r_{o2} \parallel r_{p3})}{r_{o3} + r_{p4} + (r_{o2} \parallel r_{p3})} \right] \cong r_{o4} \frac{\mathbf{b}_o r_{p3}}{r_{o3}} = r_{o4} \frac{\mathbf{b}_o^2}{\mathbf{m}_f}$

$$T_{OC} = (g_{m3} r_{o3}) \frac{r_{o2} \parallel r_{p3}}{r_{o3} + r_{p4} + r_{o2} \parallel r_{p3}} \cong (g_{m3} r_{o3}) \frac{r_{p3}}{r_{o3}} = \mathbf{b}_o$$

$$T_{SC} \cong (g_{m3} r_{o3}) \frac{(\mathbf{b}_o + 1)(r_{o2} \parallel r_{p3})}{r_{o3} + r_{p4} + (\mathbf{b}_o + 1)(r_{o2} \parallel r_{p3})} \cong \mathbf{m}_f \mid R_{out} \cong r_{o4} \frac{\mathbf{b}_o^2}{\mathbf{m}_f} \frac{1 + \mathbf{m}_f}{1 + \mathbf{b}_o} \cong \mathbf{b}_o r_{o4}$$

We cannot exceed the $\mathbf{b}_o r_{o4}$ limit as long as the base current of Q₄ reaches ground!

$$R_{inD} = r_{o3} \parallel [r_{p4} + (\mathbf{b}_o + 1)(r_{o2} \parallel r_{p3})] \cong r_{o3} \parallel \mathbf{b}_o r_{p3} \cong r_{o3} \mid T_{SC} = 0$$

$$T_{OC} = \mathbf{m}_{f3} \frac{g_{m4} (r_{o2} \parallel r_{o4})}{1 + g_{m4} (r_{o2} \parallel r_{o4})} \cong \mathbf{m}_{f3} \mid R_{in} = r_{o3} \frac{1 + 0}{1 + \mathbf{m}_{f3}} \cong \frac{1}{g_{m3}}$$

18.59

$$(a) A(s) = \frac{\frac{2 \times 10^{14} \mathbf{p}^2}{(2 \mathbf{p} \times 10^3)(2 \mathbf{p} \times 10^5)}}{\left(1 + \frac{s}{2 \mathbf{p} \times 10^3}\right) \left(1 + \frac{s}{2 \mathbf{p} \times 10^5}\right)} = \frac{5 \times 10^5}{\left(1 + \frac{s}{2 \mathbf{p} \times 10^3}\right) \left(1 + \frac{s}{2 \mathbf{p} \times 10^5}\right)}$$

$A(s)$ represents a low - pass amplifier with two widely - spaced poles

$$\text{Open - loop : } A_o = 5 \times 10^5 = 114 \text{ dB} \mid f_L = 0 \mid f_H \cong f_1 = 1000 \text{ Hz}$$

(b) A common mistake would be the following :

$$\text{Closed - loop : } f_H = 1000 \text{ Hz} [1 + 5 \times 10^5 (0.01)] = 5 \text{ MHz}$$

Oops! - This exceeds $f_2 = 100 \text{ kHz}$! This is a two - pole low - pass amplifier.

$$A_v(s) = \frac{\frac{2 \times 10^{14} \mathbf{p}^2}{(s + 2 \mathbf{p} \times 10^3)(s + 2 \mathbf{p} \times 10^5)}}{1 + \frac{2 \times 10^{14} \mathbf{p}^2}{(s + 2 \mathbf{p} \times 10^3)(s + 2 \mathbf{p} \times 10^5)} (0.01)} = \frac{2 \times 10^{14} \mathbf{p}^2}{s^2 + 1.01(2 \mathbf{p} \times 10^5)s + 2 \times 10^{12} \mathbf{p}^2}$$

Using dominant - root factorization : $f_1 = 101 \text{ kHz}$, $f_2 = 4.95 \text{ MHz}$

So the closed - loop values are $f_H = 101 \text{ kHz}$ and $f_L = 0$.

18.60

$$(a) A(s) = \frac{\frac{2p \times 10^{10} s}{(2p \times 10^6)}}{(s + 2p \times 10^3) \left(1 + \frac{s}{2p \times 10^6}\right)} = \frac{10^4 s}{(s + 2p \times 10^3) \left(1 + \frac{s}{2p \times 10^6}\right)}$$

$A(s)$ represents a band - pass amplifier with two widely - spaced poles

Open - loop : $A_o = 10^4$ or 80 dB | $f_L = 1 \text{ kHz}$ | $f_H = 1 \text{ MHz}$

$$(b) A_v(s) = \frac{\frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}}{1 + \frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}} (0.01) = \frac{6.28 \times 10^{10} s}{s^2 + 1.01(2p \times 10^8)s + 4p^2 \times 10^9}$$

Using dominant - root factorization :

$$f_H = \frac{1.01(2p \times 10^8)}{2p} = 101 \text{ MHz}, \quad f_L = \frac{1}{2p} \left(\frac{4p^2 \times 10^9}{1.01(2p \times 10^8)} \right) = 9.90 \text{ Hz}$$

$$(c) A_v(s) = \frac{\frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}}{1 + \frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}} (0.025) = \frac{6.28 \times 10^{10} s}{s^2 + 2.51(2p \times 10^8)s + 4p^2 \times 10^9}$$

Using dominant - root factorization :

$$f_H = \frac{2.51(2p \times 10^8)}{2p} = 251 \text{ MHz}, \quad f_L = \frac{1}{2p} \left(\frac{4p^2 \times 10^9}{2.51(2p \times 10^8)} \right) = 3.98 \text{ Hz}$$

18.61

$$(a) A(s) = \frac{\frac{4p^2 \times 10^{18} s^2}{(2p \times 10^6)(2p \times 10^7)}}{(s + 200p)(s + 2000p) \left(1 + \frac{s}{2p \times 10^6}\right) \left(1 + \frac{s}{2p \times 10^7}\right)}$$

$$A(s) = \frac{10^5 s^2}{(s + 200p)(s + 2000p) \left(1 + \frac{s}{2p \times 10^6}\right) \left(1 + \frac{s}{2p \times 10^7}\right)}$$

$A(s)$ represents a band - pass amplifier with four widely - spaced poles

Open - loop : $A_o = 10^5$ or 100 dB | $f_L \cong 1 \text{ kHz}$ | $f_H \cong 1 \text{ MHz}$

$$(b) A_v(s) = \frac{\frac{4p^2 \times 10^{18} s^2}{(s + 200p)(s + 2000p)(s + 2p \times 10^6)(s + 2p \times 10^7)}}{1 + \frac{4p^2 \times 10^{18} s^2}{(s + 200p)(s + 2000p)(s + 2p \times 10^6)(s + 2p \times 10^7)}} (0.01)$$

Using MATLAB : $D(s) = s^4 + 6.9122 \times 10^7 s^3 + 3.9518 \times 10^{17} s^2 + 2.7288 \times 10^{18} s + 1.5585 \times 10^{21}$

The closed loop amplifier has complex roots :

$$\frac{1}{2p}(-3.45 \pm j62.7) = (-0.637 \pm j9.98) \text{ Hz} \quad \text{and} \quad \frac{10^8}{2p}(-0.346 \pm j6.28) = (-0.0637 \pm j1) \times 10^8 \text{ Hz}$$

Note that the amplifier is stable since all the poles are in the left half plane. See Problem 18.67.

$$(c) A_v(s) = \frac{\frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}}{1 + \frac{2p \times 10^{10} s}{(s + 2p \times 10^3)(s + 2p \times 10^6)}} \quad (0.025)$$


Using MATLAB : $D(s) = s^4 + 6.9122 \times 10^7 s^3 + 9.909 \times 10^{16} s^2 + 2.7288 \times 10^{18} s + 1.5585 \times 10^{21}$

The closed loop amplifier has complex roots :

$$\frac{1}{2p}(-13.8 \pm j124.7) = (-2.20 \pm j19.9) \text{ Hz} \quad \text{and} \quad \frac{10^8}{2p}(-0.346 \pm j3.13) = (-0.637 \pm j4.98) \times 10^7 \text{ Hz}$$


Note that the amplifier is stable since all the poles are in the left half plane.

18.62

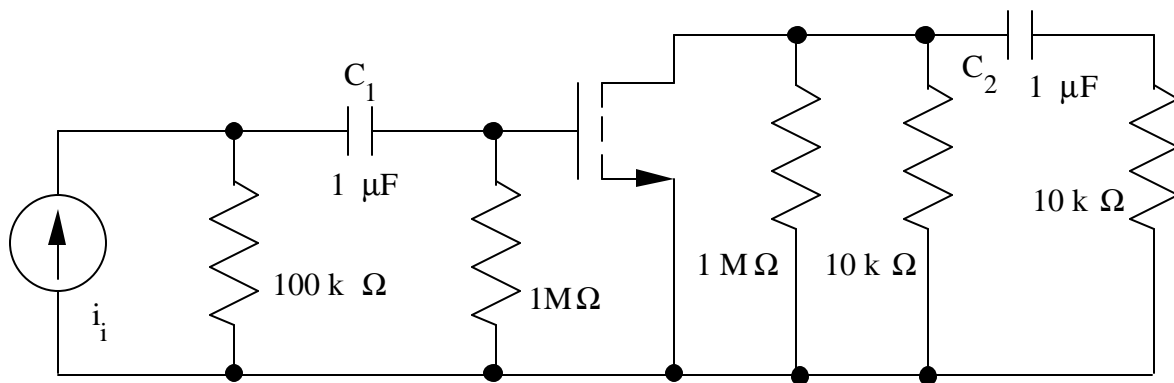

$$w_1 = \frac{1}{10^{-6}(100k\Omega + 1M\Omega)} = 0.909 \frac{\text{rad}}{s} \quad | \quad w_2 = \frac{1}{10^{-6}(10k\Omega + 25k\Omega || 10k\Omega || 1M\Omega)} = 58.5 \frac{\text{rad}}{s}$$
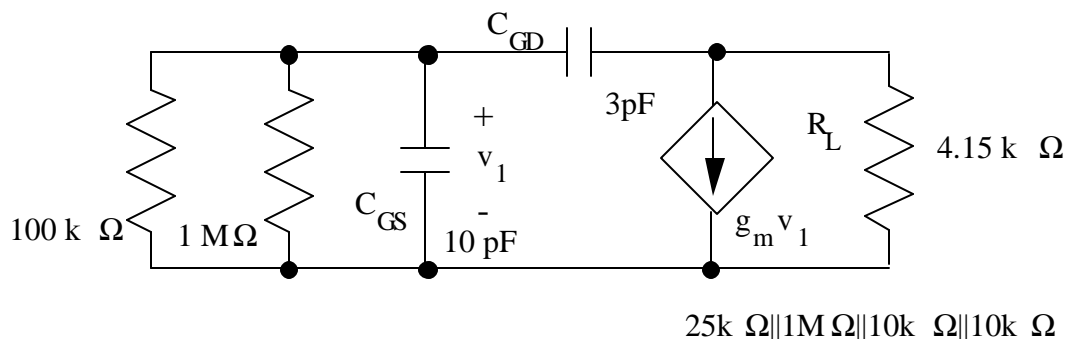
$$\text{Separate, widely - spaced, poles} \rightarrow f_L^A = f_2 = \frac{58.5}{2p} = 9.31 \text{ Hz}$$



$$w_H^A = \frac{1}{r_{po} C_T} = \frac{1}{(100k\Omega \parallel 1M\Omega) \left[10pF + 3pF \left(1 + 2mS(4.15k\Omega) + \frac{4.15k\Omega}{100k\Omega \parallel 1M\Omega} \right) \right]}$$

$$f_H^A = \frac{1}{2\pi (90.9k\Omega)(38.0pF)} = 46.1 \text{ kHz}$$

$$v_{gs} = i_s (100k\Omega \parallel 1M\Omega) = (90.9k\Omega) i_s \quad | \quad v_o = -(2 \times 10^{-3}) v_{gs} (25k\Omega \parallel 10k\Omega \parallel 10k\Omega \parallel 1M\Omega)$$

$$A = \frac{v_o}{i_s} = -(2mS)(4.15k\Omega)(90.9k\Omega) = -7.55 \times 10^5 \Omega \quad | \quad y_{12}^F = -10^{-5} S$$

$$1 + Ab = 1 + (-7.55 \times 10^5 \Omega)(-10^{-6} S) = 1.76$$


$$f_L = \frac{9.31}{1.76} = 5.29 \text{ Hz} \quad f_H = 46.1 \text{ kHz}(1.76) = 81.0 \text{ kHz}$$

18.63

$$S_{A_o}^{w_H^F} = \frac{A_o}{w_H^F} \frac{f(w_H^F)}{f(A_o)} \quad | \quad w_H^F = w_H^A (1 + Ab) \quad | \quad S_{A_o}^{w_H^F} = \frac{A_o}{w_H^A (1 + A_o b)} w_H^A b = \frac{A_o b}{(1 + A_o b)} \cong +1$$

$$\frac{f(w_H^F)}{w_H^F} = S_{A_o}^{w_H^F} \frac{f(A_o)}{A_o} = \frac{10^5 (0.01)}{1 + 10^5 (0.01)} 10\% = 9.99\%$$

18.64

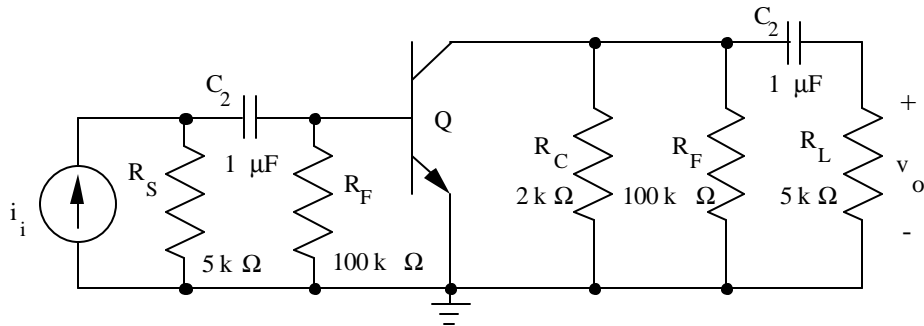

$$\text{From the Exercise : } g_m = 40.3 \text{ mS} \quad | \quad r_p = 3.72 \text{ k}\Omega \quad | \quad r_o = 50.8 \text{ k}\Omega \quad | \quad 1 + Ab = 2.19$$

$$r_{o2} = \frac{50 + 1.4}{10^{-4}} = 514 \text{ k}\Omega \quad | \quad r_{o4} = \frac{50 + 11.3}{10^{-4}} = 613 \text{ k}\Omega \quad | \quad r_{p5} = \frac{100(0.025)}{0.0012} = 2.08 \text{ k}\Omega$$


$$C_{p1} = \frac{40.3 \text{ mS}}{2\pi(500 \text{ MHz})} - 0.75 \text{ pF} = 12.1 \text{ pF}$$

$$\text{Using the open - circuit time constant approach with } C_1 = C_2 = 1 \text{ nF :}$$

$$R_{1o} = 5 \text{ k}\Omega + 100 \text{ k}\Omega \parallel r_p \parallel 5 \text{ k}\Omega + 100 \text{ k}\Omega \parallel 3.72 \text{ k}\Omega = 8.59 \text{ k}\Omega$$

$$R_{2o} = 5 \text{ k}\Omega + 50.8 \text{ k}\Omega \parallel 2 \text{ k}\Omega \parallel 100 \text{ k}\Omega = 6.89 \text{ k}\Omega$$

$$f_L = \frac{1}{2\pi} \left[\frac{1}{1 \text{ nF}(8.59 \text{ k}\Omega)} + \frac{1}{1 \text{ nF}(6.89 \text{ k}\Omega)} \right] = 41.6 \text{ Hz} \quad | \quad f_L^F = \frac{f_L}{1 + Ab} = 19.0 \text{ Hz}$$

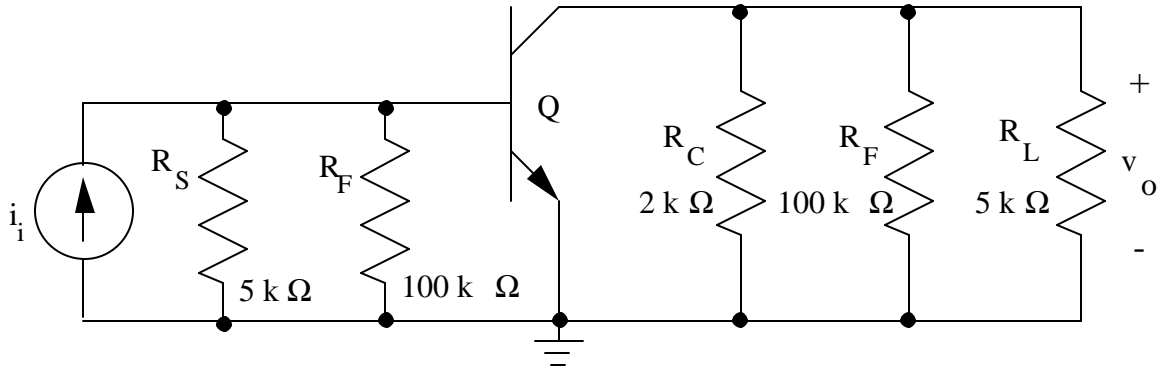

$$r_{po} = 3.72 k\Omega \parallel 100 k\Omega \parallel 5 k\Omega = 2.09 k\Omega \quad | \quad R_L = 50.8 k\Omega \parallel 2 k\Omega \parallel 100 k\Omega \parallel 5 k\Omega = 1.37 k\Omega$$

$$C_T = 12.1 pF + 0.75 pf \left[1 + 40.3 mS(1.37 k\Omega) + \frac{1.37 k\Omega}{2.09 k\Omega} \right] = 54.8 pF$$

$$f_H = \frac{1}{2\pi r_{po} C_T} = \frac{1}{2\pi(1.37 k\Omega)(54.8 pF)} = 1.39 MHz \quad | \quad f_H^F = f_H(1 + Ab) = 3.04 MHz$$

18.65

$$A(s) = \frac{2p \times 10^7}{s + 2000p} \quad | \quad A = \frac{25 k\Omega}{1 k\Omega + 25 k\Omega + 9.01 k\Omega} \left(\frac{2p \times 10^7}{s + 2000p} \right) \frac{1.96 k\Omega}{1.96 k\Omega + 1 k\Omega} = \frac{2.97 \times 10^7}{s + 2000p}$$

$$A_v(s) = \frac{\frac{2.97 \times 10^7}{s + 2000p}}{1 + \frac{2.97 \times 10^7}{s + 2000p}(0.0990)} = \frac{2.97 \times 10^7}{s + 2.95 \times 10^6} = \frac{10.1}{1 + \frac{s}{2.95 \times 10^6}} \quad | \quad f_H = \frac{2.95 \times 10^6}{2p} = 470 kHz$$

18.66

(a) At high frequencies with $b = 0.01$, $Ab = \frac{(2 \times 10^{14} p^2)(0.01)}{(s + 2000p)(s + 2px10^5)} \cong \frac{(2 \times 10^{12} p^2)}{s(s + 2px10^5)}$

$$|Ab| = \frac{(2 \times 10^{12} p^2)}{w \sqrt{w^2 + (2px10^5)^2}} = 1 \quad | \quad \text{Using MATLAB, } w = 4.42 \times 10^6$$

$$\angle Ab = -90 - \tan^{-1} \left(\frac{4.42 \times 10^6}{2px10^5} \right) = 171.9^\circ \quad | \quad \Phi_M = 8.1^\circ$$

(b) At high frequencies with $b = 0.025$, $Ab = \frac{(2 \times 10^{14} p^2)(0.025)}{(s + 2000p)(s + 2px10^5)} \cong \frac{(5 \times 10^{12} p^2)}{s(s + 2px10^5)}$

$$|Ab| = \frac{(5 \times 10^{12} p^2)}{w \sqrt{w^2 + (2px10^5)^2}} = 1 \quad | \quad \text{Using MATLAB, } w = 7.01 \times 10^6$$

$$\angle Ab = -90 - \tan^{-1} \left(\frac{7.01 \times 10^6}{2px10^5} \right) = 174.9^\circ \quad | \quad \Phi_M = 5.1^\circ$$

18.67

(a) At high frequencies with $b = 0.01$, $Ab = \frac{s(2p \times 10^{10})(0.01)}{(s + 2000p)(s + 2p \times 10^6)} \cong \frac{2p \times 10^8}{(s + 2p \times 10^6)}$

$$|Ab| = \frac{2p \times 10^8}{\sqrt{w^2 + (2p \times 10^6)^2}} = 1 \quad | \quad w \cong 2p \times 10^8$$

$$\angle Ab = -\tan^{-1}\left(\frac{2p \times 10^8}{2p \times 10^6}\right) = -89.4^\circ \quad | \quad \Phi_M = 90.6^\circ$$

(b) At high frequencies with $b = 0.025$, $Ab = \frac{s(2p \times 10^{10})(0.025)}{(s + 2000p)(s + 2p \times 10^6)} \cong \frac{5p \times 10^8}{(s + 2p \times 10^6)}$

$$|Ab| = \frac{5p \times 10^8}{w\sqrt{w^2 + (2p \times 10^6)^2}} = 1 \quad | \quad w \cong 5p \times 10^8$$

$$\angle Ab = -\tan^{-1}\left(\frac{5p \times 10^8}{2p \times 10^6}\right) = -89.8^\circ \quad | \quad \Phi_M = 90.2^\circ$$

18.68

(a) At high frequencies with $b = 0.01$, $Ab = \frac{s^2(4p^2 \times 10^{18})(0.01)}{(s + 200p)(s + 2000p)(s + 2p \times 10^6)(s + 2p \times 10^7)}$

$$Ab \cong \frac{s^2(4p^2 \times 10^{18})(0.01)}{s^2(s + 2p \times 10^6)(s + 2p \times 10^7)} \cong \frac{4p^2 \times 10^{16}}{(s + 2p \times 10^6)(s + 2p \times 10^7)}$$

$$|Ab| = \frac{4p^2 \times 10^{16}}{\sqrt{w^2 + (2p \times 10^6)^2}\sqrt{w^2 + (2p \times 10^6)^2}} = 1 \quad | \quad \text{Using MATLAB, } w \cong 6.2673 \times 10^8$$

$$\angle Ab = -\tan^{-1}\left(\frac{6.2673 \times 10^8}{2p \times 10^6}\right) - \tan^{-1}\left(\frac{6.2673 \times 10^8}{2p \times 10^7}\right) = -173.7^\circ \quad | \quad \Phi_M = 6.3^\circ$$

(b) At high frequencies with $b = 0.025$, $Ab = \frac{s^2(4p^2 \times 10^{18})(0.025)}{(s + 200p)(s + 2000p)(s + 2p \times 10^6)(s + 2p \times 10^7)}$

$$Ab \cong \frac{s^2(4p^2 \times 10^{18})(0.025)}{s^2(s + 2p \times 10^6)(s + 2p \times 10^7)} \cong \frac{p^2 \times 10^{17}}{(s + 2p \times 10^6)(s + 2p \times 10^7)}$$

$$|Ab| = \frac{p^2 \times 10^{17}}{\sqrt{w^2 + (2p \times 10^6)^2}\sqrt{w^2 + (2p \times 10^6)^2}} = 1 \quad | \quad \text{Using MATLAB, } w \cong 9.9246 \times 10^8$$

$$\angle Ab = -\tan^{-1}\left(\frac{9.9246 \times 10^8}{2p \times 10^6}\right) - \tan^{-1}\left(\frac{9.9246 \times 10^8}{2p \times 10^7}\right) = -176.0^\circ \quad | \quad \Phi_M = 4.0^\circ$$

18.69

$$(a) T(s) = \frac{4 \times 10^{19} p^3}{(s + 2p \times 10^4)(s + 2p \times 10^5)^2} \mathbf{b} \quad | \quad \angle T(j\omega) = -\tan^{-1} \frac{f}{10^4} - 2 \tan^{-1} \frac{f}{10^5} = -180^\circ$$

For $f \gg 10^4$, $-2 \tan^{-1} \frac{f}{10^5} = -90^\circ \rightarrow f = 10^5 \text{ Hz}$. Using this as a starting point

for iteration, we find $f = 110 \text{ kHz}$ or $\omega = 2.2 \times 10^5 p$

$$(b) |A(j2.2 \times 10^5 p)| = \frac{4 \times 10^{19} p^3}{\sqrt{(2.2 \times 10^5 p)^2 + (2p \times 10^4)^2} [(2.2 \times 10^5 p)^2 + (2p \times 10^5)^2]} = 2048$$

The amplifier will oscillate for closed - loop gains ≤ 2048 (66.2 dB).

18.70

$$T(s) = A \mathbf{b} = \left(\frac{10^7}{s+50} \right) \frac{1}{sC_L} = \left(\frac{10^7}{s+50} \right) \frac{1}{sC_L R_o + 1} = \left(\frac{10^7}{s+50} \right) \frac{1}{500sC_L + 1}$$

Assume that the unity - gain occurs at $\omega_1 \gg 50$: $\angle T(j\omega_1) = \angle A + \angle \mathbf{b} = -90^\circ - \tan^{-1}(500\omega_1 C_L)$
 $-90^\circ - \tan^{-1}(500\omega_1 C_L) = -180^\circ + 60^\circ \quad | \quad \tan^{-1}(500\omega_1 C_L) = 30^\circ \quad | \quad 500\omega_1 C_L = 0.5774$

$$|T(j\omega_1)| = 1 \quad | \quad \frac{10^7}{\omega_1 \sqrt{1 + (500\omega_1 C_L)^2}} = \frac{10^7}{\omega_1 \sqrt{1 + [\tan(30^\circ)]^2}} = 1 \rightarrow \omega_1 = 8.66 \times 10^6$$

$$C_L = \frac{\tan(30^\circ)}{500(8.66 \times 10^6)} = 133 \text{ pF}$$

18.71

$$(a) T = A \mathbf{b} = \frac{2 \times 10^{14} p^2}{(s + 2 \times 10^3 p)(s + 2 \times 10^5 p)} \left(\frac{1}{5} \right) \quad | \quad \text{Yes, it is a second - order system and will}$$

have some phase margin, although Φ_M may be vanishingly small.

$$(b) \text{ For } \omega \gg 2p \times 10^5, \quad |T(j\omega)| \approx \frac{4 \times 10^{13} p^2}{\omega^2} \quad \text{and} \quad |T(j\omega)| = 1 \text{ for } \omega = 1.987 \times 10^7 \frac{\text{rad}}{\text{s}}$$

$$\angle T(j1.987 \times 10^7) = -\tan^{-1} \frac{1.987 \times 10^7}{2000p} - \tan^{-1} \frac{1.987 \times 10^7}{2 \times 10^5 p} = 178.2^\circ \rightarrow \Phi_M = 1.83^\circ \quad | \quad \text{A very small phase margin.}$$

18.72 (a)


The following command line will generate the complete bode plot:

```
w=logspace(3,8,400); bode((2e14*pi^2/5),conv([1 2000*pi],[1 2e5*pi]),w)
```

The following command line will generate the bode plot between 10^7 and 10^8 rad/s :


```
w=logspace(7,8,100); bode((2e14*pi^2/5),conv([1 2000*pi],[1 2e5*pi]),w)
```

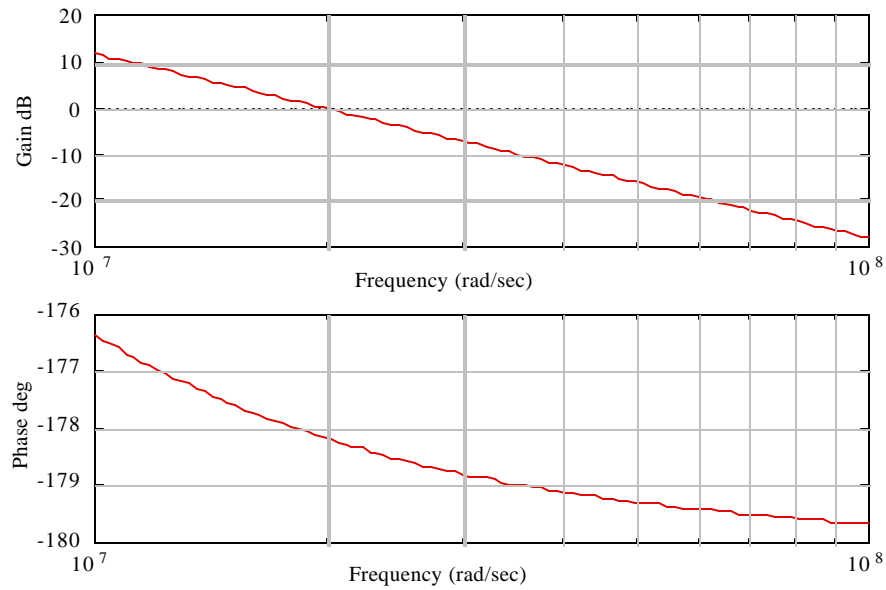The second plot agrees with the results calculated in the previous problem.



(b) `w=logspace(7,8,100); bode((2e14*pi^2),conv([1 2000*pi],[1 2e5*pi]),w)`
yields a phase margin of only 0.75 degrees

18.73

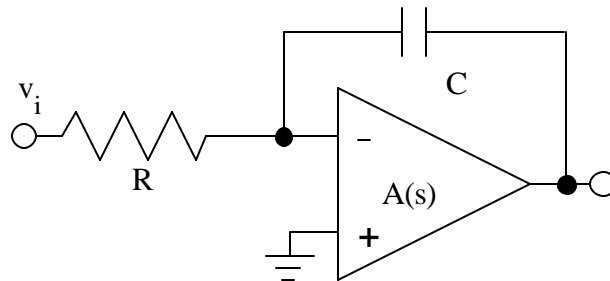

$$\mathbf{b} = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{sRC + 1} \quad \bigg| \quad T = \frac{2\mathbf{p} \times 10^6}{s + 20\mathbf{p}} \frac{sRC}{(sRC + 1)} \quad \bigg| \quad \text{For } \mathbf{w}RC \gg 1, \quad T \cong \frac{2\mathbf{p} \times 10^6}{s + 20\mathbf{p}}$$

$$\text{and } |T| = 1 \text{ for } \mathbf{w} = 2\mathbf{p} \times 10^6. \text{ Given } RC = 10^{-8}(10^5) = 10^{-3}, \quad \mathbf{b} = \frac{s}{s + 1000}$$

$$\angle T = 90^\circ - \tan^{-1} \frac{2\mathbf{p} \times 10^6}{20\mathbf{p}} - \tan^{-1} \frac{2\mathbf{p} \times 10^6}{1000} = -90.0^\circ \quad \bigg| \quad \Phi_M = 90.0^\circ$$

18.74

$$b = \frac{R}{R + \frac{1}{sC}} = \frac{sRC}{sRC + 1} = \frac{s10^5(10^{-8})}{s10^5(10^{-8}) + 1} = \frac{s}{s + 1000}$$

$$A(s) = \frac{10^5}{\left(1 + \frac{s}{2000p}\right)\left(1 + \frac{s}{200000p}\right)} = \frac{4p^2 \times 10^{13}}{(s + 2000p)(s + 200000p)}$$


$$T = \frac{4p^2 \times 10^{13}}{(s + 2000p)(s + 200000p)} \frac{s}{(s + 1000)} \quad | \quad \text{At high frequencies, } T \cong \frac{4p^2 \times 10^{13}}{s^2}$$

and the integrator will have a positive phase margin, although Φ_M may be very small.

$$\text{For } w \gg 2p \times 10^5, \quad |T(jw_1)| \approx \frac{4p^2 \times 10^{13}}{w_1^2} = 1 \Rightarrow w = 1.987 \times 10^7 \frac{\text{rad}}{s} \gg 2p \times 10^5$$

$$\angle T = 90^\circ - \tan^{-1} \frac{1.987 \times 10^7}{2000p} - \tan^{-1} \frac{1.987 \times 10^7}{200000p} - \tan^{-1} \frac{1.987 \times 10^7}{1000} \quad | \quad \Phi_M = 1.83^\circ$$

18.75

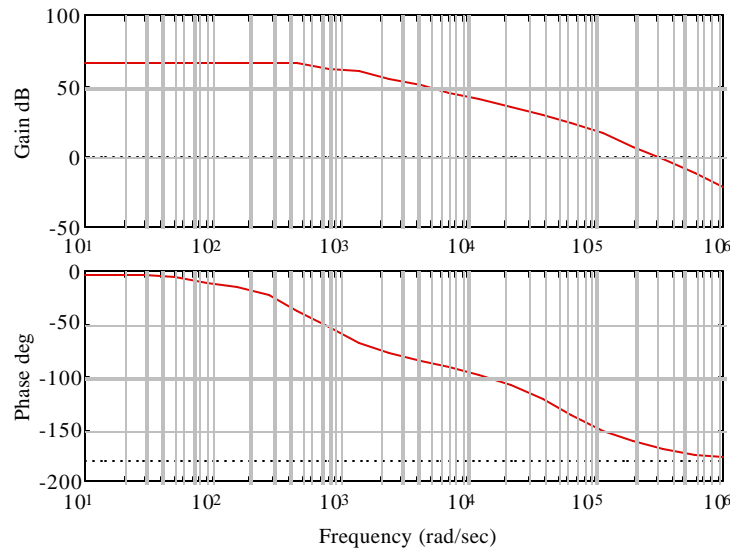

$$(a) \quad b = \frac{R_1}{R_2 \frac{1}{sC_C}} = \frac{R_1}{R_1 + \frac{R_2}{sC_C R_2 + 1}} = \frac{R_1}{R_1 + R_2} \frac{sC_C R_2 + 1}{sC_C (R_1 \parallel R_2) + 1}$$

$$\text{For } C_C = 0, \quad T = \frac{2 \times 10^{11} p^2}{(s + 200p)(s + 20000p)} \frac{1}{21}$$


The graphs above were generated using

`bode(2e11*pi^2/21,[1 2.02e4*pi 4e6*pi^2])`

Blowing up the last decade:

```
w=linspace(1e5,1e6); bode(2e11*pi^2/21,[1 2.02e4*pi 4e6*pi^2],w)
```

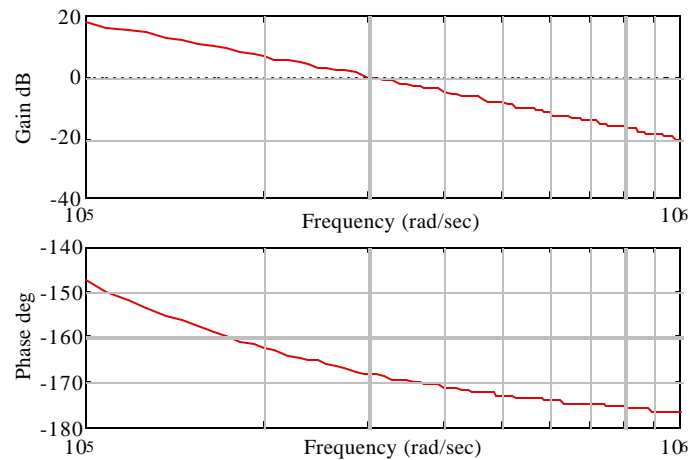and the phase margin is approximately 12°



Setting the zero to cancel the second pole,

$$b(s) = \frac{R_1}{R_1 + R_2} \frac{sC_c R_2 + 1}{sC_c (R_1 \parallel R_2) + 1} = \frac{s + \frac{1}{C_c R_2}}{s + \frac{1}{C_c (R_1 \parallel R_2)}}$$


$$T = \frac{2 \times 10^{11} p^2}{(s + 200p)(s + 20000p)} \frac{(s + 20000p)}{s + 1.319 \times 10^6} = \frac{2 \times 10^{11} p^2}{s^2 + 1.320 \times 10^6 s + 8.288 \times 10^6}$$

Using MATLAB:

```
bode(2e11*pi^2,[1 1.320e6 8.288e8])
```

and then
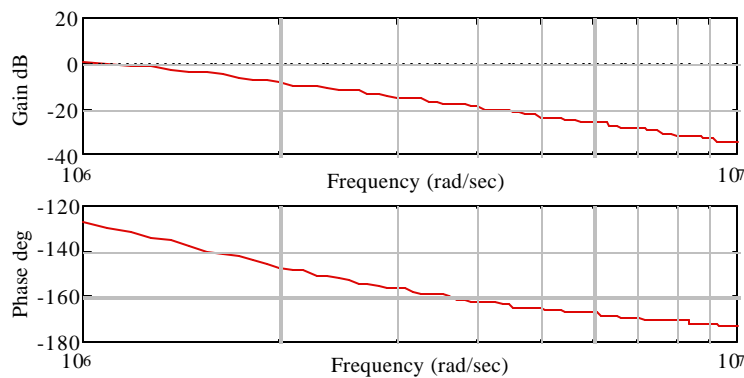
```
w=linspace(1e6,1e7); bode(2e11*pi^2,[1 1.320e6 8.288e8],w)
```



The phase margin is now approximately 50°

18.76


```
num=4e19*pi^3;
p=conv([1 2e5*pi],[1 2e5*pi]);
den=conv([1 2e4*pi],p);
bode(num,den)
```

Results: Frequency = 6.9×10^5 rad/s and approximately 66 dB

which agree with the hand calculations in Problem 18.47.


18.77

Bode Diagrams

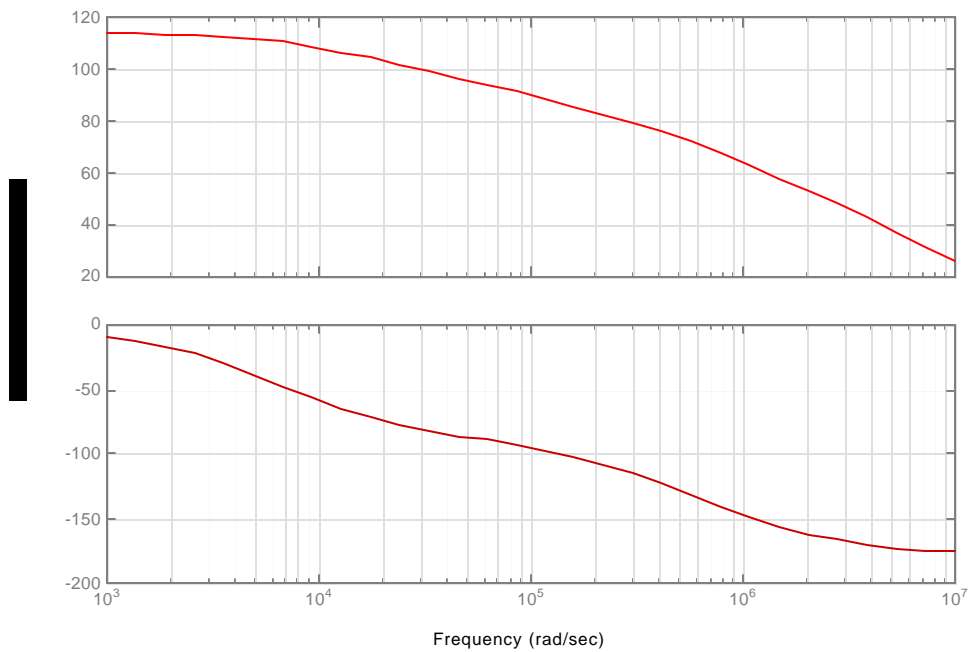


Expanded view:

Bode Diagrams

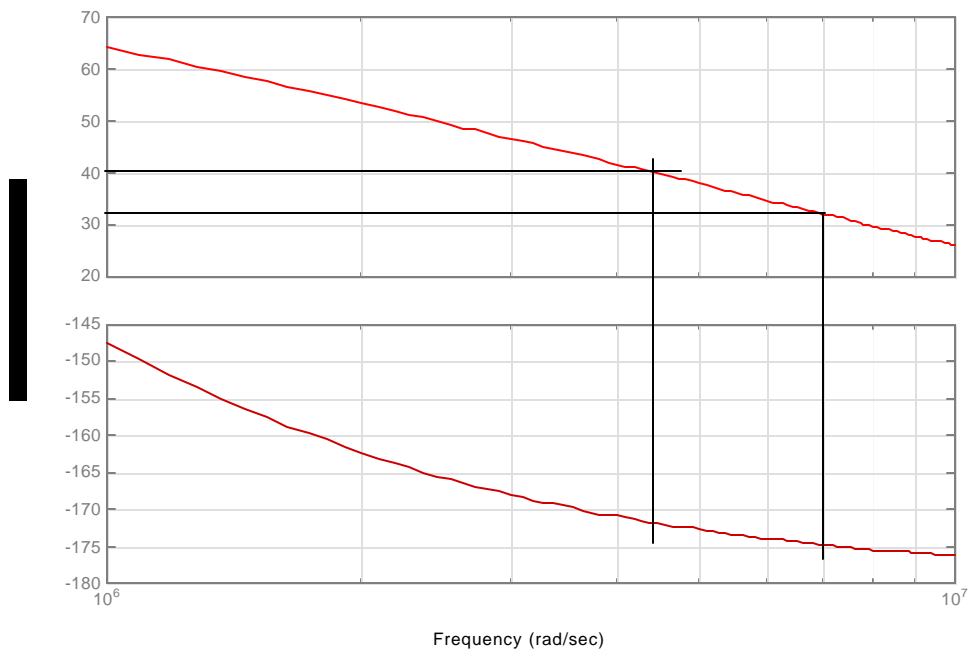


For a gain of 100 (40 dB), the phase margin is approximately 8° . For a gain of 40 (32 dB), the phase margin is approximately 5° . The gain margin is infinite in both cases since the phase shift never reaches 180° . These values agree with the calculations in Problem 18.66. (b) The amplifier will not oscillate.

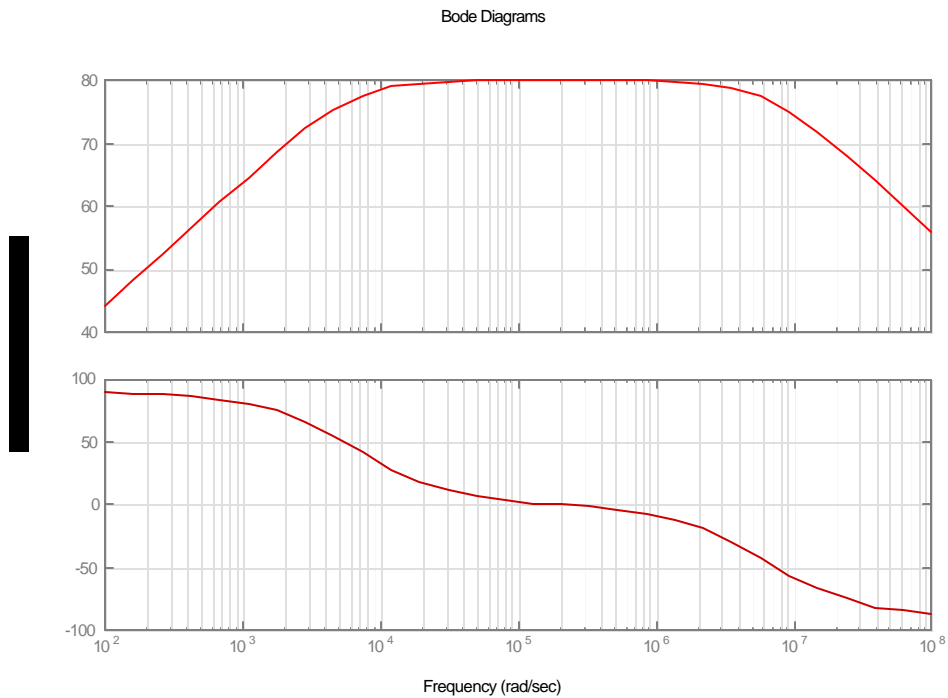18.78


The phase shift ranges from $+90^\circ$ at low frequencies to -90° at high frequencies. The phase margin for both gains of 100 and 40 is 90° at the high frequency intersection and 270° at the low end. These values agree with the calculations in Problem 18.67. (b) The amplifier will not oscillate.

Expanded view at high frequencies:

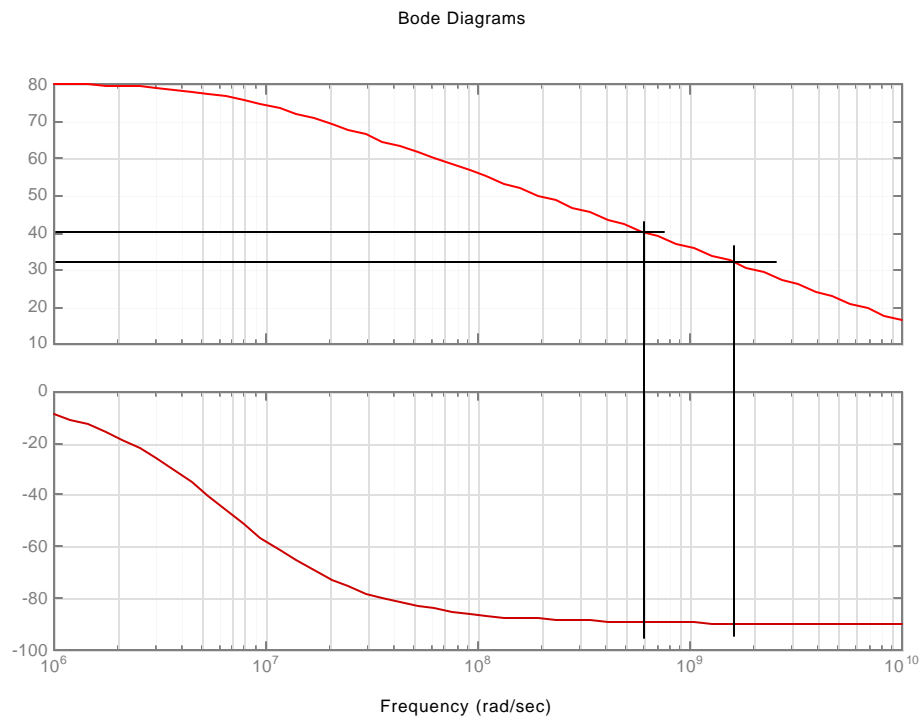


18.79

Bode Diagrams

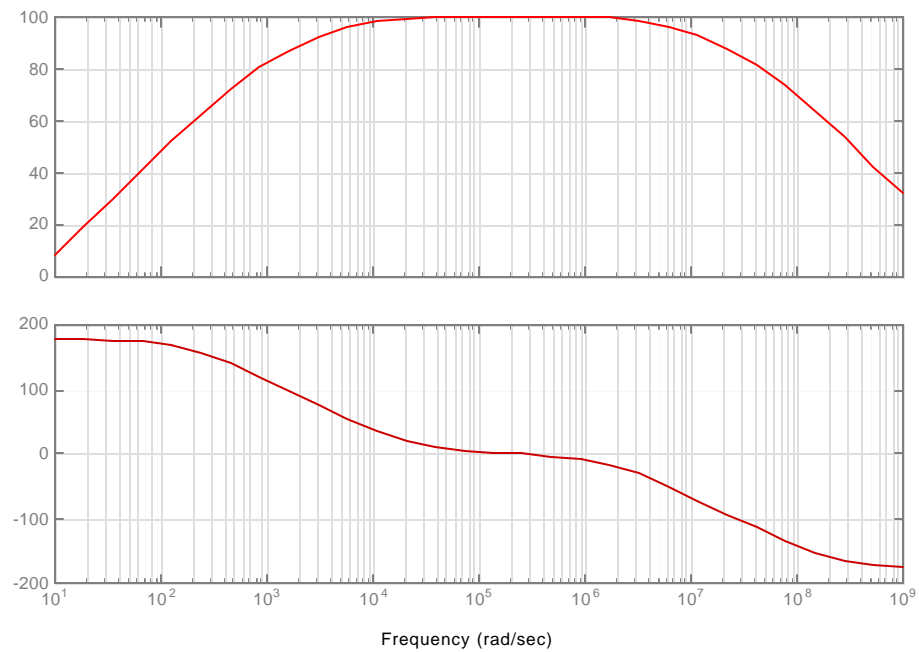

Bode Diagrams

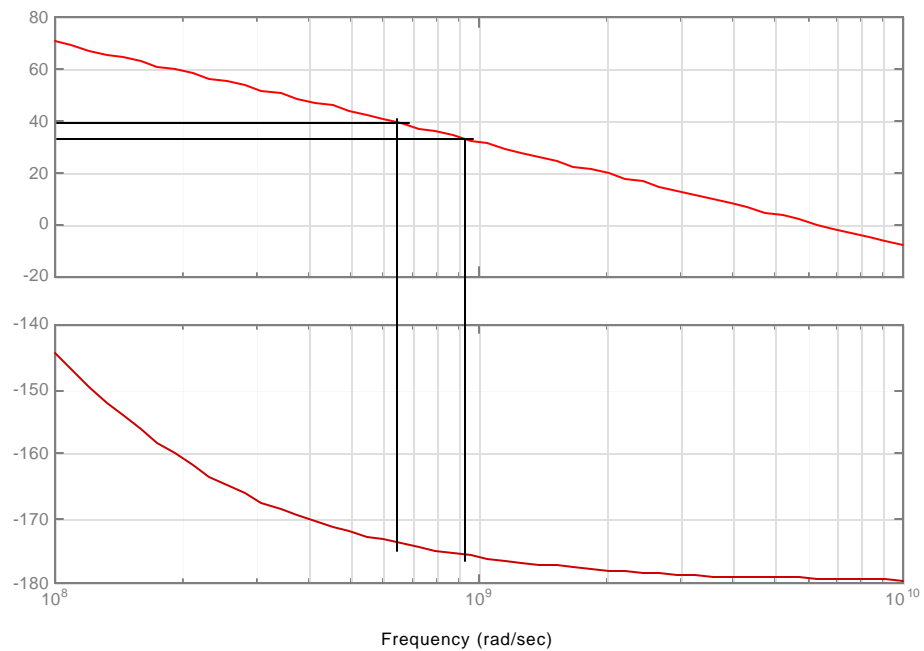

The phase margin is approximately 6° and 4° for gains of 40 dB and 32 dB respectively. The gain margin is infinite in both cases. These values agree with the calculations in Problem 18.68. (b) The amplifier will not oscillate.

18.80

```


num=2e11*pi^2
den=conv([1 200*pi],[1 20000*pi]);
bode(num/100,den)

w=logspace(5,6,100); bode(num/100,den,w)

```

Results: Yes, the amplifier is stable with a phase margin of approximately 26° .

Bode Diagrams

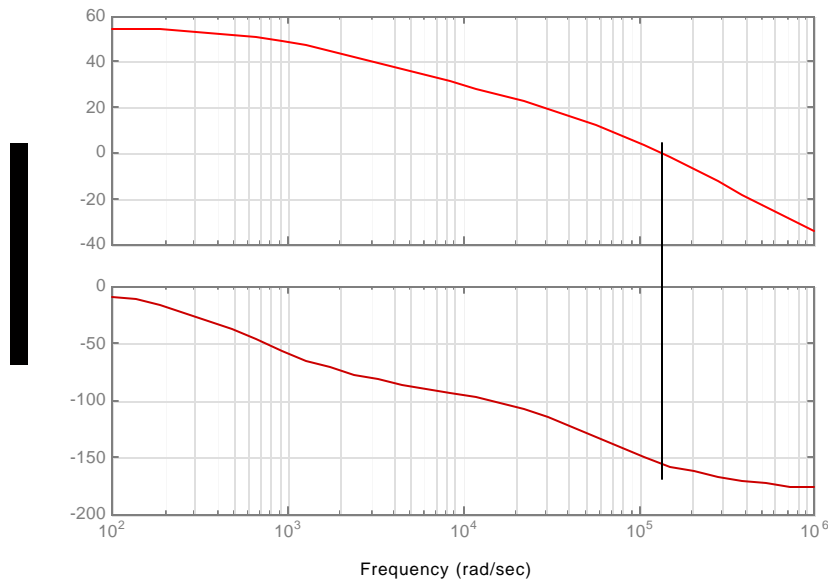

18.81

$$A_v(s) = \frac{\frac{A_o w_o}{s + w_o}}{1 + \frac{A_o w_o}{s + w_o}} = \frac{w_T}{s + (1 + A_o)w_o} \cong \frac{w_T}{s + w_T} = \frac{2p \times 10^6}{s + 2p \times 10^6}$$

$$\text{From problem 18.45 : } b(s) = \frac{5 \times 10^4 s}{s^2 + 7 \times 10^4 s + 5 \times 10^8}$$

$$T(s) = A_v(s)b(s) = \frac{10^{11} p s}{(s + 2p \times 10^6)(s^2 + 7 \times 10^4 s + 5 \times 10^8)}$$

Using MATLAB:

```


num=[pi*1e11 0]
den=conv([1 3e5 1e10],[1 5e6])
bode(num,den)

```

It is also instructive to use: `nyquist(num,den)`

One finds that $|T(j\omega)| < 1$ for all ω , so the phase margin is undefined. The filter is stable. Note that this is a positive feedback system so the point of interest is $+1$. The gain of the filter is approximately -3 dB. So the filter has a gain margin of 3 dB.

Bode Diagrams

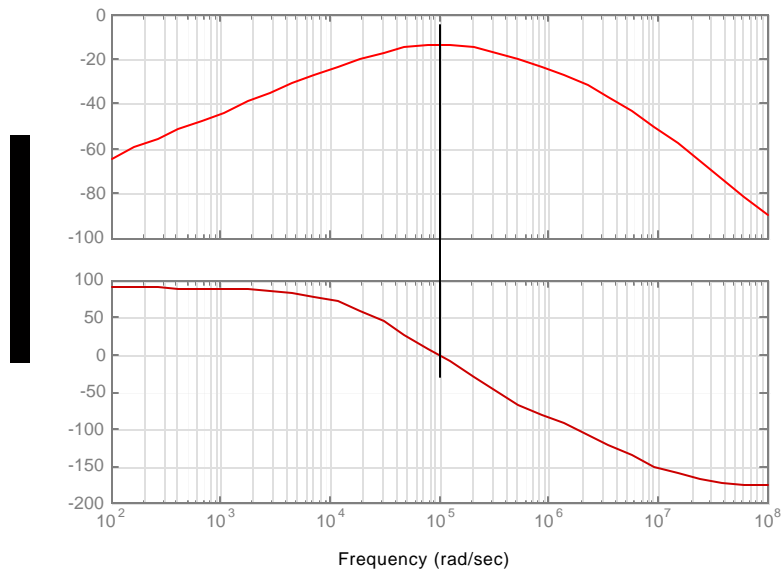

18.82

$$T(s) = K(s)b(s) = \left(\frac{10^7}{s + 5 \times 10^6} \right) \left(\frac{10^5 s}{s^2 + 3 \times 10^5 s + 10^{10}} \right) = \frac{10^{12} s}{(s + 5 \times 10^6)(s^2 + 3 \times 10^5 s + 10^{10})}$$


Using MATLAB:

```
num=[1e12 0]
den=conv([1 3e5 1e10],[1 5e6])
bode(num,den)
```

It is also instructive to use: nyquist(num,den)

One finds that $|T(j\omega)| < 1$ for all ω , so the phase margin is undefined. The filter is stable. Note that this is a positive feedback system so the point of interest is +1. The gain of the filter is approximately -3 dB. So the filter has a gain margin of 3 dB.

Bode Diagrams

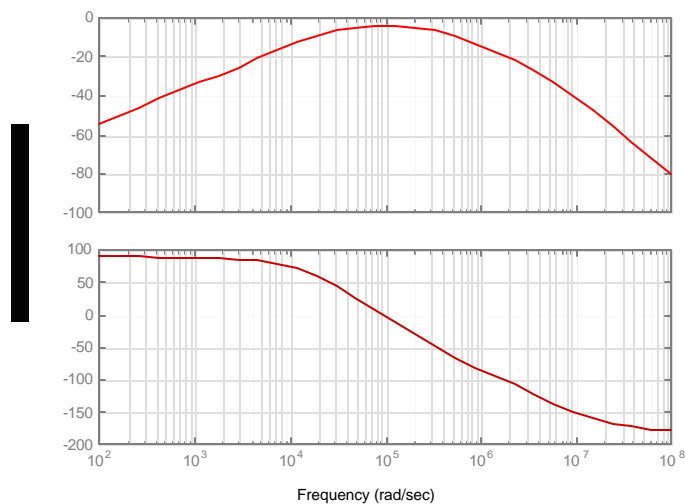

18.83


$$\mathbf{b} = \frac{sRC}{sRC + 1} = \frac{s}{s + 1000} \quad | \quad T = \frac{2\mathbf{p} \times 10^6 s}{(s + 20\mathbf{p})(s + 1000)}$$

Using MATLAB:

```
num=[2e6*pi 0]; den=conv([1 20*pi],[1 1000]);
w=logspace(0,8,400);
bode(num,den,w)
```

The phase margin is 90° which agrees with Problem 18.73.

Bode Diagrams

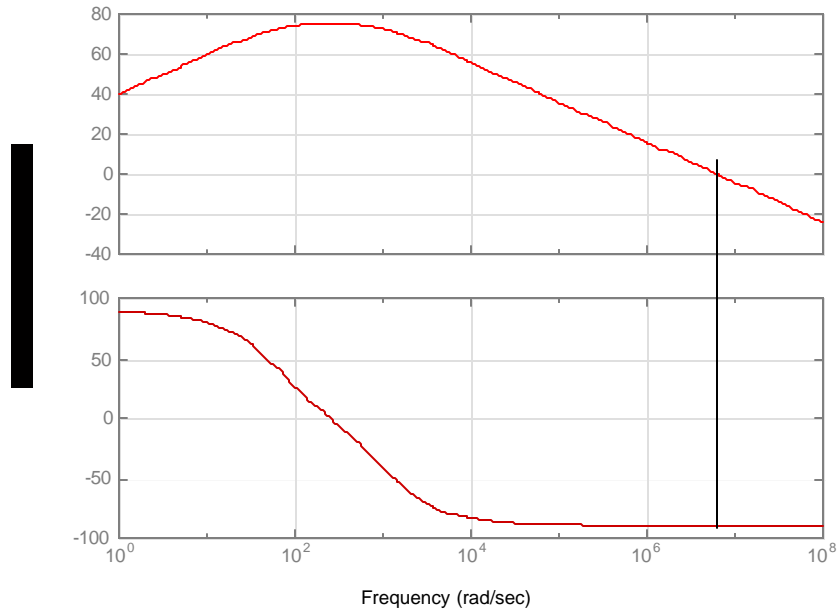

18.84

$$\mathbf{b} = \frac{sRC}{sRC + 1} = \frac{s}{s + 1000} \quad | \quad A(s) = \frac{10^5}{\left(1 + \frac{s}{2000\mathbf{p}}\right)\left(1 + \frac{s}{200000\mathbf{p}}\right)} = \frac{4\mathbf{p}^2 \times 10^{13}}{(s + 2000\mathbf{p})(s + 200000\mathbf{p})}$$


$$T = \frac{4\mathbf{p}^2 \times 10^{13} s}{(s + 2000\mathbf{p})(s + 200000\mathbf{p})(s + 1000)}$$

Using MATLAB:

```
num=[4e13*pi^2 0]; den=conv([1 1000],conv([1 2000*pi],[1 200000*pi]));
w=logspace(7,8,100); bode(num,den,w)
```

The phase margin is 1.8° which agrees with Problem 18.74.

Bode Diagrams

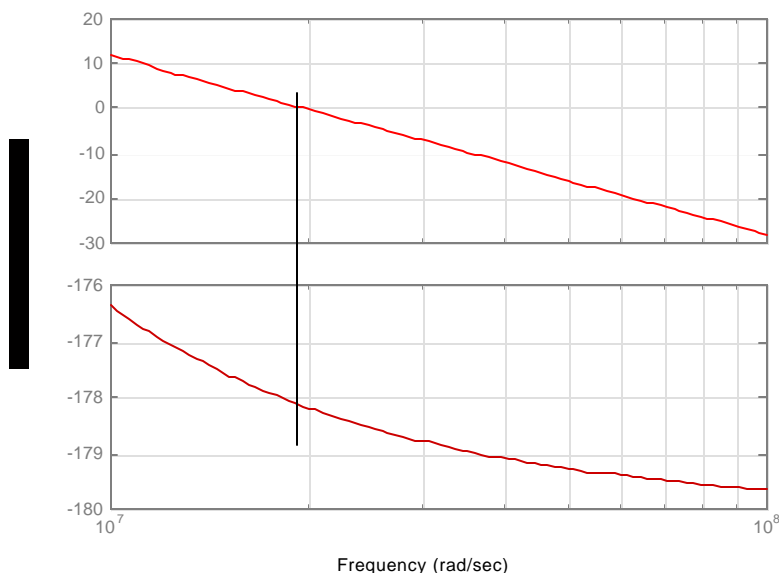

18.85

$$b(s) = \frac{\frac{R_1}{sC_s R_1 + 1}}{\frac{R_1}{sC_s R_1 + 1} + R_2} = \frac{R_1}{R_1 + R_2} \frac{1}{sC_s (R_1 \parallel R_2) + 1} = \frac{1}{9.30(1.89 \times 10^{-6} s + 1)}$$

$$b(s) = \frac{5.69 \times 10^4}{s + 5.29 \times 10^5} \quad A_v(s) = \frac{10^7}{s + 50} \quad T(s) = A_v(s)b(s)$$

$$\text{For } \omega \gg 50, |T(j\omega)| \cong \frac{5.69 \times 10^{11}}{\omega \sqrt{\omega^2 + (5.29 \times 10^5)^2}} \rightarrow |T(j\omega)| = 1 \text{ for } \omega = 6.68 \times 10^5$$

$$\Phi_M = 180 - \tan^{-1} \frac{6.68 \times 10^5}{50} - \tan^{-1} \frac{6.68 \times 10^5}{5.29 \times 10^5} = 38.4^\circ$$

18.86

$$A_{v1} = \frac{V_{o1}}{V_{o2}} = -\frac{1}{sRC} \quad V_{o2} = \left(1 + \frac{2R}{2R}\right) V_+ = 2V_+$$

$$(V_+ - V_{o1}) \frac{G}{2} + sC V_+ + (V_+ - V_{o2}) G_F = 0 \quad \text{Combining these yields}$$

$$A_{v2} = \frac{V_{o2}}{V_{o1}} = \frac{G}{sC + \left(\frac{G}{2} - G_F\right)} \quad \text{and} \quad T(s) = A_{v1} A_{v2} = \frac{1}{sRC \left(sRC + \frac{1}{2} - \frac{R}{R_F}\right)}$$

$$\angle T(j\omega_o) = 0 \rightarrow R_F = 2R \quad \text{and} \quad |T(j\omega_o)| = 1 \rightarrow \omega_o = \frac{1}{RC}$$

18.87


Define V_1 as the output of the inverting amplifier and V_2 as the output of the right-hand non-inverting amplifier.

$$V_1 = -V_2 \frac{Z_2}{Z_1} = -V_2 \frac{R}{R + \frac{1}{sC}} = -V_2 \frac{sCR}{sCR + 1} \quad | \quad V_2 = V_1 \left(\frac{R}{R + \frac{1}{sC}} \right) \left(1 + \frac{R_2}{R_1} \right) \left(\frac{R}{R + \frac{1}{sC}} \right) \left(1 + \frac{R_2}{R_1} \right)$$

$$V_2 \left[1 + \left(\frac{sCR}{sCR + 1} \right)^3 \left(1 + \frac{R_2}{R_1} \right)^2 \right] = 0 \quad | \quad \left(\frac{jwCR}{jwCR + 1} \right)^3 \left(1 + \frac{R_2}{R_1} \right)^2 = -1$$

$$3[90^\circ - \tan^{-1}(wCR)] = 180^\circ \quad | \quad \tan^{-1}(wCR) = 30^\circ \quad | \quad wCR = \tan(30^\circ) = 0.5774$$

$$\left(1 + \frac{R_2}{R_1} \right)^2 \left(\frac{wCR}{\sqrt{1 + (wCR)^2}} \right)^3 = \left(1 + \frac{R_2}{R_1} \right)^2 \left[\frac{\tan(30^\circ)}{\sqrt{1 + \tan^2(30^\circ)}} \right]^3 = 1 \rightarrow \frac{R_2}{R_1} = \sqrt{8} - 1 = 1.83$$

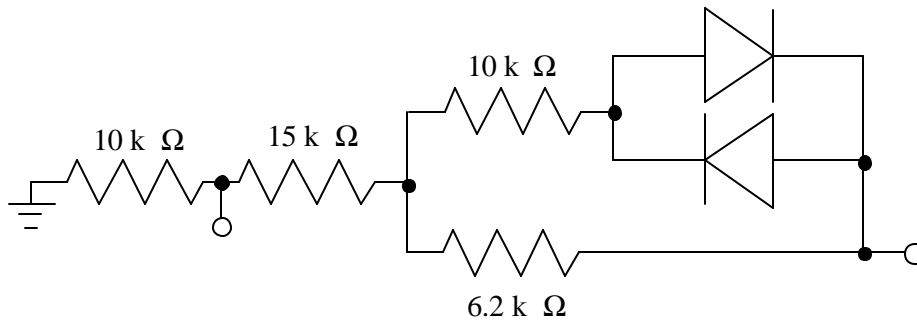18.88

$$f_o = \frac{1}{2p(5k\Omega)(500pF)} = 63.7 \text{ kHz} \quad | \quad |v_o| = \frac{3(0.7V)}{\left(2 - \frac{15k\Omega}{10k\Omega} \right) \left(1 + \frac{10k\Omega}{6.2k\Omega} \right) - \frac{10k\Omega}{10k\Omega}} = 6.85 \text{ V}$$

18.89

*Problem 18.89 - Wien-Bridge Oscillator

C1 1 0 500PF IC=1

RA 1 0 5K

C2 1 2 500PF

RB 2 3 5K

E1 3 0 1 6 1E6

R1 6 0 10K

R2 5 6 15K

R3 3 5 6.2K

R4 4 5 10K

D1 3 4 DMOD

D2 4 3 DMOD


.MODEL DMOD D

.TRAN 10U 10M UIC

.PROBE V(1) V(2) V(3) V(4) V(5) V(6)

.END

Results: f = 60.0 kHz, amplitude = 6.8 V

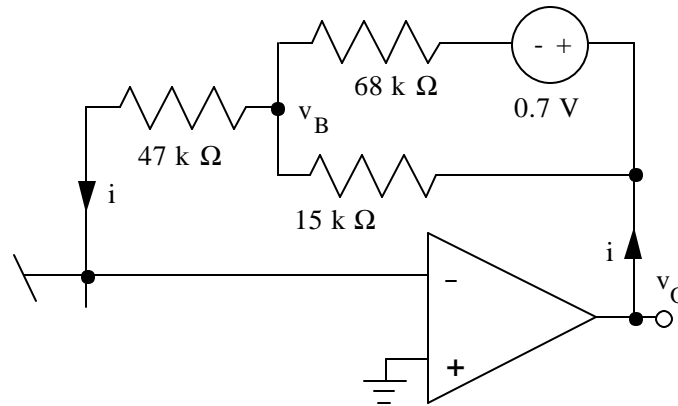18.90

Using Eq. (18.124), $f_o = \frac{1}{2\pi\sqrt{3}(5000)(10^{-9})} = 18.4 \text{ kHz}$

Using Eq. (18.125), the total feedback resistance should be $R_1 = 12R = 60\text{k}\Omega$.

The current in R_1 is $I = \frac{V_o}{R_1} = \frac{V_o}{12R} = \frac{V_o}{60\text{k}\Omega}$. The voltage at V_B is

$$V_B = I(47\text{k}\Omega) = \frac{47\text{k}\Omega}{60\text{k}\Omega} V_o \quad | \quad \text{In the diode network, } I = \frac{V_o}{60\text{k}\Omega} = \frac{V_o - V_B}{15\text{k}\Omega} + \frac{V_o - 0.7 - V_B}{68\text{k}\Omega}$$

$$\frac{13}{60} V_o + \frac{13}{60} V_o - \frac{V_o}{60\text{k}\Omega} = \frac{0.7}{68\text{k}\Omega} \rightarrow V_o = 10.7 \text{ V}$$

18.91

*Problem 18.91 - Phase Shift Oscillator

C1 1 6 1000PF IC=1

RA 1 0 5K

C2 1 2 1000PF

RB 2 0 5K

C3 2 3 1000PF

E1 3 0 0 6 1E6

R2 6 5 47K

R3 5 3 15K

R4 5 4 68K

D1 3 4 DMOD

D2 4 3 DMOD

.MODEL DMOD D

.TRAN 10U 20M UIC

.PROBE V(1) V(2) V(3) V(4) V(5) V(6)


.END

Results: $f = 17.5 \text{ kHz}$, amplitude = 11.5 V

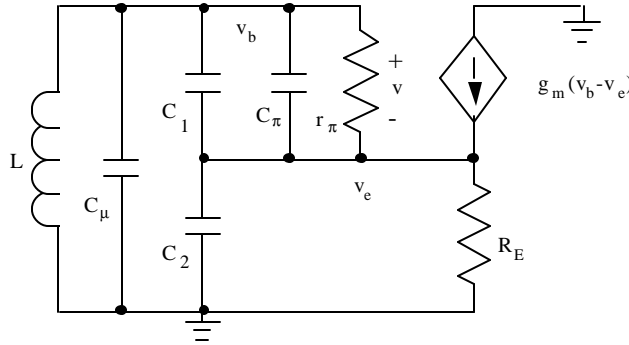18.92 Note that the presence of r_π makes the analysis more complex than the FET case. C_4 is a coupling capacitor, and its impedance is neglected in the analysis. $C_5 = C_1 + C_\pi$. However, the effect of r_π can usually be neglected in the f_o calculation as shown below.

$$\begin{bmatrix} s(C_5 + C_m) + g_p + \frac{1}{sL} & -(sC_5 + g_p) \\ -(sC_5 + g_m + g_p) & s(C_2 + C_5) + g_m + g_p + G_E \end{bmatrix} \begin{bmatrix} V_b \\ V_e \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$

$$\Delta(s) = s^2 [C_5 C_2 + C_m (C_2 + C_5)] + s [C_2 g_p + C_m (g_m + g_p + G_E) + C_5 G_E] + \frac{g_m + g_p + G_E}{sL} + g_p G_E + \frac{(C_2 + C_5)}{L}$$



$$\Delta(j\omega_o) = 0 \quad | \quad \omega_o^2 = \frac{1}{C_{TC}} \left[\frac{1}{L} + \frac{1}{r_p R_E (C_2 + C_5)} \right] = \frac{1}{C_{TC}} \left[\frac{1}{L} + \frac{g_m}{b_o R_E (C_2 + C_5)} \right] \quad | \quad C_{TC} = C_m + \frac{C_2 C_5}{C_2 + C_5}$$

$$\omega_o [C_2 g_p + C_m (g_m + g_p + G_E) + C_5 G_E] = \frac{g_m + g_p + G_E}{\omega_o L}$$

$$\omega_o^2 L \left[C_m + \frac{C_2}{b_o + 1 + \frac{r_p}{R_E}} + \frac{C_5}{1 + g_m R_E + \frac{R_E}{r_p}} \right] = 1 \quad | \quad \omega_o^2 L \left[C_m + \frac{C_2}{b_o + 1 + \frac{b_o}{g_m R_E}} + \frac{C_5}{1 + g_m R_E + \frac{g_m R_E}{b_o}} \right] = 1$$

$$(a) \quad C_{TC} = \frac{100 pF (20 pF)}{100 pF + 20 pF} = 16.7 pF \quad | \quad \omega_o^2 = \frac{1}{16.7 pF} \left[\frac{1}{5 mH} + \frac{10 mS}{100 (1 k\Omega) (100 pF + 20 pF)} \right]$$

$$\omega_o^2 = \frac{1}{16.7 pF} [2 \times 10^5 + 833] \rightarrow f_o = 17.5 MHz$$

Note that the correction term is negligible $: \omega_o \cong \frac{1}{LC_{TC}} \quad (b) \quad C_{TC} = \frac{1}{\frac{1}{C_2} + \frac{1}{C_5} + \frac{1}{C_3}}$

$$C_{TC}^{\min} = \frac{1}{\frac{1}{100pF} + \frac{1}{20pF} + \frac{1}{5pF}} = 3.85pF \quad | \quad f_o \cong \frac{1}{2p\sqrt{LC_{TC}}} = \frac{1}{2p\sqrt{(5mH)(3.85pF)}} = 36.3MHz$$

$$C_{TC}^{\max} = \frac{1}{\frac{1}{100pF} + \frac{1}{20pF} + \frac{1}{50pF}} = 12.5pF \quad | \quad f_o \cong \frac{1}{2p\sqrt{(5mH)(12.5pF)}} = 20.1MHz$$

$$(c) \quad w_o^2 L \left[\frac{C_2}{b_o + 1 + \frac{b_o}{g_m R_E}} + \frac{C_5}{1 + g_m R_E + \frac{g_m R_E}{b_o}} \right] \cong \frac{1}{C_{TC}} \left[\frac{C_2}{b_o + 1 + \frac{b_o}{g_m R_E}} + \frac{C_5}{1 + g_m R_E + \frac{g_m R_E}{b_o}} \right] = 1$$

$$\frac{1}{16.7pF} \left[\frac{100pF}{101 + \frac{100}{g_m(1k\Omega)}} + \frac{20pF}{1 + g_m(1k\Omega) + \frac{g_m(1k\Omega)}{100}} \right] = 1 \quad | \quad \text{MATLAB yields } g_m = 0.211mS$$

$$I_C = (0.211mS)(0.025V) = 5.28mA$$

18.93 Assuming the effect of r_{π} is negligible:

$$(a) \quad f_o \cong \frac{1}{2p\sqrt{C_{EQ}L}} \quad | \quad C_{EQ} = \frac{1}{\frac{1}{C_4} + \frac{1}{C_m + \frac{1}{\frac{1}{C_1 + C_p} + \frac{1}{C_2}}}} \quad | \quad C_p = \frac{40(5mA)}{10^9p} - 3pF = 60.7pF$$

$$C_{EQ} = \frac{1}{\frac{1}{0.01\mu F} + \frac{1}{3pF + \frac{1}{\frac{1}{(20 + 60.7)pF} + \frac{1}{100pF}}}} = 47.4pF \quad | \quad f_o \cong \frac{1}{2p\sqrt{47.4pF(20mH)}} = 5.17MHz$$

$$(b) \quad C_p = \frac{40(10mA)}{10^9p} - 3pF = 124pF \quad | \quad C_{EQ} = \frac{1}{\frac{1}{0.01\mu F} + \frac{1}{3pF + \frac{1}{\frac{1}{20pF + 124pF} + \frac{1}{100pF}}}} = 61.6pF$$

$$f_o \cong \frac{1}{2p\sqrt{61.6pF(20mH)}} = 4.53MHz$$

18.94

$$C_{TC} = \frac{1}{\omega_o^2 L} = \frac{1}{(4 \times 10^7 \text{ p})^2 (3 \text{ mH})} = 21.1 \text{ pF} \quad | \quad C_{TC} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}} \quad | \quad g_m R \geq \frac{C_1}{C_2} \rightarrow \frac{2I_{DS}R}{V_{GS} - V_P} \geq \frac{C_1}{C_2}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 + \frac{V_{GS}}{4} \right)^2 \quad | \quad -4 \leq V_{GS} \leq 0. \quad \text{Suppose we pick } V_{GS} \text{ in the middle}$$


$$\text{of this range : } V_{GS} = -2 \text{ V} \rightarrow I_D = 10 \text{ mA} \left(1 - \frac{2}{4} \right)^2 = 2.50 \text{ mA} \quad | \quad R = \frac{2 \text{ V}}{2.5 \text{ mA}} = 800 \Omega \rightarrow 820 \Omega$$

$$\frac{C_1}{C_2} \leq \frac{2I_D R}{V_{GS} - V_P} = \frac{2(2)}{-2 - (-4)} = 2 \quad | \quad C_1 \leq 2C_2 \quad | \quad \text{Select } C_1 \cong C_2 \cong 42 \text{ pF} \quad | \quad \text{Choosing}$$

$$C_1 = 47 \text{ pF} \text{ from Appendix C, } C_2 = \frac{1}{\frac{1}{21.1 \text{ pF}} - \frac{1}{47 \text{ pF}}} = 38.3 \text{ pF} \text{ which is close to } 39 \text{ pF}.$$

$$\text{If } 47 \text{ pF and } 39 \text{ pF are used : } f_o = \frac{1}{2\pi \sqrt{(21.3 \text{ pF})(3 \text{ mH})}} = 19.9 \text{ MHz}$$

In order to obtain an exact frequency of oscillation, a 33-pF capacitor in parallel with a small variable capacitor could be used. Note that including the FET capacitances would modify the design values.

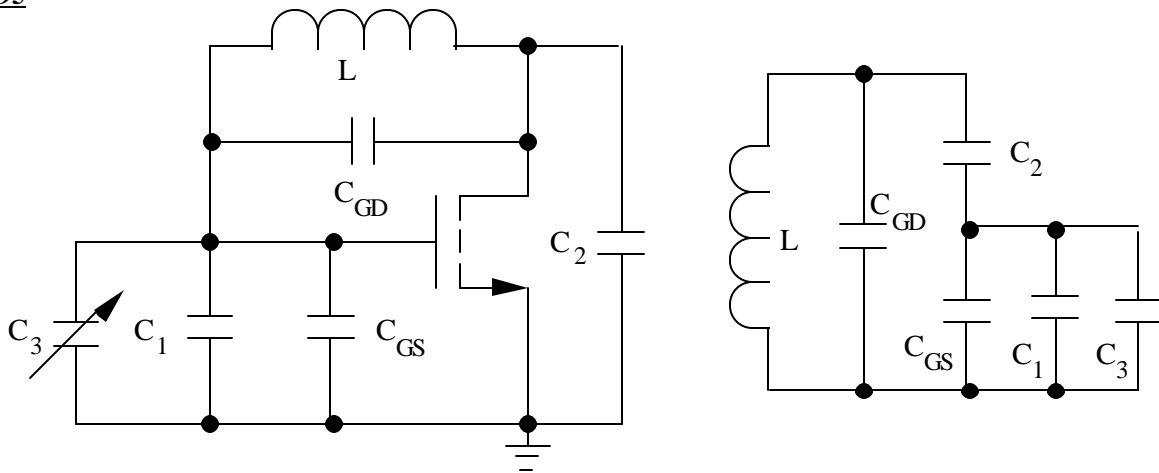18.95

$$C_{TC} = C_{GD} + \frac{1}{\frac{1}{C_2} + \frac{1}{C_1 + C_3 + C_{GS}}} = 4 \text{ pF} + \frac{1}{\frac{1}{50 \text{ pF}} + \frac{1}{50 \text{ pF} + 0 + 10 \text{ pF}}} = 31.27 \text{ pF}$$

$$f_o = \frac{1}{2\pi \sqrt{LC_{TC}}} = \frac{1}{2\pi \sqrt{(10^{-5} \text{ H})(31.27 \times 10^{-12} \text{ F})}} = 9.00 \text{ MHz}$$

$$g_m r_o \geq \frac{C_1 + C_3 + C_{GS}}{C_2} = \frac{50 \text{ pF} + 0 + 10 \text{ pF}}{50 \text{ pF}} = 1.20 \text{ which is easily met.}$$

18.96

$$(a) C_{TC} = C_{GD} + \frac{1}{\frac{1}{C_2} + \frac{1}{C_1 + C_3 + C_{GS}}} \quad | \quad C_{TC}^{\max} = 4pF + \frac{1}{\frac{1}{50pF} + \frac{1}{50pF + 5pF + 10pF}} = 32.3pF$$

$$f_o = \frac{1}{2p\sqrt{LC_{TC}}} = \frac{1}{2p\sqrt{(10mH)(32.3pF)}} = 8.87 \text{ MHz}$$

$$C_{TC}^{\min} = 4pF + \frac{1}{\frac{1}{50pF} + \frac{1}{50pF + 50pF + 10pF}} = 38.4pF \quad | \quad f_o = \frac{1}{2p\sqrt{(10mH)(38.4pF)}} = 8.12 \text{ MHz}$$

$$(b) g_m r_o \geq \frac{C_1 + C_3 + C_{GS}}{C_2} \quad | \quad g_m r_o \geq \frac{50pF + 5pF + 10pF}{50pF} = 1.30 \text{ and}$$

$$g_m r_o \geq \frac{50pF + 50pF + 10pF}{50pF} = 2.20 \quad | \quad \therefore g_m r_o \geq 2.20 \text{ which is easily met.}$$

18.97

$$(a) C_D = \frac{C_{jo}}{\sqrt{1 + \frac{V_{TUNE}}{f_j}}} \quad | \quad C_D = \frac{20pF}{\sqrt{1 + \frac{2V}{0.8V}}} = 10.7pF \quad | \quad C_{TC} = \frac{1}{\frac{1}{75pF + 10.7pF} + \frac{1}{75pF}} = 40.0pF$$

$$C_D = \frac{20pF}{\sqrt{1 + \frac{20V}{0.8V}}} = 3.92pF \quad | \quad C_{TC} = \frac{1}{\frac{1}{75pF + 3.92pF} + \frac{1}{75pF}} = 38.5pF$$

$$f_o^{\min} = \frac{1}{2p\sqrt{(10mH)(40.0pF)}} = 7.96 \text{ MHz} \quad | \quad f_o^{\max} = \frac{1}{2p\sqrt{(10mH)(38.5pF)}} = 8.11 \text{ MHz}$$

$$(b) \text{ In this circuit, } R = r_o : m_f = g_m r_o \geq \frac{C_1 + C_D}{C_2} \quad | \quad m_f \geq \frac{78.9pF}{75pF} = 1.05$$

18.98

$$C_{TC} = \frac{1}{\frac{1}{470pF} + \frac{1}{220pF}} = 150pF \quad | \quad f_o = \frac{1}{2p\sqrt{(10mH)(150pF)}} = 4.11 \text{ MHz}$$

$$\text{The required } g_m R \geq \frac{C_2}{C_1} = \frac{220pF}{470pF} = 0.468 \text{ is met :}$$

$$g_m R = \frac{2I_D R}{V_{GS} - V_P} \cong \frac{2(2.5mA)(820\Omega)}{-2 - (-4)} = 1.03$$

This analysis is borne out by the SPICE simulation below.

```
VDD 3 0 DC 10
R 1 0 820
C1 1 0 470PF IC=2
C2 2 1 220PF IC=0
*C1 1 0 220PF IC=2
*C2 2 1 470PF IC=0
```



```

L 2 0 10UH
J1 3 2 1 NFET
.MODEL NFET NJF VTO=-4 BETA=0.625MA
.OP
.TRAN 10N 30U UIC
.PROBE
.END

```

(b) For this case, the required $g_m R \geq \frac{C_2}{C_1} = \frac{470 pF}{220 pF} = 2.14$ is not met.

and the circuit fails to oscillate.

This analysis is borne out by the SPICE simulation below. The circuit does not oscillate.

18.99

$$C_{TC} = 3 pF + \frac{1}{\frac{1}{50 pF + 10 pF} + \frac{1}{50 pF}} = 30.3 pF \quad | \quad f_o = \frac{1}{2\pi \sqrt{(10 mH)(30.3 pF)}} = 9.15 MHz$$

*Problem 18.99 NMOS Colpitts Oscillator

```

VDD 3 0 DC 12
LRFC 3 2 20MH
C1 1 0 50PF
C2 2 0 50PF
L 2 1 10UH
M1 2 1 0 0 NFET
CGS 1 0 10PF
CGD 1 2 4PF
.MODEL NFET NMOS VTO=1 KP=10MA LAMBDA=0.02
.OP
.TRAN 50N 40U UIC
.PROBE
.END

```

Results: $f = 7.5 MHz$, amplitude = 80 V peak-peak. There is little to set the amplitude in this circuit, and the frequency of oscillation is significantly in error. Also, μ_f of the transistor greatly exceeds the gain required for oscillation and the waveform at the drain is highly nonlinear. The voltage at the gate is filtered by the LC network and is more sinusoidal in character. A diode from ground to gate could be employed to help limit the amplitude of the oscillation.

18.100

$$f_o = \frac{1}{2\pi \sqrt{(10 mH + 10 mH)(20 pF)}} = 7.96 MHz$$

18.101

$$f_o = \frac{1}{2\pi\sqrt{LC_{TC}}} \mid C_{TC} = \frac{1}{\frac{1}{C} + \frac{1}{C_D}} \mid C = 220\text{pF} \mid C_D = \frac{20\text{pF}}{\sqrt{1 + \frac{V_{TUNE}}{0.8V}}} \mid L = L_1 + L_2 = 20\text{mH}$$

$$(a) \ C_D = \frac{20\text{pF}}{\sqrt{1 + \frac{2V}{0.8V}}} = 10.7\text{pF} \mid C_{TC} = \frac{1}{\frac{1}{220\text{pF}} + \frac{1}{10.7\text{pF}}} = 10.2\text{pF}$$

$$f_o = \frac{1}{2\pi\sqrt{20\text{mH}(10.2\text{pF})}} = 11.1\text{MHz}$$

$$C_D = \frac{20\text{pF}}{\sqrt{1 + \frac{20V}{0.8V}}} = 3.92\text{pF} \mid C_{TC} = \frac{1}{\frac{1}{220\text{pF}} + \frac{1}{3.92\text{pF}}} = 3.85\text{pF}$$

$$f_o = \frac{1}{2\pi\sqrt{20\text{mH}(3.85\text{pF})}} = 18.1\text{MHz} \quad (b) \ m_f \geq \frac{L_1}{L_2} = 1.00$$


18.102

$$w_s = \frac{1}{\sqrt{LC_s}} \mid L = \frac{RQ}{w_s}$$

$$(a) \ L = \frac{40(25000)}{2 \times 10^7 \text{p}} = 15.915\text{mH} \mid C_s = \frac{1}{w_s^2 L} = \frac{1}{(2 \times 10^7 \text{p})^2 15.915\text{mH}} = 15.916\text{fF}$$

$$(b) \ C_p = \frac{1}{\frac{1}{15.915\text{fF}} + \frac{1}{10\text{pF}}} = 15.890\text{fF} \mid f_p = \frac{1}{2\pi\sqrt{15.915\text{mH}(15.890\text{fF})}} = 10.008\text{MHz}$$

$$(c) \ C_p = \frac{1}{\frac{1}{15.915\text{fF}} + \frac{1}{32\text{pF}}} = 15.907\text{fF} \mid f_p = \frac{1}{2\pi\sqrt{15.915\text{mH}(15.907\text{fF})}} = 10.003\text{MHz}$$

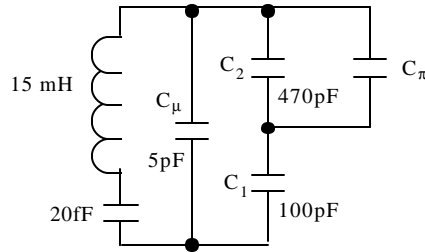18.103

$$(a) C_{TC} = \frac{1}{\frac{1}{20 fF} + \frac{1}{470 pF} + \frac{1}{100 pF}} = 19.995 fF \quad | \quad f_p = \frac{1}{2\pi\sqrt{15 mH(19.995 fF)}} = 9.190 MHz$$

$$(b) I_C = 100 \frac{5 - 0.7}{100 k\Omega + 101(1 k\Omega)} = 2.14 mA \quad | \quad C_p = \frac{40(2.14 mA)}{2\pi(2.5 \times 10^8 Hz)} - 5 pF = 49.5 pF$$

$$C_{TC} = \frac{1}{\frac{1}{20 fF} + \frac{1}{5 pF + \frac{1}{\frac{1}{100 pF} + \frac{1}{470 pF + 49.5 pF}}}} = 19.996 fF$$

$$f_p = \frac{1}{2\pi\sqrt{15 mH(19.996 fF)}} = 9.190 MHz$$

18.104

$$C_{TC}^{max} = \frac{1}{\frac{1}{20 fF} + \frac{1}{1 pF} + \frac{1}{100 pF} + \frac{1}{470 pF}} = 19.60 fF \quad | \quad f_p = \frac{1}{2\pi\sqrt{15 mH(19.60 fF)}} = 9.28 MHz$$

$$C_{TC}^{max} = \frac{1}{\frac{1}{20 fF} + \frac{1}{35 pF} + \frac{1}{100 pF} + \frac{1}{470 pF}} = 19.98 fF \quad | \quad f_p = \frac{1}{2\pi\sqrt{15 mH(19.98 fF)}} = 9.19 MHz$$

18.105

```

*Problem 18.105 BJT Colpitts Crystal Oscillator
VCC 1 0 DC 5
VEE 4 0 DC -5
Q1 1 2 3 NBJT
RE 3 4 1K
RB 2 0 100K
C1 3 0 100PF
C2 2 3 470PF
LC 2 6 15M
CC 6 5 20FF IC=5
RC 5 0 50
.MODEL NBJT NPN BF=100 VA=50 TF=1N CJC=5PF
.OP
.TRAN 2N 20U UIC
.PROBE
.END

```

In the period of time used in the simulation results, node 6 at the interior of the crystal oscillates vigorously, but the oscillation is not coupled well to the other nodes.