

**Başkent University**  
**Department of Electrical and Electronics Engineering**  
**EEM 214 Electronics I**  
**Experiment 9**

**COMMON-SOURCE JFET AMPLIFIER**

**Aim:**

1. To evaluate the common-source amplifier using the small signal equivalent model.
2. To learn what effects the voltage gain.

**Theory:**

A self-biased n-channel JFET with an AC source capacitively coupled to the gate is shown in Figure 1-a. The resistor,  $R_G$ , serves for two purposes: it keeps the gate at approximately 0 V dc (because  $I_{GSS}$  is extremely small), and its large value (usually several megohms) prevents loading of the ac signal source. The bias voltage is created by the drop across  $R_S$ . The bypass capacitor,  $C_2$ , keeps the source of the FET effectively at ac ground. The signal voltage causes the gate-to-source voltage to swing above and below its Q-point value, causing a swing in drain current. As the drain current increases, the voltage drop across  $R_D$  also increases, causing the drain voltage to decrease. The drain current swings above and below its Q-point value in-phase with the gate-to-source voltage. The drain-to-source voltage swings above and below its Q-point value  $180^\circ$  out-of-phase with the gate-to-source voltage, as illustrated Figure 1-b.

The signal voltage causes the gate-to-source voltage to swing above and below its Q-point value, causing a swing in drain current. As the drain current increases, the voltage drop across  $R_D$  also increases, causing the drain voltage to decrease. The drain current swings above and below its Q-point value in-phase with the gate-to-source voltage. The drain-to-source voltage swings above and below its Q-point value  $180^\circ$  out-of-phase with the gate-to-source voltage, as illustrated Figure 1-b.


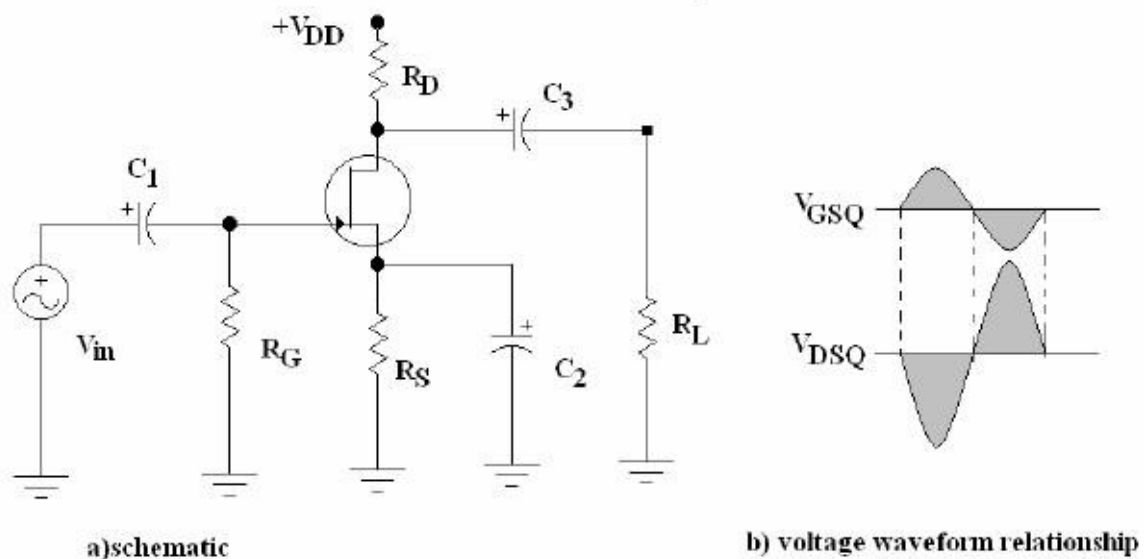


Figure 1


The operation just described for an n-channel JFET can be illustrated graphically on both the transfer characteristic curve and the drain characteristic curve in Figure 2. Figure 2-a shows how a sinusoidal variation,  $V_{gs}$ , produces a corresponding variation in  $I_d$ . As  $V_{gs}$  swings from the Q point to a more negative value,  $I_d$  decreases from its Q-point value. As  $V_{gs}$  swings to a less negative value,  $I_d$  increases. Figure 2-b shows a view of the same operation using the drain curves. The signal at the gate drives the drain current equally above and below the Q

 point on the load line, as indicated by the arrows. Lines projected from the peaks of the gate voltage across to the  $I_D$  axis and down to the  $V_{DS}$  axis indicate the peak-to-peak variations of the drain current and drain-to-source voltage, as shown.



a) JFET (n-channel) transfer characteristic curve showing signal operation

Figure 2

 

b) JFET (n-channel) drain curves showing signal operation

Small signal model of JFET is identical to that of the MOSFET in Figure 3. Here,  $g_m$  is given by

$$g_m = \frac{2 I_{DSS} V_{GS}}{|V_p| V_p} \left( 1 - \frac{V_{GS}}{V_p} \right)$$

or alternatively by

$$g_m = \left( \frac{2 I_{DSS}}{|V_p|} \right) \sqrt{\frac{I_D}{I_{DSS}}}$$

where  $V_{GS}$  and  $I_D$  are the DC bias quantities, and

$$r_o = \frac{|V_A|}{I_D} \quad \text{and} \quad g_{m0} = -2 I_{DSS} / V_p$$

At high frequencies, the equivalent circuit of Figure 4 applies with  $C_{gs}$  and  $C_{gd}$  being both depletion capacitances. Typically,  $C_{gs}=1..3$  pF,  $C_{gd}=0.1..0.5$  pF and  $f_T=20..100$  MHz; and also there is a knowledge about the following:

 


Figure 3

 


Figure 4

$$A_v = g_m (R_D // R_L) \dots \dots \dots (R_s \text{ bypass})$$

$$A_v = g_m R_d / (1 + g_m R_s), R_d = (R_D // R_L) \dots \dots (\text{normally})$$

$$I_D = 2 I_{DSS} [ (R_{sgmo} + 1) - (2 R_{sgmo} + 1)^{1/2} ] / (R_{sgmo})^2$$

For the n-channel JFET current-voltage characteristics described as follows:

—Cutoff :  $V_{GS} \leq V_p, i_D = 0$

Triode region :  $V_p \leq V_{GS} \leq 0, V_{DS} \leq V_{GS} - V_p$

$$i_D = I_{DSS} \left[ 2 \left( 1 - \frac{V_{GS}}{V_p} \right) \left( \frac{V_{DS}}{-V_p} \right) - \left( \frac{V_{DS}}{V_p} \right)^2 \right]$$

Saturation reg.:  $V_p \leq V_{GS} \leq 0, V_{DS} \geq V_{GS} - V_p$   
(pinch-off)

$$i_D = I_{DSS} \left[ 1 - \left( \frac{V_{GS}}{V_p} \right)^2 \right] \left( 1 + \lambda V_{DS} \right)$$

$\lambda$  is the inverse of the Early voltage;  $\lambda = 1/V_A$ .  $V_A$  and  $\lambda$  are positive for n-channel devices.

### Preliminary Work:

A. Find the values of  $I_D$ ,  $V_{GS}$  and  $V_{DS}$  and find  $g_m$  in the circuit of Figure 7 then fill the Table 1 in the report to compare the measured ones.

B. In questions 2 to 5, let the n-channel JFET have  $V_p = -4V$  and  $I_{DSS} = 10mA$ , and unless otherwise specified assume that in pinch-off (saturation) the output resistance is infinite.

1. For  $V_{GS} = -2V$ , find the minimum  $V_{DS}$  for the device to operate in pinch-off. Calculate  $i_D$  for  $V_{GS} = -2V$  and  $V_{DS} = 3V$ .

2. For small  $V_{DS}$ , calculate the value of  $r_{DS}$  at  $V_{GS} = 0V$  and at  $V_{GS} = -3V$ .

3. If  $V_A = 100V$ , find the JFET output resistance  $r_O$  when operating in pinch-off at a current of 1 mA, 2.5 mA and 10 mA.

C.

1. The JFET in the circuit of Figure 5 has  $V_p = -3V$ ,  $I_{DSS} = 9 mA$ , and  $\lambda = 0$ . Find the values of all resistors so that  $V_G = 5V$ ,  $I_D = 4 mA$ , and  $V_D = 11V$ . Design for 0.05 mA in the voltage divider.

2. For the JFET circuit designed in question 6, let an input signal  $v_i$  be capacitively coupled to the gate, a large bypass capacitor be connected between the source and ground, and the output signal  $v_O$  be taken from the

drain through a large coupling capacitor. The resulting common-source amplifier is shown in Figure 6. Calculate  $g_m$  and  $r_o$  (assuming  $V_A = 100V$ ). Also find  $R_i$ ,  $A_v = v_o/v_i$ , and  $R_o$ .

 


Figure 5

 


Figure 6

**Procedure:**

1. Construct the circuit in Figure 7:

 


Figure 7

2. Measure the values of  $I_D$ ,  $V_{GS}$  and  $V_{DS}$  and find  $g_m$  then fill the Table 1 in report part with your calculated values and compare the results.
3. With oscillator, obtain a 5 KHz signal with 0.5 V<sub>pp</sub> and connect to the circuit as  $V_{in}$ , observe the  $V_{out}$  signal and find the voltage gain.
4. Measure the AC voltage at source point of FET as  $V_S$  and write some comments on this occurrence.
5. Reduce the  $R_L$  and find the voltage gain.
6. Reduce the capacitor and find the voltage gain. (!Never ask “which capacitor?”!)
7. Draw all graphs for  $V_{in}$  and  $V_{out}$ , indicate the phase differences if they exist.

#### **Equipment List:**

- MPF102 FET transistor or equivalent
- DC power supply (15 V)
- Capacitors : 2\*2.2  $\mu F$ , 1\*100  $\mu F$
- Resistors: 2\*1 k $\Omega$ , 1\*4.7 k $\Omega$ , 1\*100 k $\Omega$
- Oscilloscope

#### **References:**

Microelectronic Circuits, Fourth Edition, Sedra&Smith, FET Small Signal Analysis

Electronic Devices, Third Edition, Floyd, JFET Amplifiers

**Başkent University**  
**Department of Electrical and Electronics Engineering**  
**EEM 214 Electronics I**  
**Experiment 9**

**REPORT:**

2.

**TABLE 1**

parameter	measured	calculated
$I_D$		
$V_{GS}$		
$V_{DS}$		
$g_m$		
3.		
$A_v=$		
4.		
	.....	
	.....	
	.....	
	.....	
5.		
$A_v=$		<i>(reduced <math>R_L</math>)</i>
6.		
$A_v=$		<i>(reduced <math>C_{bypass}</math>)</i>

**Drawings for 3, 5, 6:** (Draw in different colors for  $V_{in}$  and  $V_{out}$ )

Student ID # :  
Name: